

# Signals and Circuits

ENGR 35500


## Equivalent Circuit

Chapter 2-3 (Equivalent Circuits) pp. 54-62

Ulaby, Fawwaz T., and Maharbiz, Michael M., *Circuits*, 2<sup>nd</sup> Edition, National Technology and Science Press, 2013.




# Circuit Equivalence

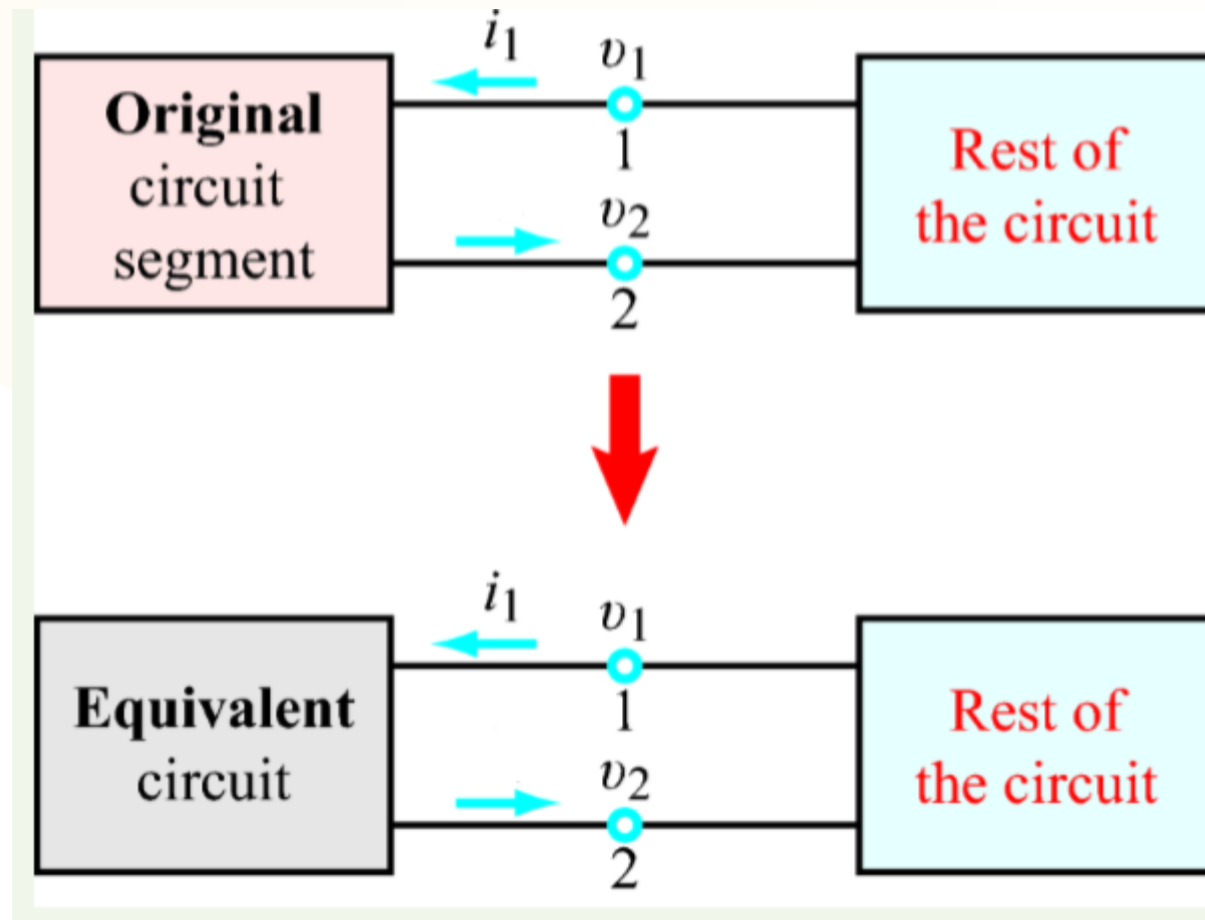

Two circuits connected between a pair of nodes are considered to be equivalent-as seen by the rest of the circuit-if they exhibit identical  $i - v$  characteristics at those nodes.

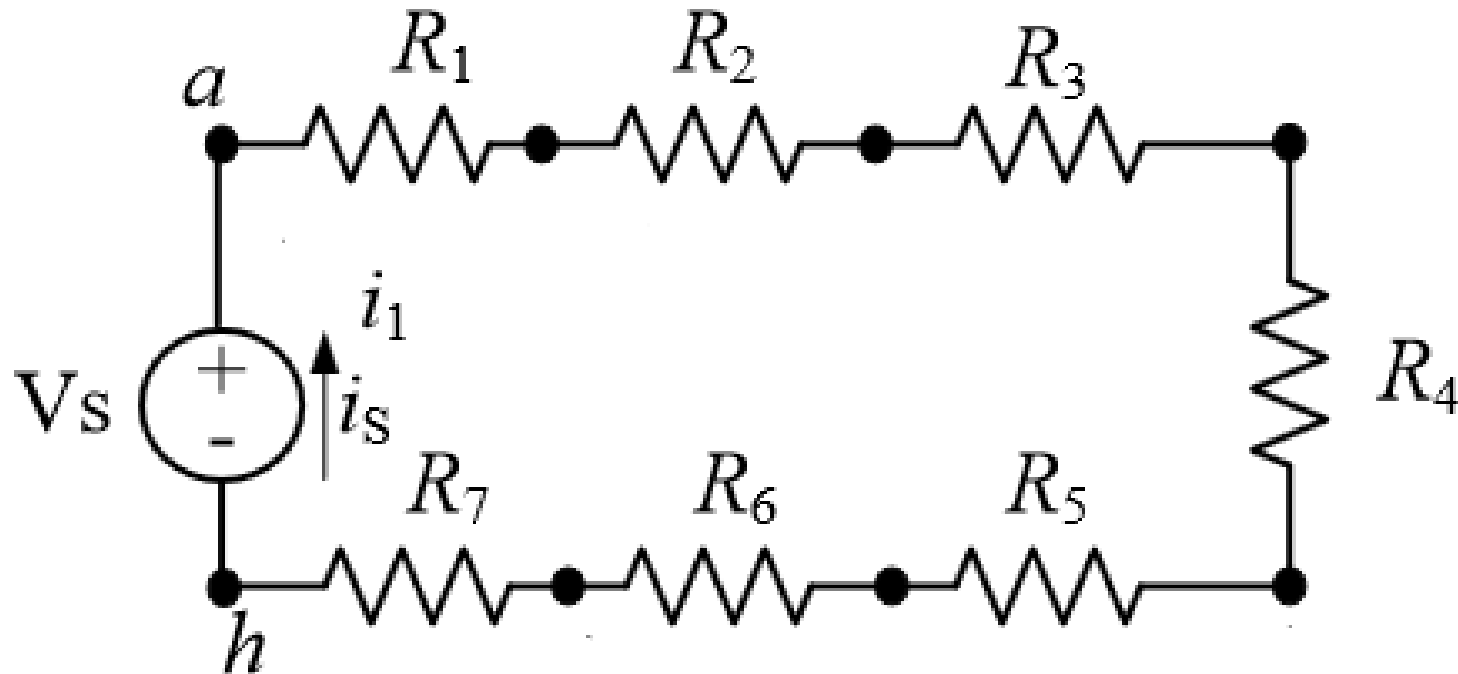
# Resistors in Series

Find the relationship between the resistors,  $i_s$  and  $V_s$


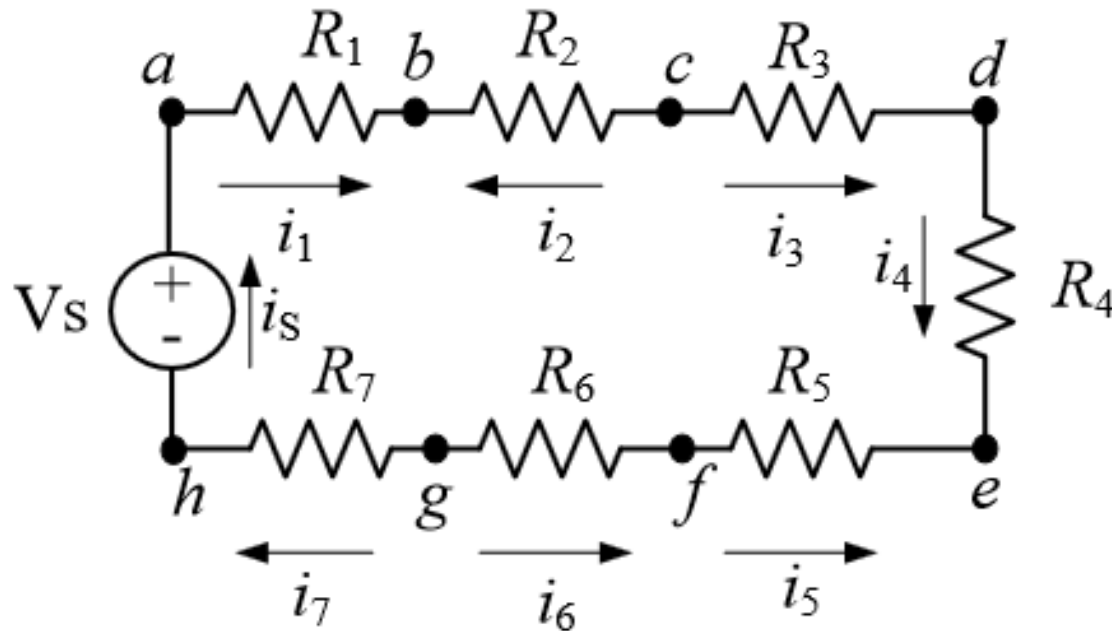
# Resistors in Series

Find the relationship between the resistors,  $i_s$  and  $V_s$



Share the same current:  $i_s = i_1 = -i_2 = i_3 = i_4 = -i_5 = -i_6 = i_7$


KVL:  $-V_s + i_s R_1 + i_s R_2 + i_s R_3 + i_s R_4 + i_s R_5 + i_s R_6 + i_s R_7 = 0$

$$\rightarrow V_s = i_s (R_1 + R_2 + R_3 + R_4 + R_5 + R_6 + R_7)$$


For nodes a and h  $V_s = i_s (R_{eq})$

$$R_{eq} = R_1 + R_2 + R_3 + R_4 + R_5 + R_6 + R_7$$

# Resistors in Series

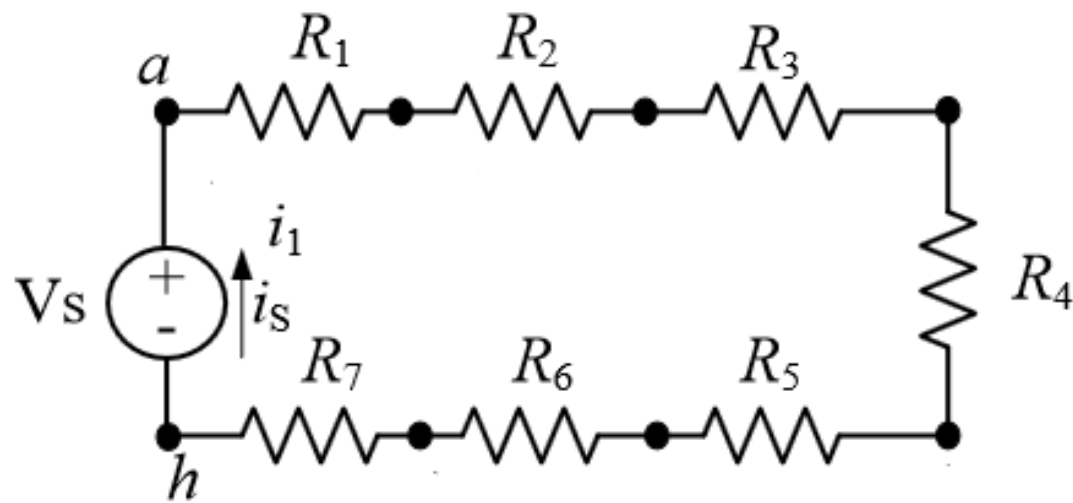

Equivalent

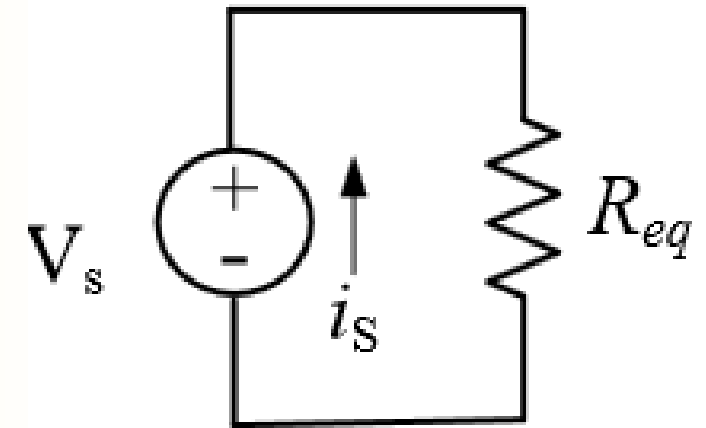


$$R_{eq} = R_1 + R_2 + R_3 + R_4 + R_5 + R_6 + R_7$$

$$\rightarrow R_{eq} = \sum_{i=1}^k R_i = (R_1 + R_2 + \dots + R_k)$$

Multiple Resistors connected in series (experiencing the same current) can be combined into a single equivalent resistor  $R_{eq}$  whose resistance is equal to the sum of all of their individual resistances.
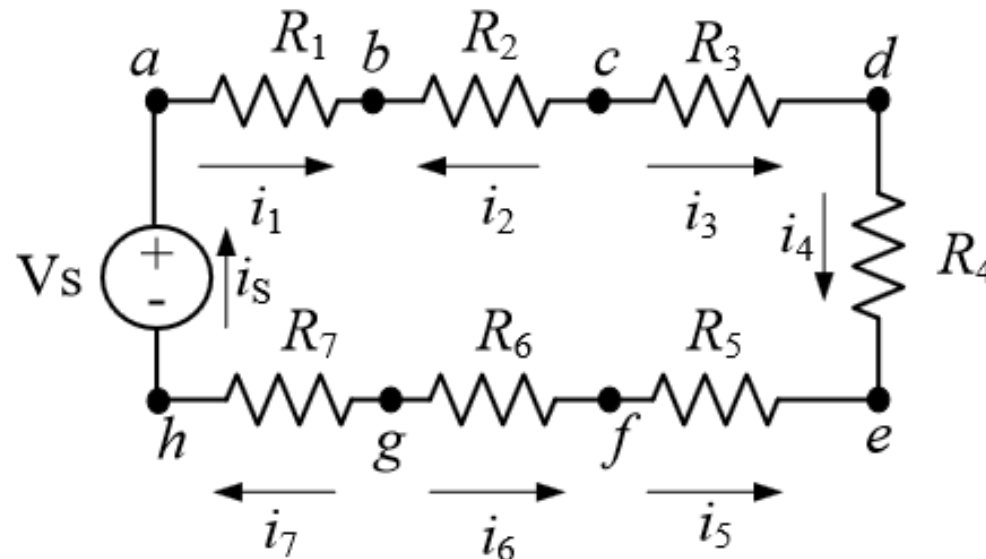
# Resistors in Series

Find the voltage across  $R_1$  and  $R_5$



Ohm's law

$$V_1 = R_1 i_s \quad (V_{ab})$$

$$V_5 = R_5 i_s \quad (V_{ef})$$

And  $R_{eq} = R_1 + R_2 + R_3 + R_4 + R_5 + R_6 + R_7$

$$V_S = i_s (R_{eq})$$

$$V_1 = \frac{R_1}{R_1 + R_2 + \dots + R_7} V_S$$

$$V_5 = \frac{R_5}{R_1 + R_2 + \dots + R_7} V_S$$


# Resistors in Series

## Voltage divider

The voltage across any individual resistor  $R_i$  in a series circuit is a proportionate fraction ( $R_i/R_{eq}$ ) of the voltage of the entire group

$$V_i = \frac{R_i}{R_{eq}} V_s$$


Example:

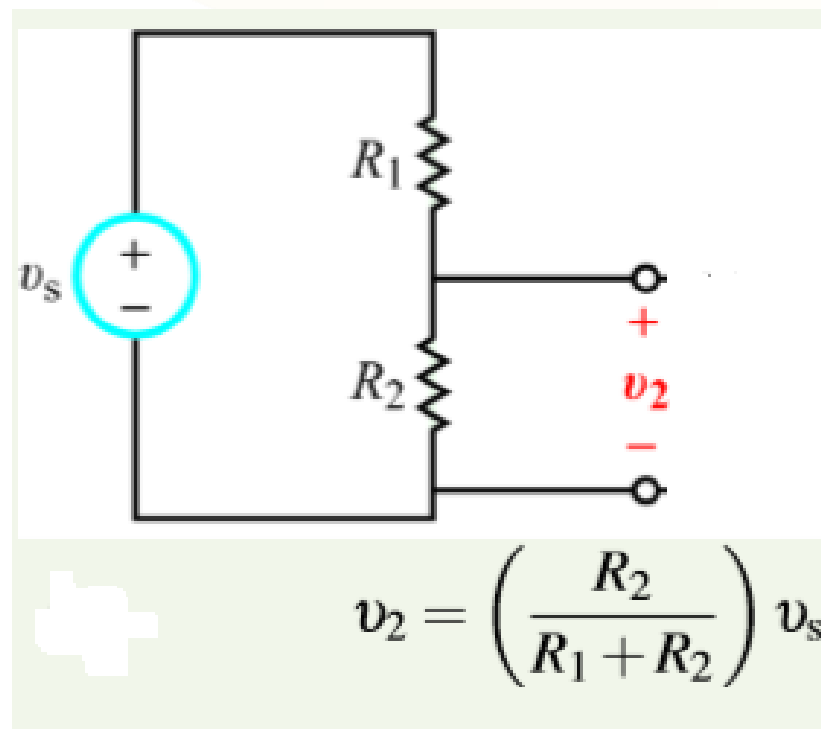


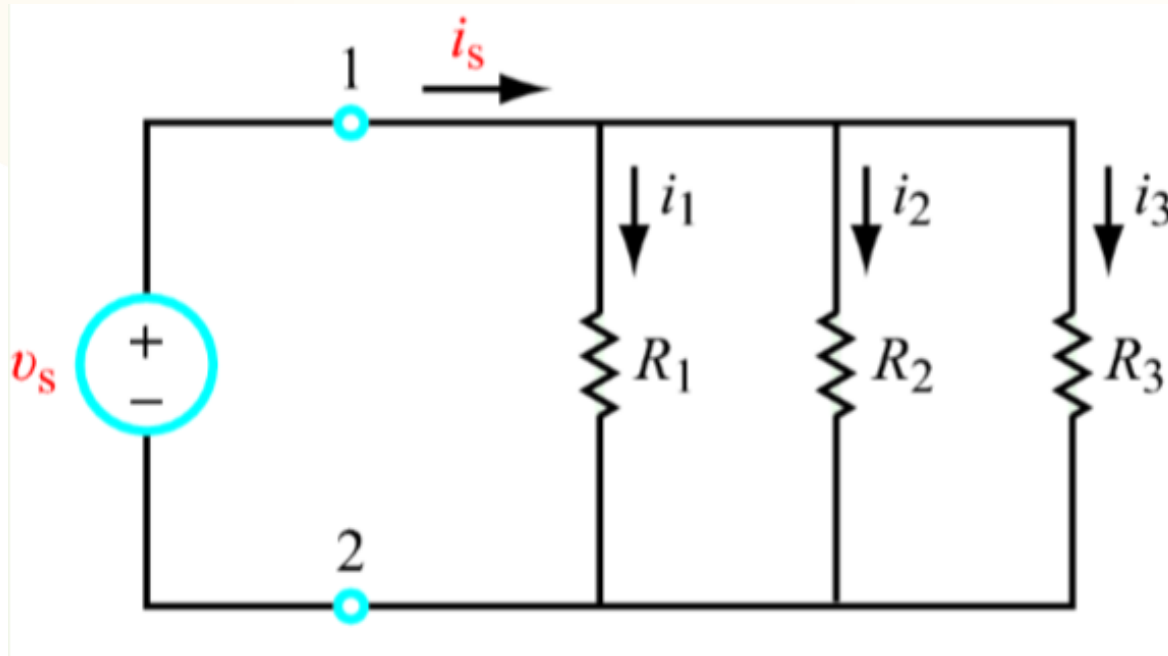
# Resistors in parallel

Find the relationship between  $i_s$ ,  $v_s$ ,  $R_1$ ,  $R_2$ ,  $R_3$



Apply ohm's law

$$i_1 = \frac{v_s}{R_1} \quad i_2 = \frac{v_s}{R_2} \quad i_3 = \frac{v_s}{R_3}$$


KCL

$$i_s = i_1 + i_2 + i_3 = \frac{v_s}{R_1} + \frac{v_s}{R_2} + \frac{v_s}{R_3}$$


$$\frac{i_s}{v_s} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \quad \longrightarrow \quad \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$



# Resistors in Parallel

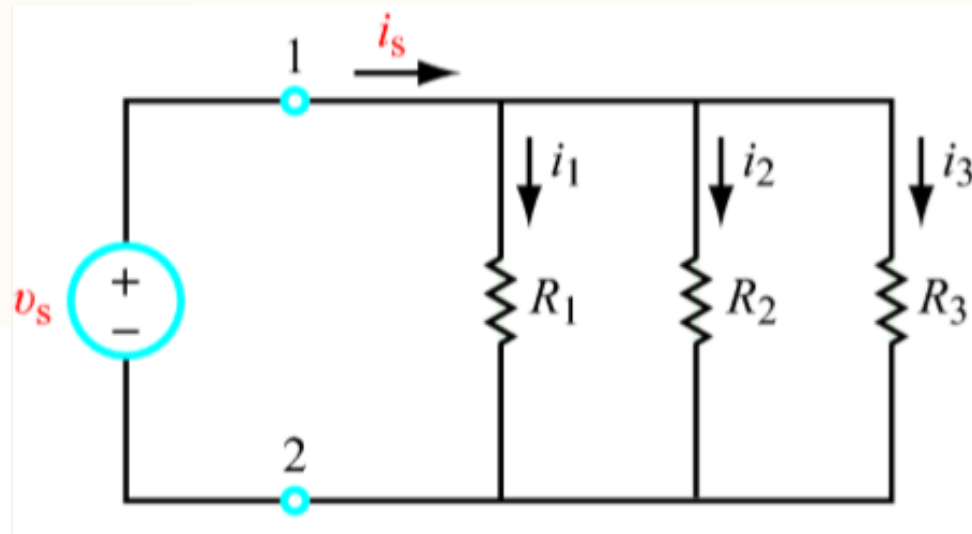

Equivalent

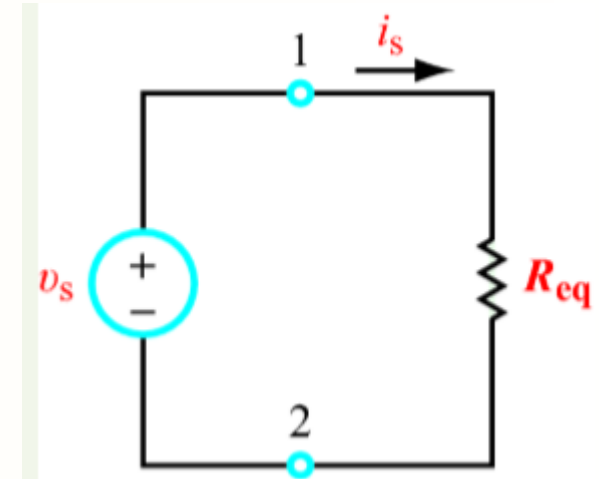


$$R_{eq} = \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1}$$

For short, we sometimes denote such a parallel  $R_1$  and  $R_2$  combination as  $R_1 || R_2$ .

# Current divider


## Current Division

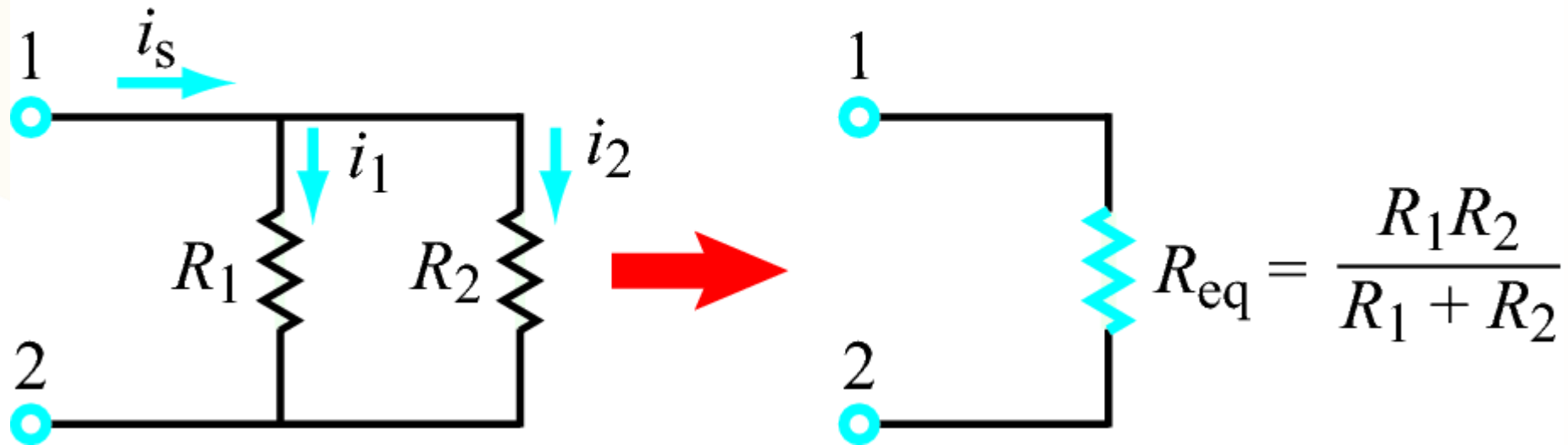

$$i_1 = \left( \frac{R_2}{R_1 + R_2} \right) i_s \quad i_2 = \left( \frac{R_1}{R_1 + R_2} \right) i_s$$


# Exercise

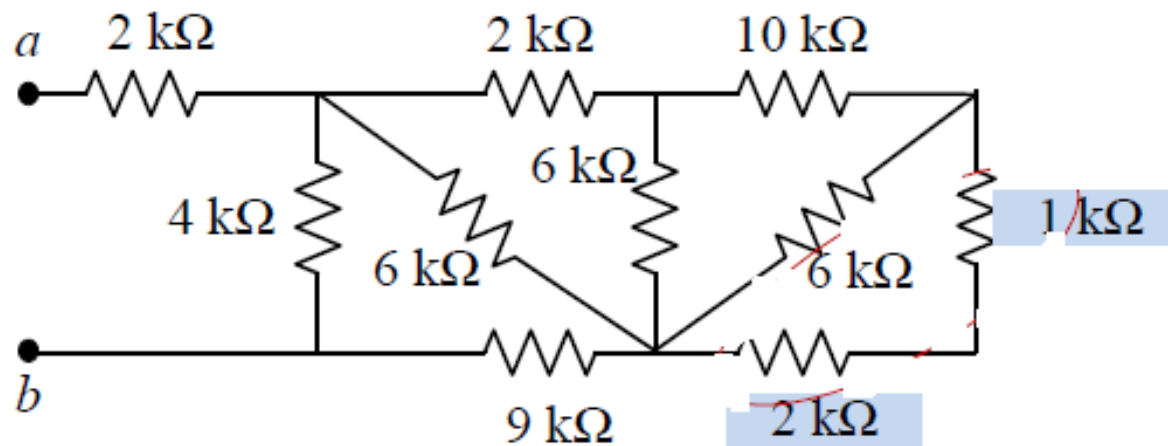Example: Find the equivalent resistance between “a” and “b”



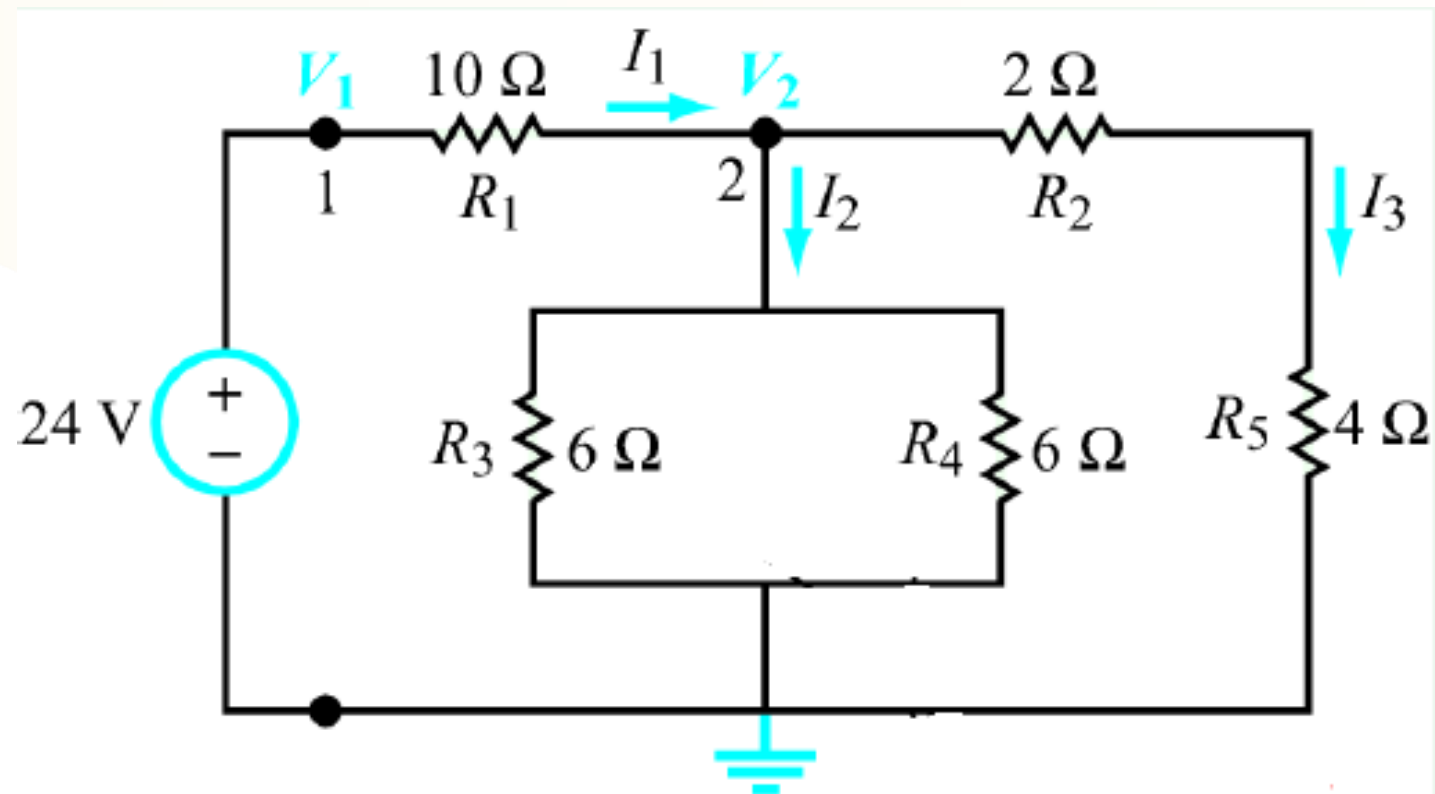
# Exercise



Use the equivalent-resistance approach to determine  $V_2$ ,  $I_1$ ,  $I_2$ , and  $I_3$  in the circuit.



# Source in series

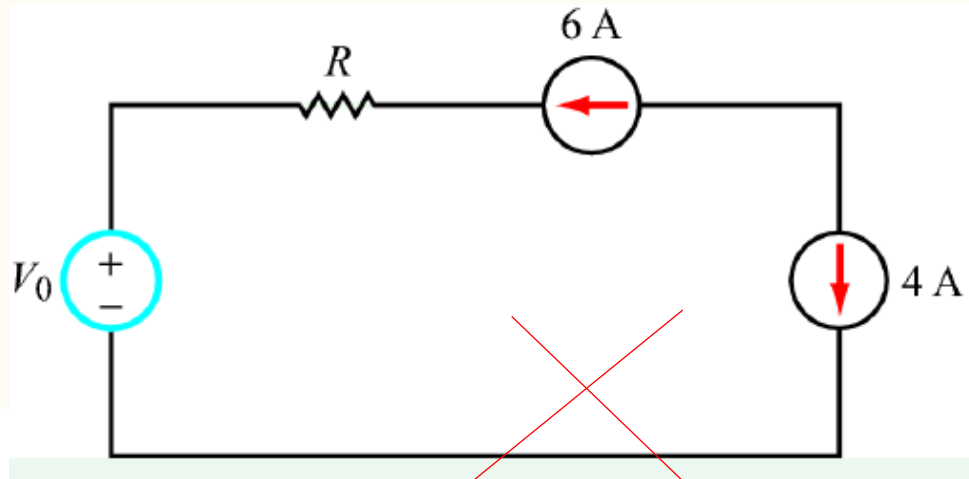

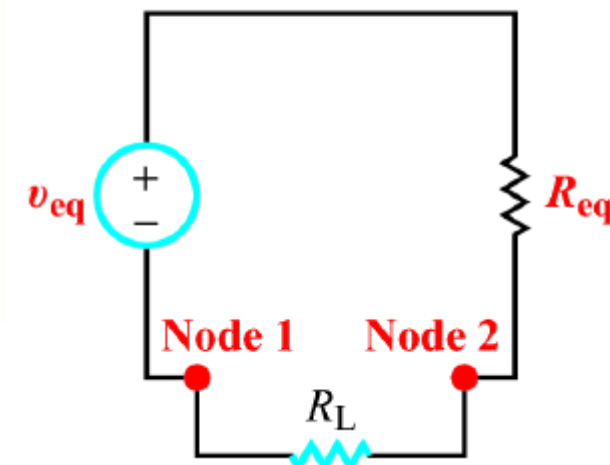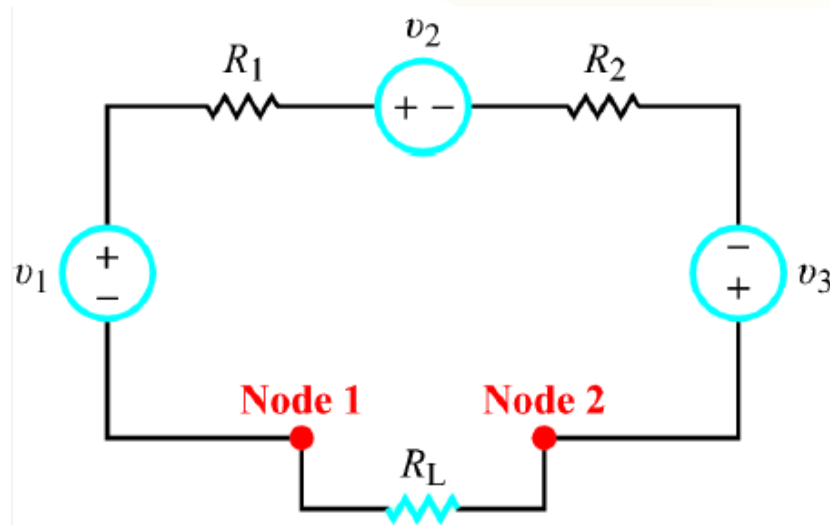
If the two current sources provide the same value current and in the same direction, so ?





$$v_{eq} = v_1 - v_2 + v_3 \quad R_{eq} = R_1 + R_2$$

Multiple voltage source connected in series can be combined into an equivalent voltage source whose voltage is equal to the algebraic sum of the voltages of the individual sources.

# Source in parallel

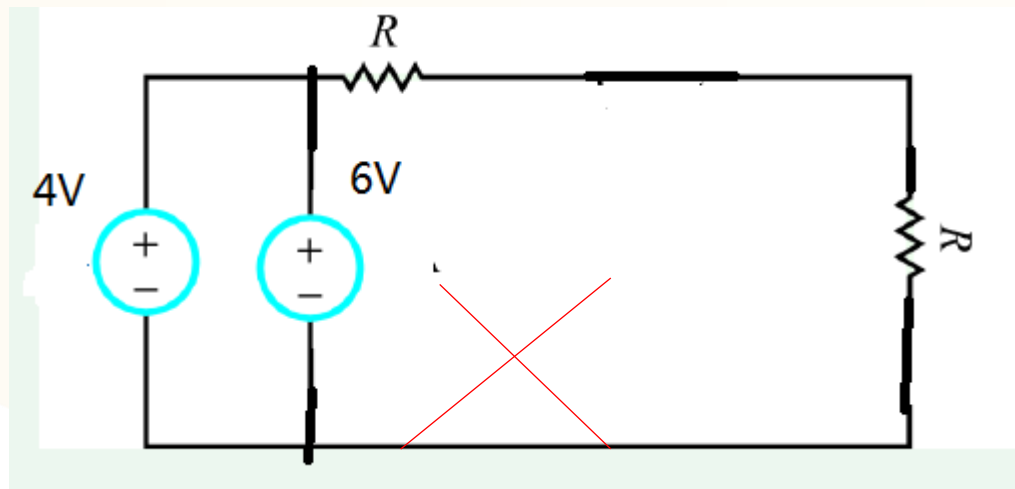

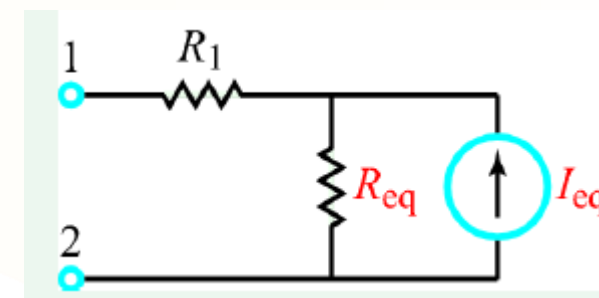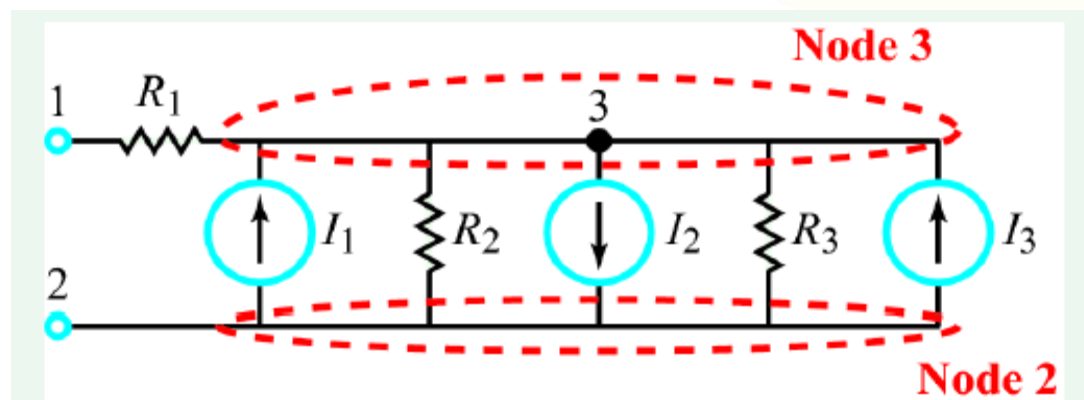
If the two voltage sources provide the same voltage and in the same direction, so ?




$$R_{eq} = R_2 \parallel R_3 = \frac{R_2 R_3}{R_2 + R_3} \quad I_{eq} = I_1 - I_2 + I_3$$
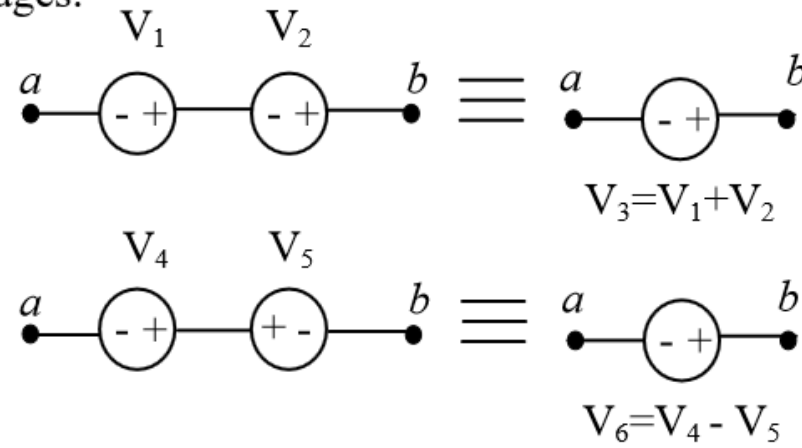
# Source in Series/parallel


- Series voltage sources have a total voltage equal to the algebraic sum of sources voltages:



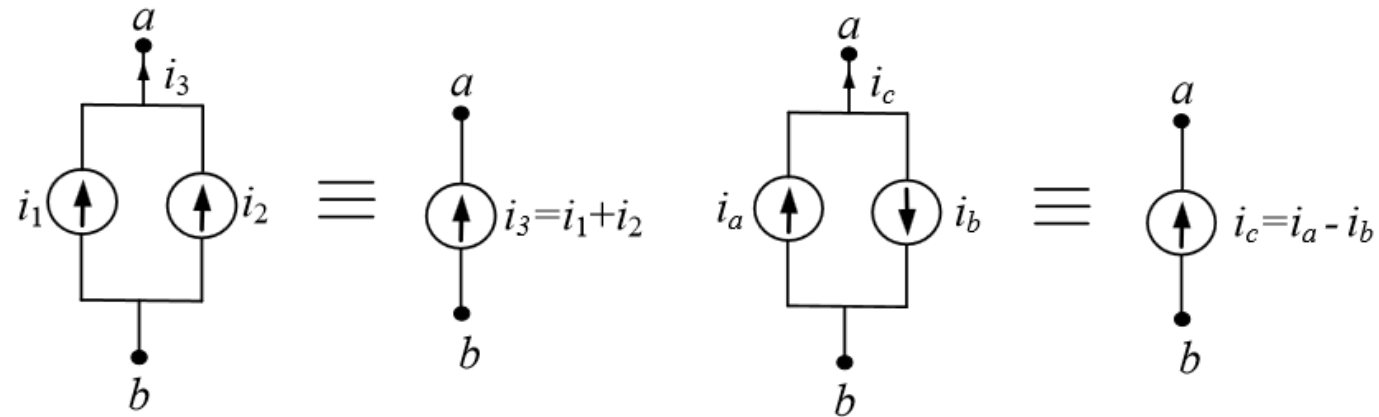- Parallel current sources have a total current equal to the algebraic sum of all sources:




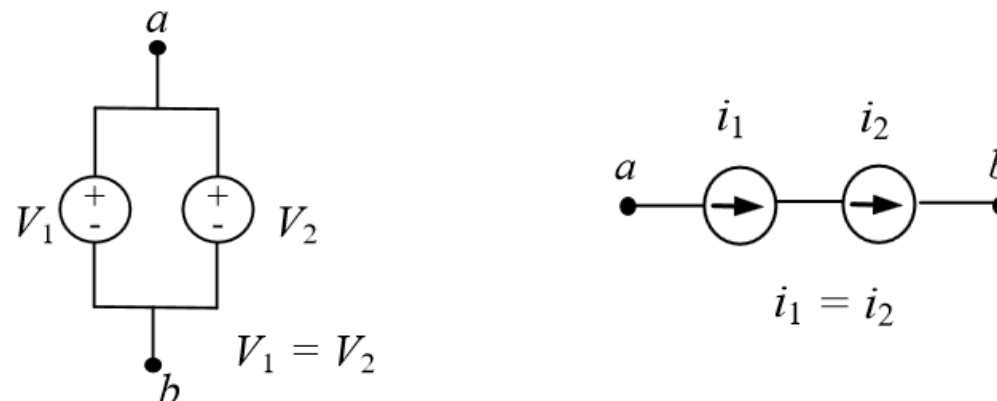- Parallel voltage sources should have the same voltage and series current sources should have the same currents:





# Source Transformation

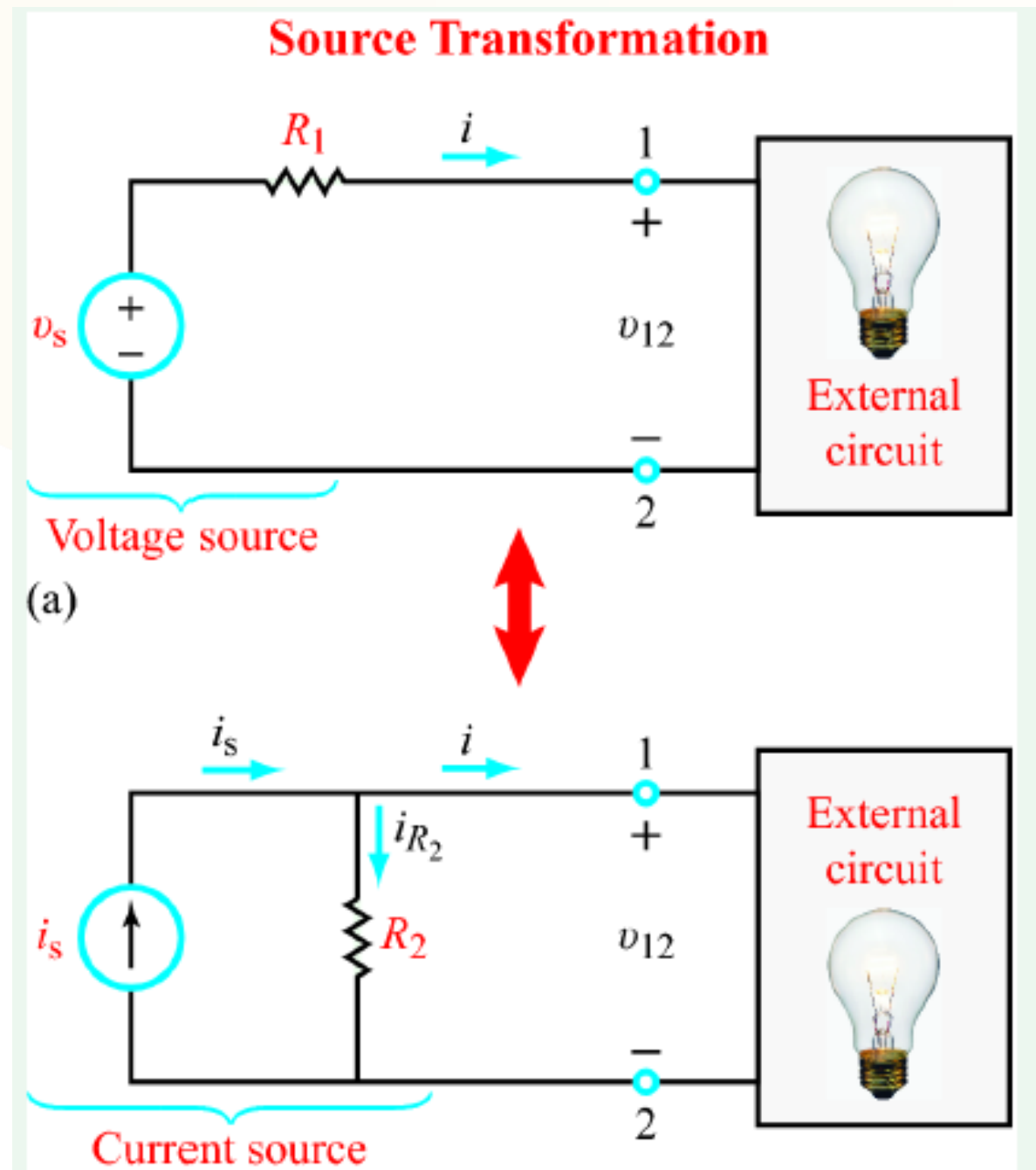

$$i_s = v_s / R_1$$
$$R_2 = R_1$$

# Exercise

