

Signals and Circuits

ENGR 35500

Power Energy Source

Chapter 1 Circuit Terminology: 1-3 (Circuit Representation) 1-5 (Voltage and Power), 1-6 (Circuit elements);
Ulaby, Fawwaz T., and Maharbiz, Michael M., *Circuits*, 2nd Edition, National Technology and Science Press, 2013.




Power of Resistor

$$p = vi = v \cdot \frac{v}{r} = \frac{v^2}{r}$$

*This equation is always correct if you measure the voltage, power and resistance simultaneously.

Circuit Architecture

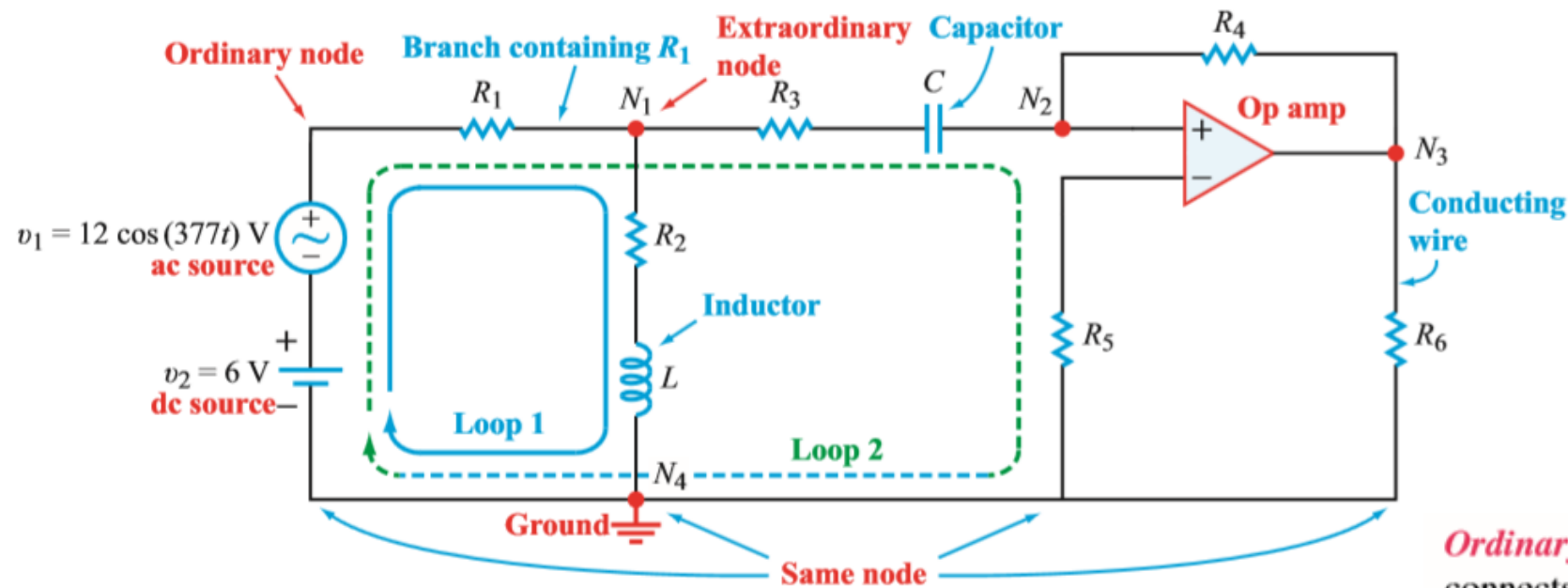

Ordinary node: An electrical connection point that connects to only two elements.

Extraordinary node: An electrical connection point that connects to three or more elements.

Branch: Trace between two consecutive nodes with only one element between them.

Path: Continuous sequence of branches with no node encountered more than once.

Extraordinary path: Path between two adjacent extraordinary nodes.

Loop: Closed path with the same start and end node.

Independent loop: Loop containing one or more branches not contained in any other independent loop.

Mesh: Loop that encloses no other loops.

In-series: Elements that share the same current.


In-parallel: Elements that share the same voltage.

Independent loop vs Mesh?

Circuit Architecture

Practice

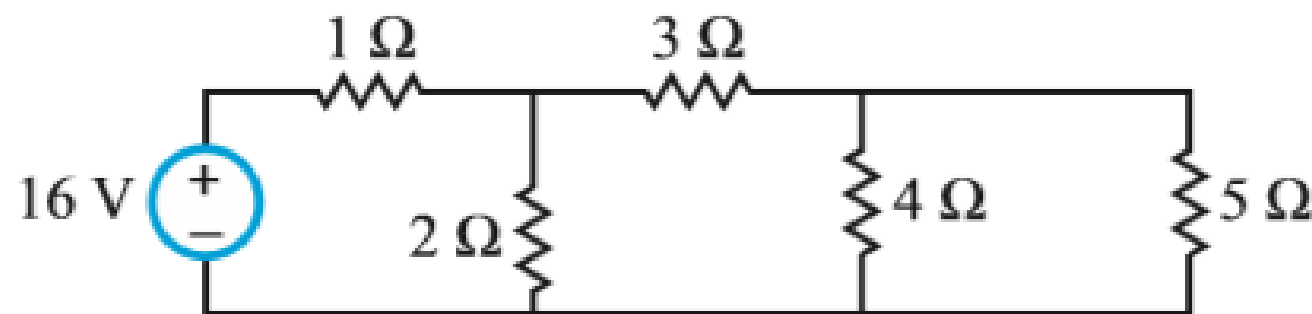- (a) Identify and label all distinct nodes.
- (b) Which of those nodes are extraordinary nodes?
- (c) Identify all combinations of 2 or more circuit elements that are connected in series.
- (d) Identify pairs of circuit elements that are connected in parallel.
- (e) Identify the mesh loops.



Ordinary node: An electrical connection point that connects to only two elements.

Extraordinary node: An electrical connection point that connects to three or more elements.

Branch: Trace between two consecutive nodes with only one element between them.

Path: Continuous sequence of branches with no node encountered more than once.

Extraordinary path: Path between two adjacent extraordinary nodes.

Loop: Closed path with the same start and end node.


Independent loop: Loop containing one or more branches not contained in any other independent loop.

Mesh: Loop that encloses no other loops.


In-series: Elements that share the same current.

In-parallel: Elements that share the same voltage.

Planar Circuit

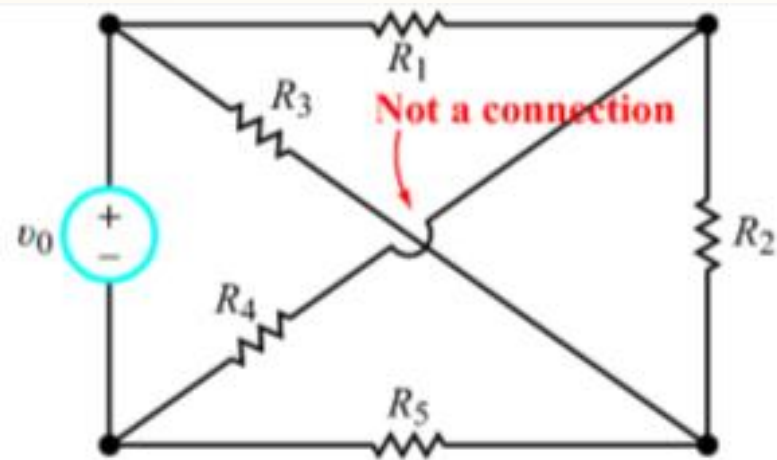


(a) Original circuit

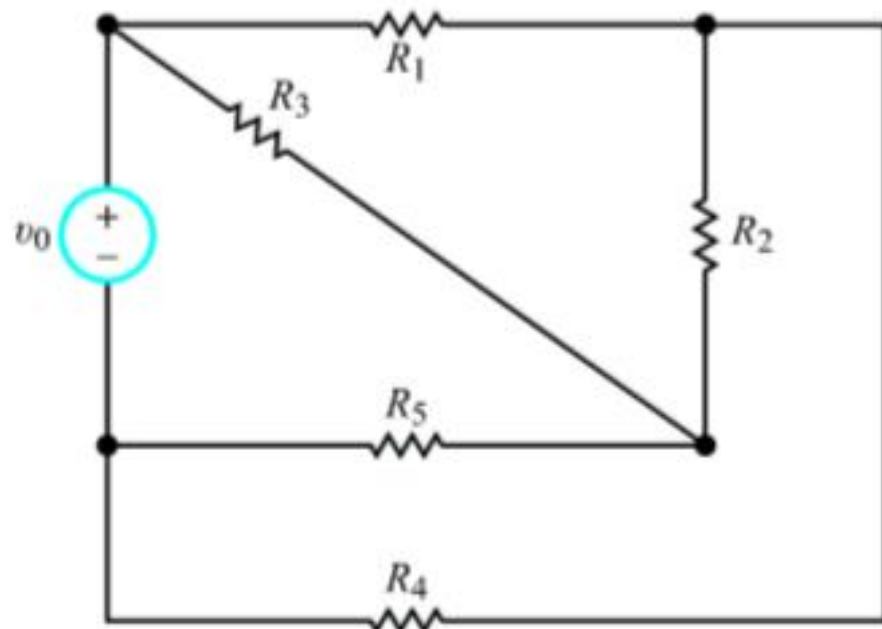


(b) Redrawn

Planar circuit

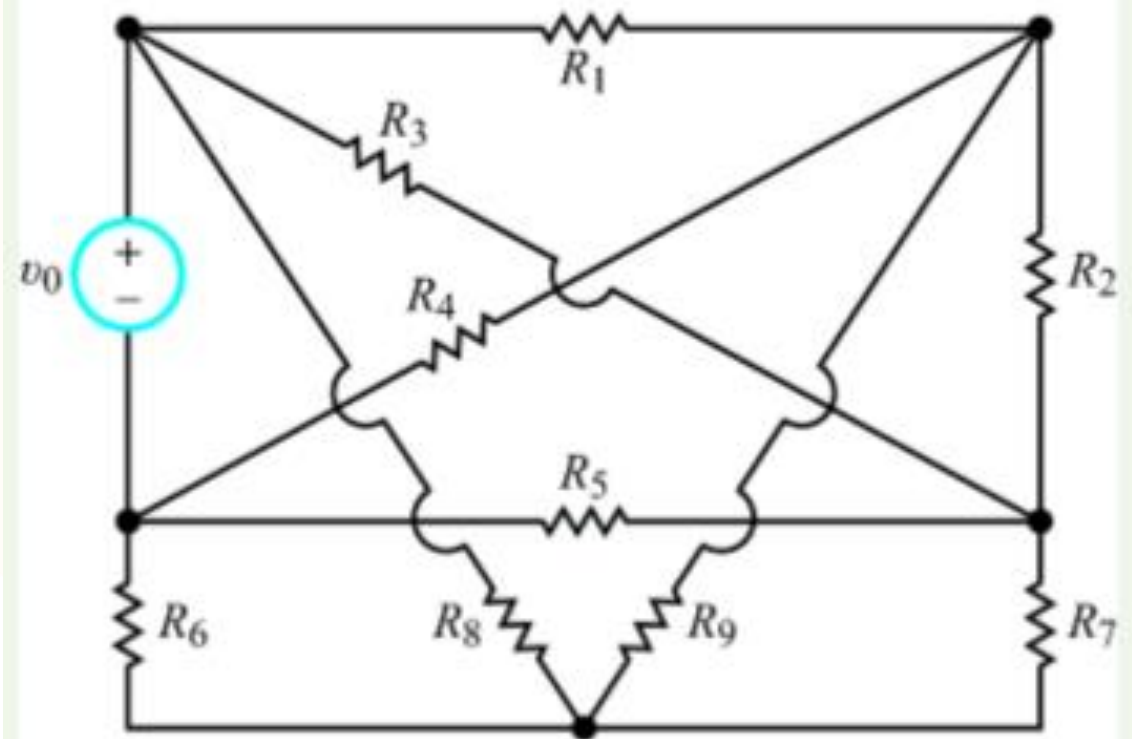

Nonplanar circuit

Open and short circuits

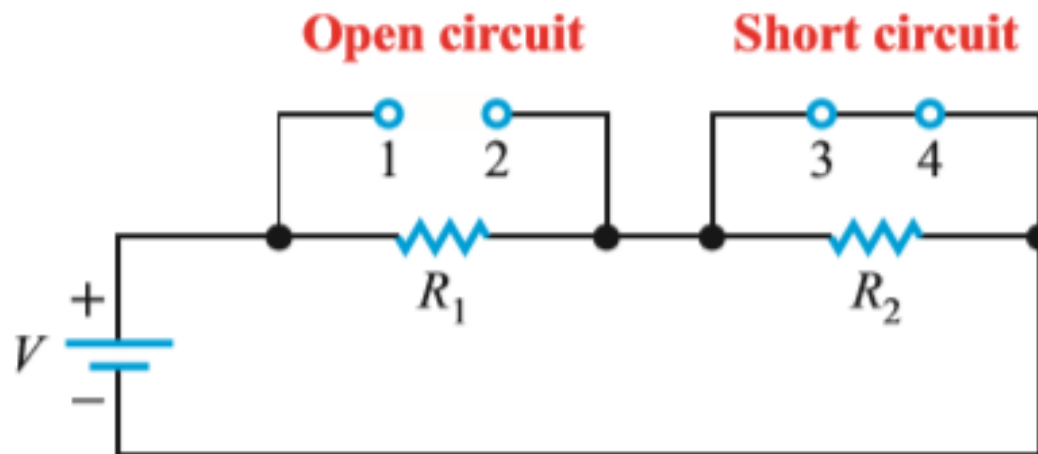


An **open circuit** refers to the condition of path discontinuity (infinite resistance) between two points. No Current can flow through an open circuit, regardless of the voltage across it.

A **short circuit** constitutes the condition of complete path continuity (with zero electrical resistance) between two points.

Power sources

Independent source

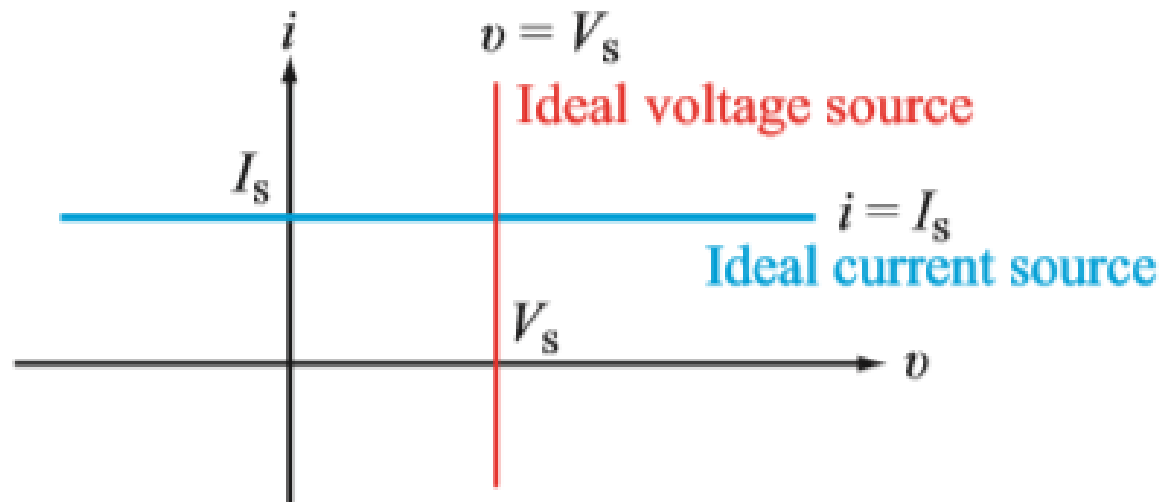


An **ideal, independent voltage source** provides a specified **voltage** across its terminals, regardless of the type of load or circuit connected to it.

An **ideal, independent current source** provides a specified **current** flowing the circuit, regardless of the type of load or circuit connected to it (**cannot do so if connected to an open circuit**).

Power sources

Independent source




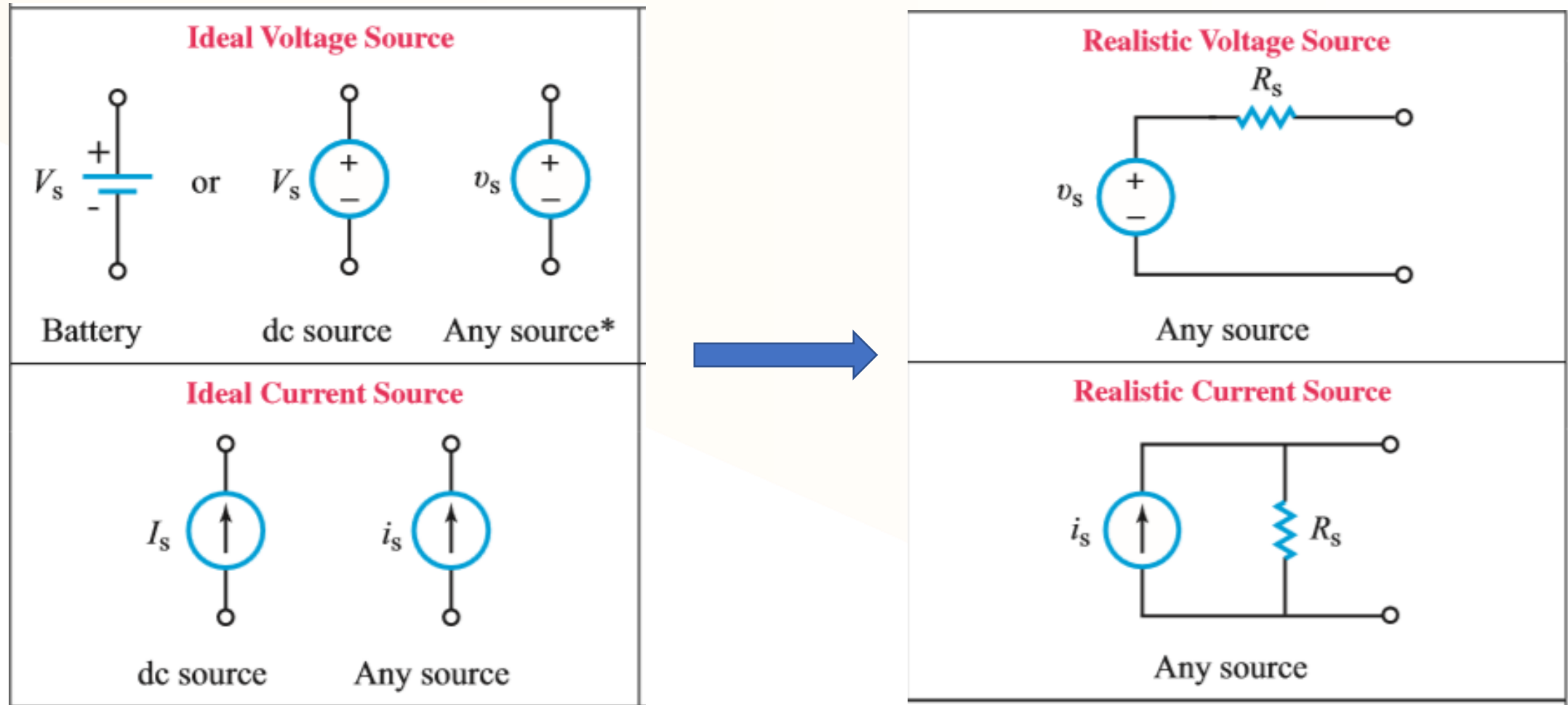


R_s ?

Power sources





Dependent source


The source depends on the relationship between the characteristics of the source and the current or voltage of other devices.

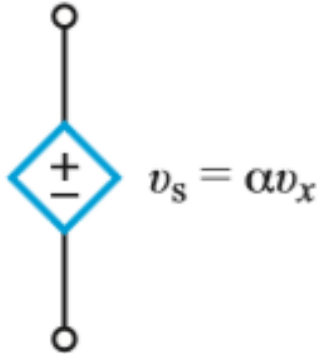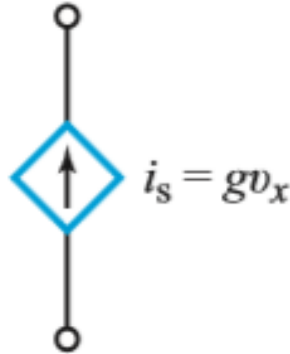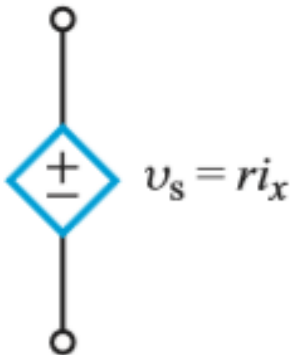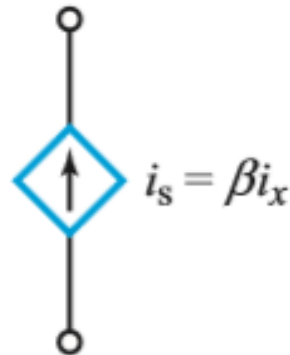Dependent Sources	
Voltage-Controlled Voltage Source (VCVS)  $v_s = \alpha v_x$	Voltage-Controlled Current Source (VCCS)  $i_s = g v_x$
Current-Controlled Voltage Source (CCVS)  $v_s = r i_x$	Current-Controlled Current Source (CCCS)  $i_s = \beta i_x$
<p><i>Note:</i> α, g, r, and β are constants; v_x and i_x are a specific voltage and a specific current elsewhere in the circuit.</p> <p>*Lowercase v and i represent voltage and current sources that may or may not be time varying, whereas uppercase V and I denote dc sources.</p>	

Power sources

Dependent source

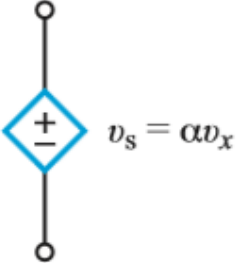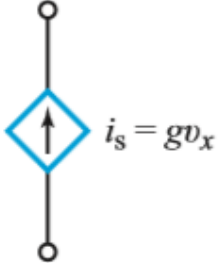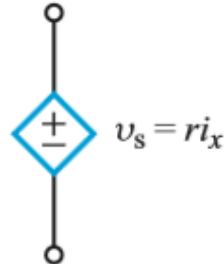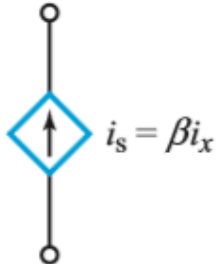Dependent Sources	
Voltage-Controlled Voltage Source (VCVS)  $v_s = \alpha v_x$	Voltage-Controlled Current Source (VCCS)  $i_s = g v_x$
Current-Controlled Voltage Source (CCVS)  $v_s = r i_x$	Current-Controlled Current Source (CCCS)  $i_s = \beta i_x$
<p><i>Note:</i> α, g, r, and β are constants; v_x and i_x are a specific voltage and a specific current elsewhere in the circuit.</p> <p>*Lowercase v and i represent voltage and current sources that may or may not be time varying, whereas uppercase V and I denote dc sources.</p>	

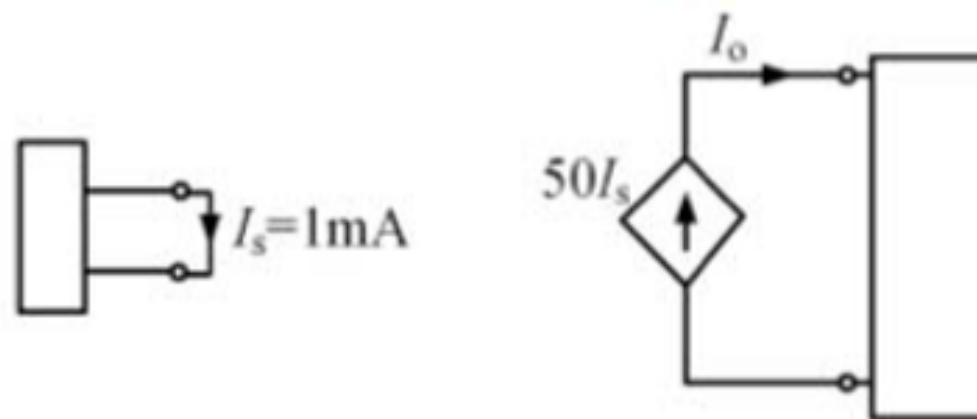

Power sources

Dependent source

Determine V , the voltage of the dependent voltage source in the circuit.

