

Signals and Circuits

AERN 35500

Capacitors

Chapter 5: 5-1(Capacitor) pp. 211-220;


Ulaby, Fawwaz T., and Maharbiz, Michael M., *Circuits*, 2nd Edition, National Technology and Science Press, 2013.



Capacitor

Capacitor is a passive element.

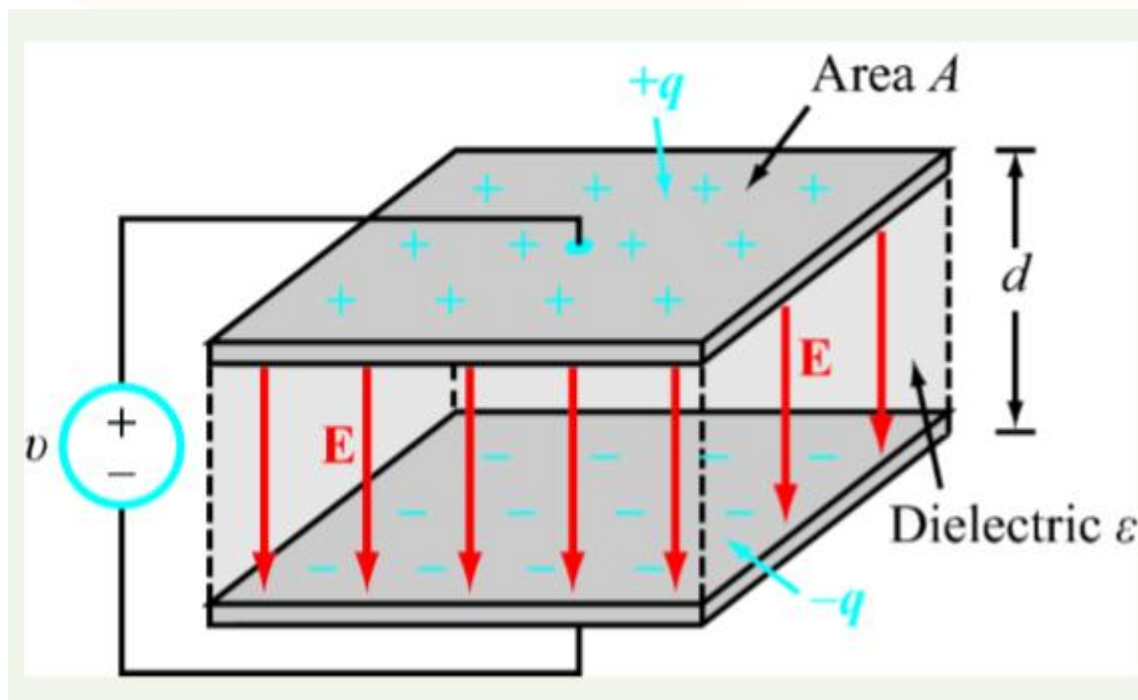A capacitor is an electrical device constructed of two parallel conductive plates separated by an insulating material called the dielectric.



It can store energy/charge and give it back at a later time.


Capacitor

Application

- **Store energy**
- **A filter**
- **Decoupling and coupling signals**
- **Circuit protection**

Capacitor

How a capacitor stores the charge.

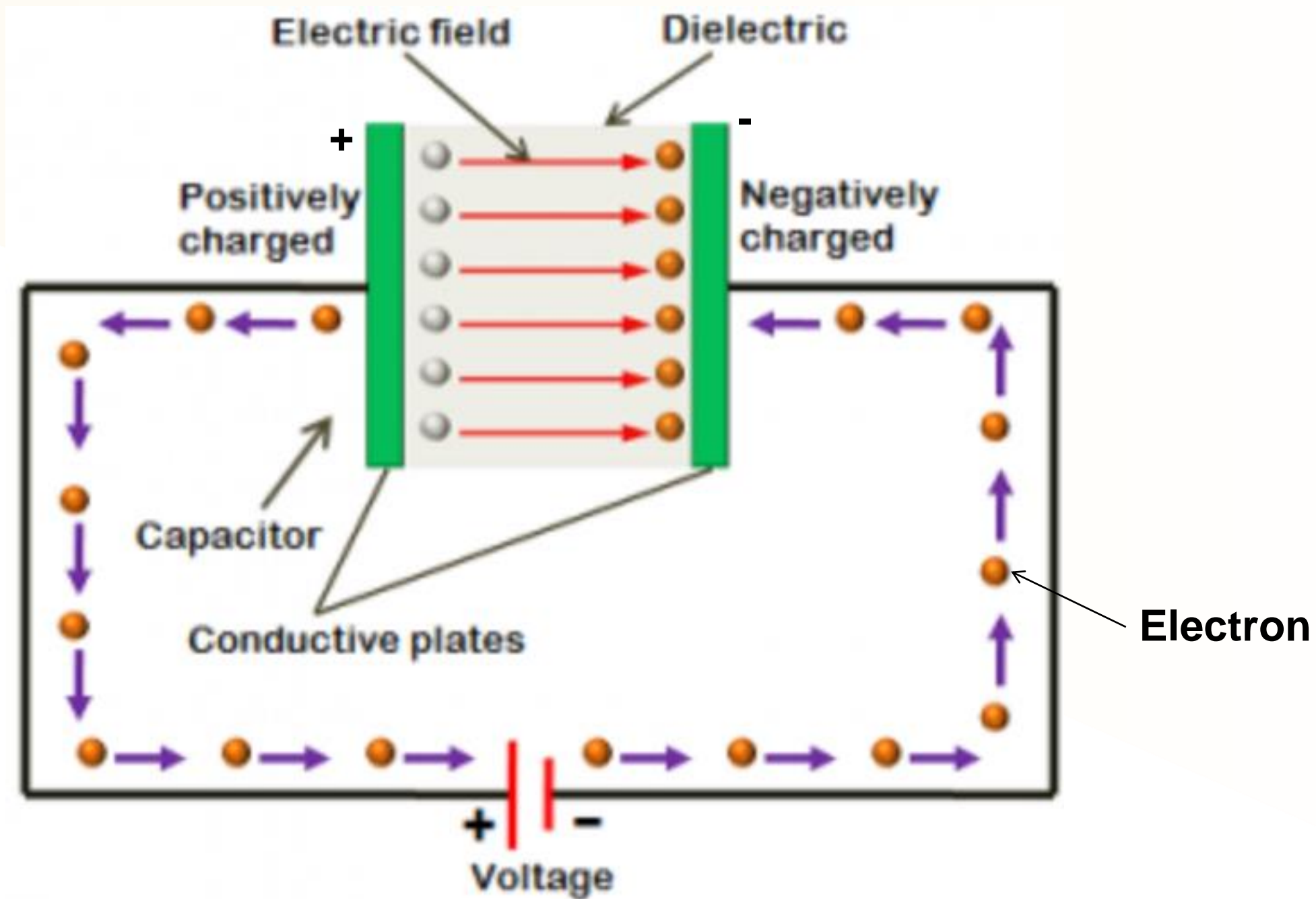

<https://www.pinterest.co.uk/pin/405957353891688200/>

Capacitor

The amount of charge that a capacitor can store per unit of voltage across its plates is its **capacitance**, designated C .


$$C = \frac{q}{v} \quad (F)$$

q is the charge of the capacitor
 v is the voltage applied between its terminals

Coulomb/Volt \equiv Farad

after Michael Faraday

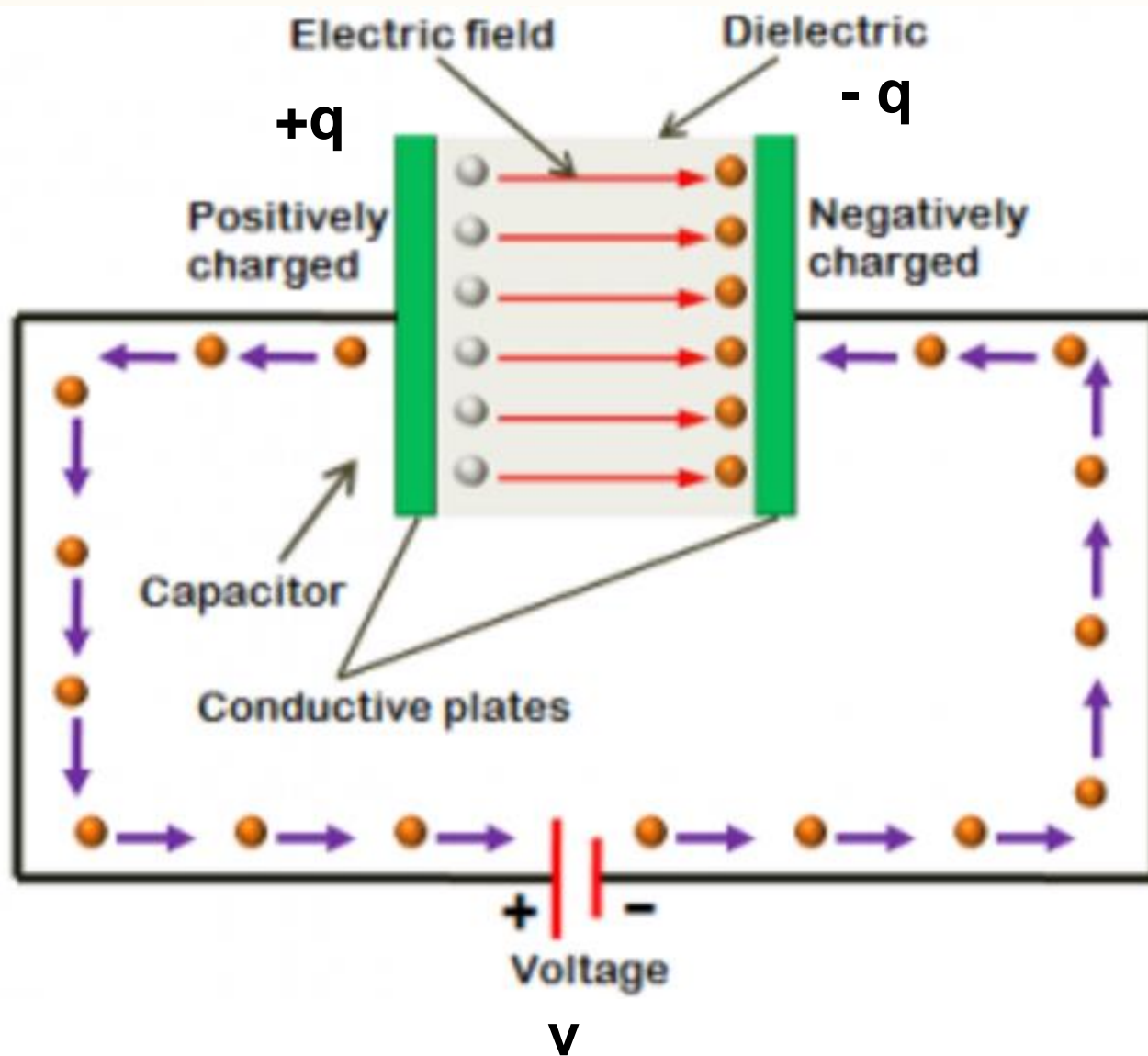- A farad is the amount of capacitance that can store 1 coulomb (C) of charge when the capacitor is charged to 1 volt.
- 1 microfarad (μF) = 10^{-6} farad
- 1 nanofarad (nF) = 10^{-9} farad
- 1 picofarad (pF) = 10^{-12} farad



<https://www.pinterest.co.uk/pin/405957353891688200/>

Capacitor


The amount of charge that a capacitor can store per unit of voltage across its plates is its **capacitance**, designated C .

$$C = \frac{q}{v} \quad (F)$$


E. g.

A $2.2 \mu F$ capacitor has 100 v across its plates. How much charge does it store?


Capacitor

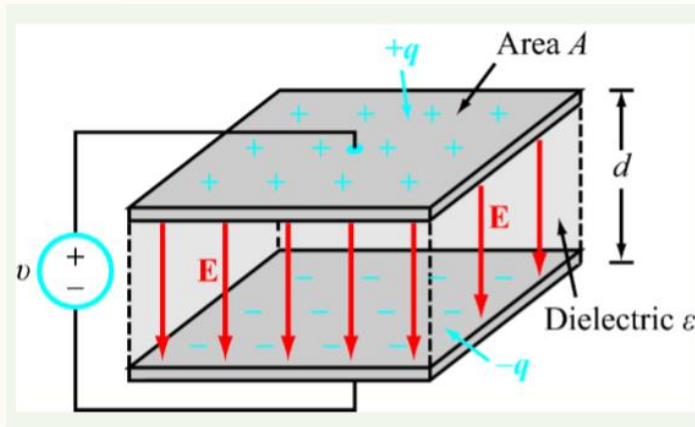


Parallel-plate capacitor

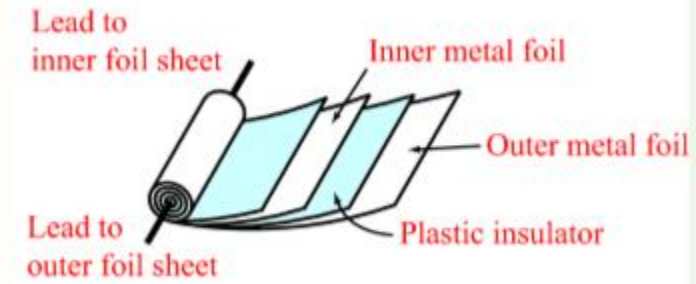



Coaxial capacitor

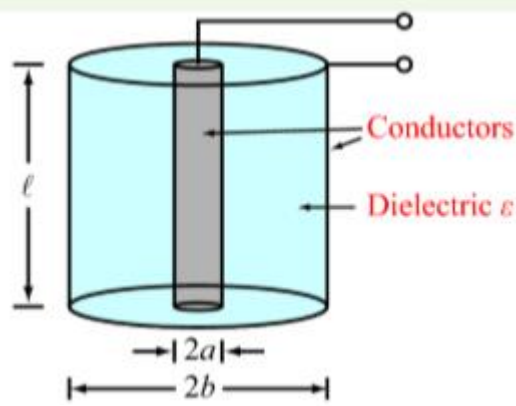

Coaxial capacitor

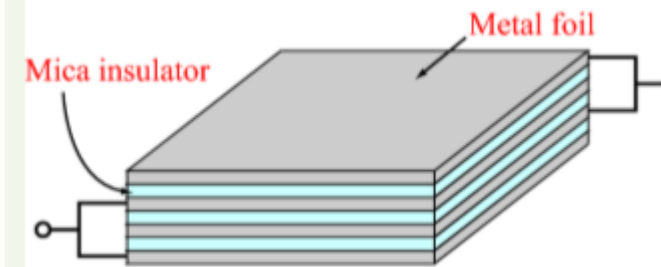

Mica capacitor

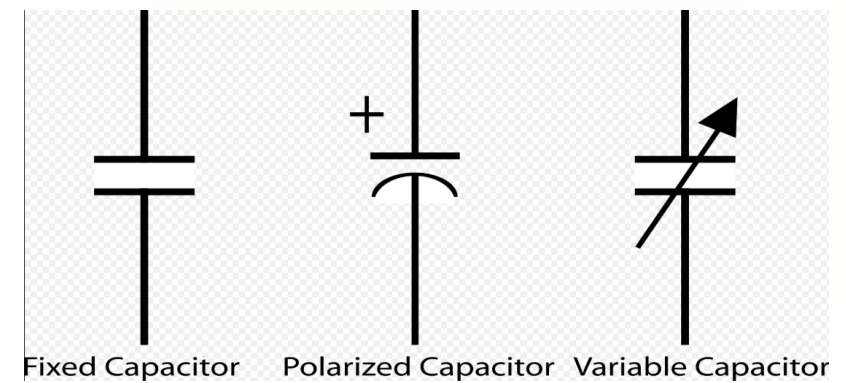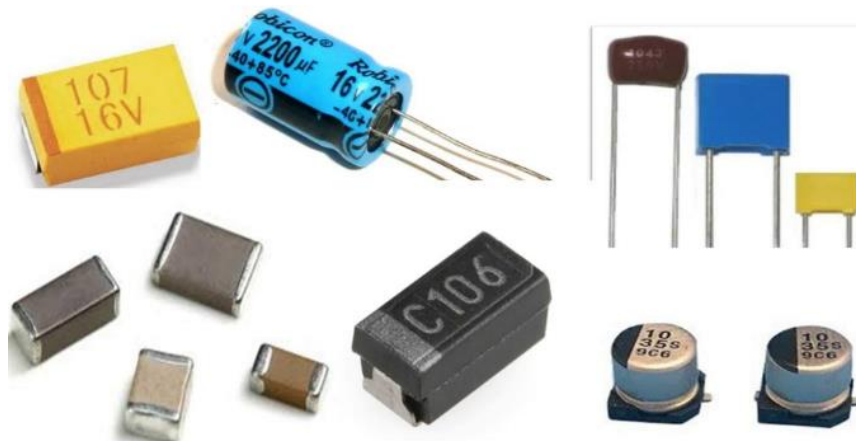


Fixed Capacitor

Polarized Capacitor

Variable Capacitor

Capacitor

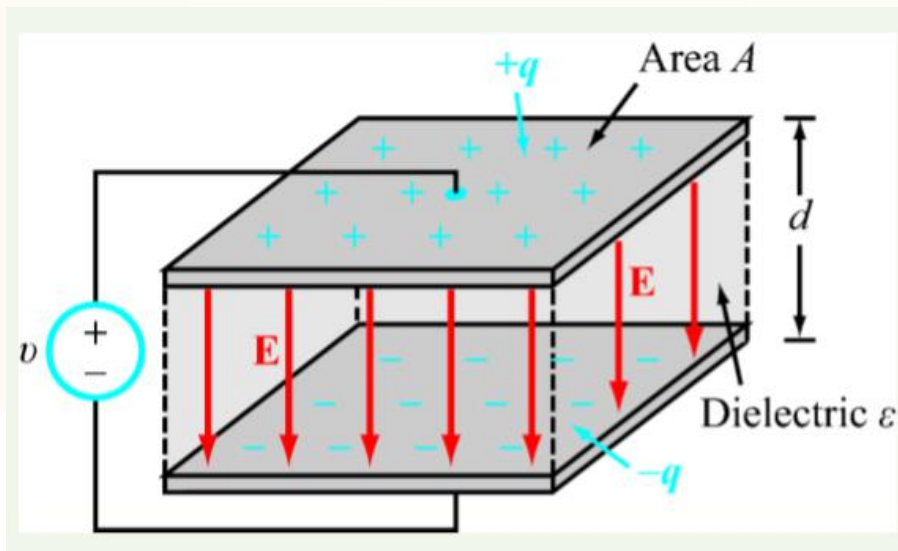

Factors affecting capacitance

- Area of the plate.
- Distance between the plates.
- Type of dielectric material.

$$C = \frac{\epsilon A}{d}$$

Where ϵ represents the permittivity of the material between the plates, A the area of the plates and d their separation distance


C : Capacitance in Farads (F)

d : distance between the conducting plates (m)


ϵ : permittivity (F/m)

A : surface area of plates (m²)

Capacitor

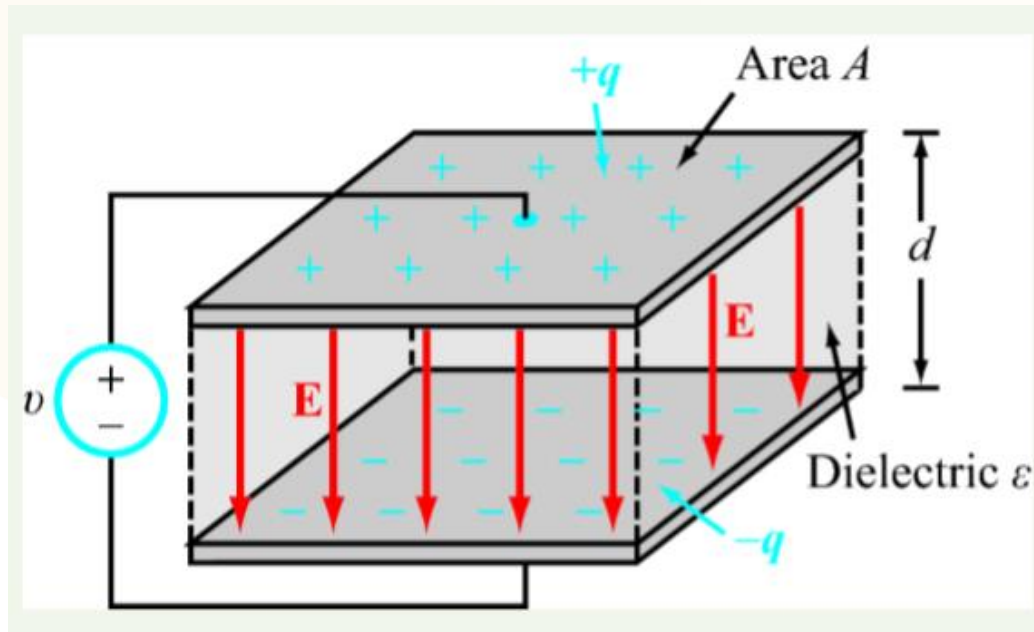

$$C = \epsilon A / d$$

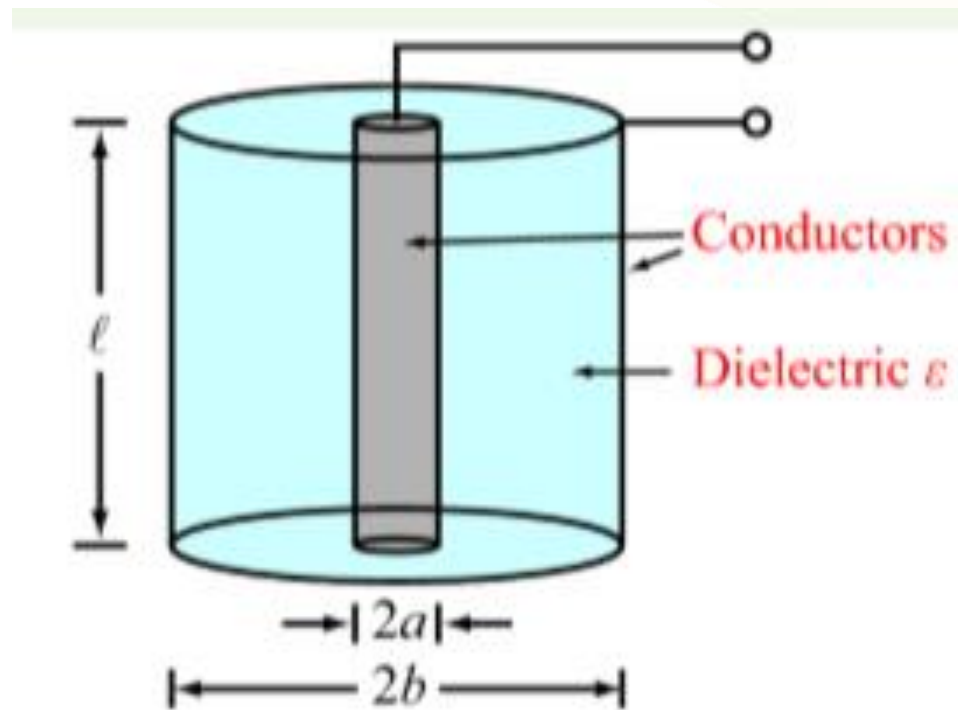

$$C = \frac{2\pi\epsilon\ell}{\ln(b/a)}$$

Capacitor

Dielectric constant ϵ_r

A measure of the effectiveness of a material as an insulator.

$$\epsilon_r = \epsilon / \epsilon_o$$

Where ϵ_r is the dielectric constant of the material, ϵ its permittivity value, and ϵ_o the permittivity of air

Some examples of dielectric constants:

- Paper = 2 - 3
- Mica = 5 - 6
- Titanium = 90 - 170

Capacitor

- The voltage across a capacitor cannot change instantaneously.

$$C = \frac{q}{v}$$

$$i = \frac{dq}{dt} = \frac{dcv}{dt} = c \frac{dv}{dt}$$

- Under a stable dc condition, a capacitor behaves like an open circuit.

For stable DC $\frac{dv}{dt} = 0$

$$i = c \frac{dv}{dt} = 0$$

- To get voltage

$$\int_{t_0}^t \frac{dv}{dt'} dt' = \frac{1}{c} \int_{t_0}^t i dt'$$

$$v(t) = v(t_0) + \frac{1}{c} \int_{t_0}^t i dt'$$

- To get power

$$p(t) = vi = Cv \frac{dv}{dt} \quad \text{Sign of the power?}$$


- To get energy change

$$w(t) = \int_{t_0}^t p dt' = C \int_{t_0}^t \left(v \frac{dv}{dt'} \right) dt' = C \int_{t_0}^t \left[\frac{d}{dt'} \left(\frac{1}{2} v^2 \right) \right] dt' = \frac{1}{2} C (v(t))^2 - \frac{1}{2} C (v(t_0))^2$$

Sign of the energy change?

- To get energy in a capacitor

$$E(t) = \frac{1}{2} C (v(t))^2$$

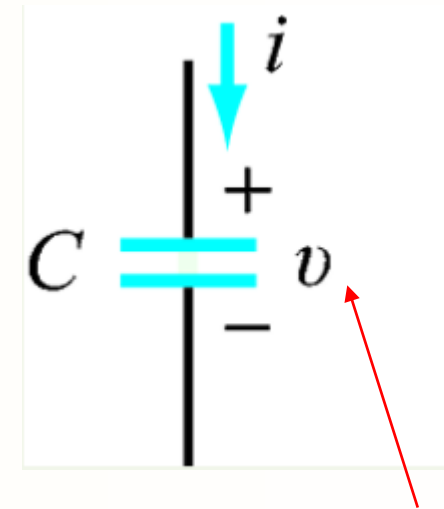

v is the voltage across the capacitor


The direction of i is entering the positive terminal of the capacitor.

Capacitor

$$i = \frac{dq}{dt} = \frac{dcv}{dt} = c \frac{dv}{dt}$$

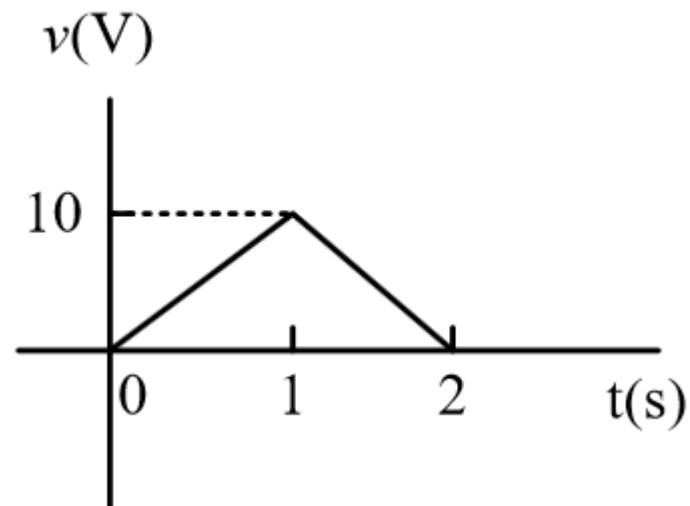E. g.

Consider the following voltage waveform across a capacitor $C = 1\text{mF}$, Find the current through the capacitor.




Capacitor


- Under a stable dc condition, a capacitor behaves like an open circuit.

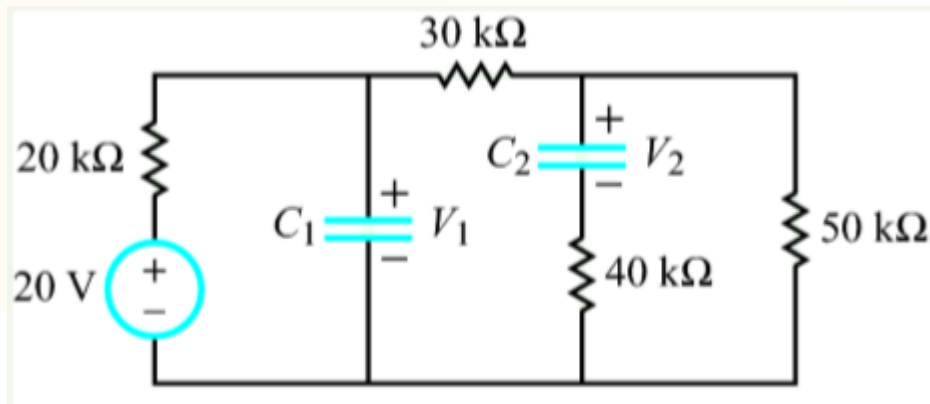E. g.

Determine voltages across the capacitors in the circuit. Assume that the circuit has been in its present condition for a long time.



Original circuit

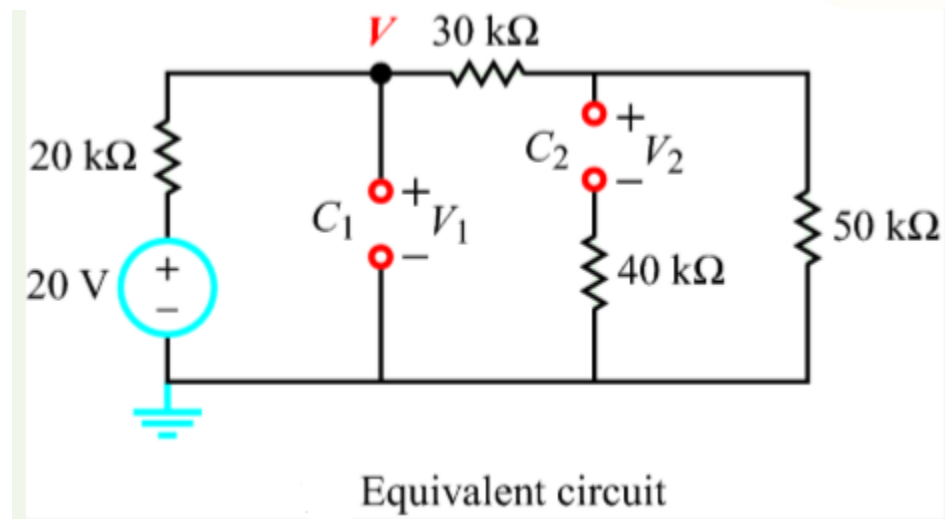


Equivalent circuit

Capacitor

➤ Capacitors in series

$$V(t) = V_1 + V_2 + V_3$$

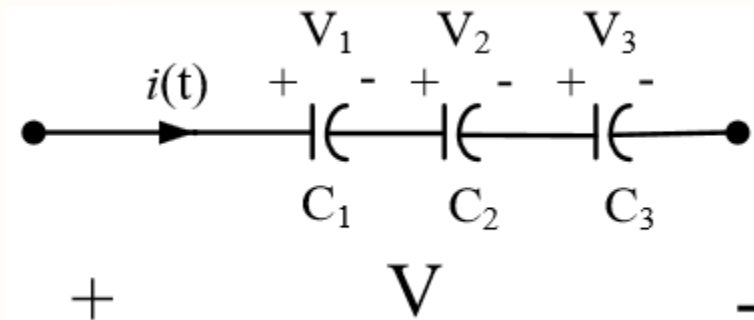

$$\frac{1}{C_{eq}} \int_0^t i(t) dt = \frac{1}{C_1} \int_0^t i(t) dt + \frac{1}{C_2} \int_0^t i(t) dt + \frac{1}{C_3} \int_0^t i(t) dt$$

$$\rightarrow \frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

The equivalence relationship for capacitors connected in series is similar in form to the relationship for resistors connected in parallel.

$$q_1 = q_2 = q_3 = q$$

$$V_1 = \frac{q_1}{C_1} \quad V_2 = \frac{q_2}{C_2} \quad V_3 = \frac{q_3}{C_3} \quad V = \frac{q}{C_{eq}}$$


$$V_x = \frac{C_{eq}}{C_x} V$$

The largest-value capacitor in a series connection will have the smallest voltage across it. The smallest-value capacitor will have the largest voltage across it.

Capacitor

➤ Capacitors in parallel:

$$i(t) = i_1(t) + i_2(t) + i_3(t)$$

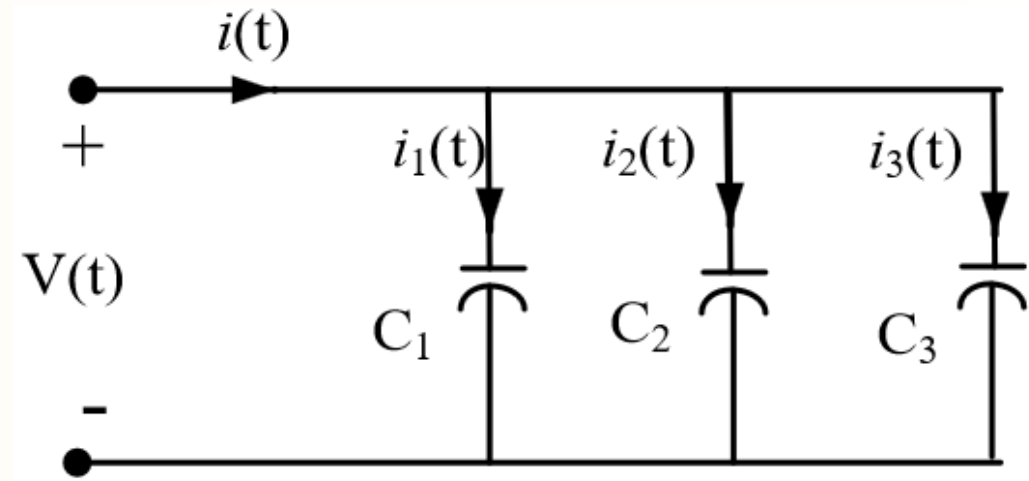

$$C_{eq} \frac{dV(t)}{dt} = C_1 \frac{dV(t)}{dt} + C_2 \frac{dV(t)}{dt} + C_3 \frac{dV(t)}{dt}$$

$$\rightarrow C_{eq} = C_1 + C_2 + C_3$$

The equivalence relationship for capacitors connected in parallel is similar in form to the relationship for resistors connected in series.

Capacitor

E. g.

Find the equivalent circuit for the following circuit.

➤ Capacitors in series

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

➤ Capacitors in parallel:

$$C_{eq} = C_1 + C_2 + C_3$$

