

Signals and Circuits

ENGR 35500

Mesh Analysis

Chapter 3: 3-2 (Mesh-Current Method) pp. 100-105; 3-5 (Thevenin and Norton Equivalent circuits) pp. 113-119;


Ulaby, Fawwaz T., and Maharbiz, Michael M., *Circuits*, 2nd Edition, National Technology and Science Press, 2013.



Mesh Analysis

- Sometimes also called Loop analysis;
- Based on KVL;
- Based on distinguishing types of loops.

Mesh Analysis

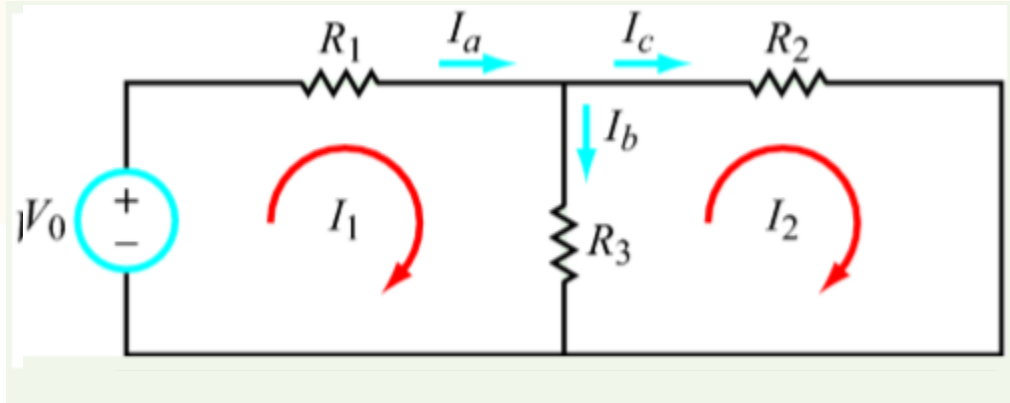

Step 1: Identify all the meshes and assign each of them an unknown mesh current (Usually clockwise).

Step 2: KVL+Ohm's law

Step 3: Solve the simultaneous equations to get the mesh current.

Step 4: Transfer mesh current to actual current

$$-V_0 + I_1 R_1 + (I_1 - I_2) R_3 = 0 \quad (\text{Mesh 1})$$

$$(I_2 - I_1) R_3 + I_2 R_2 = 0 \quad (\text{Mesh 2})$$


$$I_a = I_1$$

$$I_c = I_2$$

$$I_b = I_1 - I_2$$

Mesh Analysis

Practice

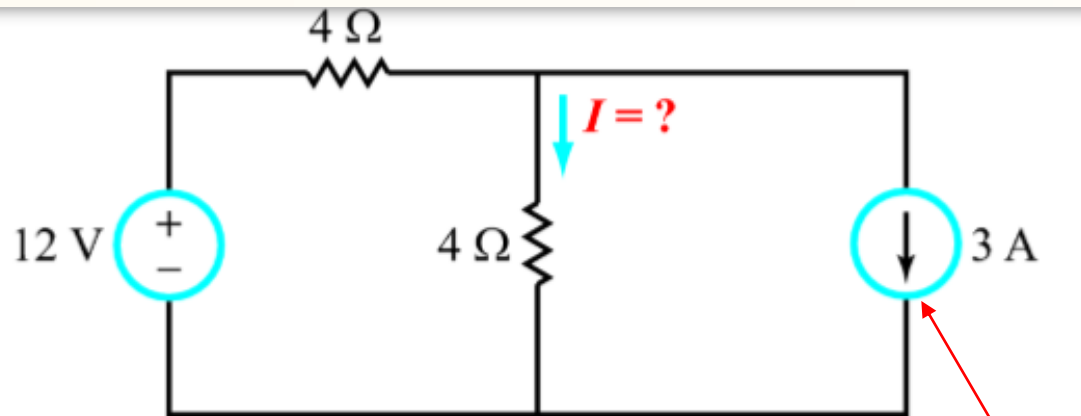

Step 1: Identify all the meshes and assign each of them an unknown mesh current (Usually clockwise).


Step 2: KVL+Ohm's law

Step 3: Solve the simultaneous equations to get the mesh current.

Step 4: Transfer mesh current to actual current

Note: sometimes some mesh current can be expressed directly by some current source

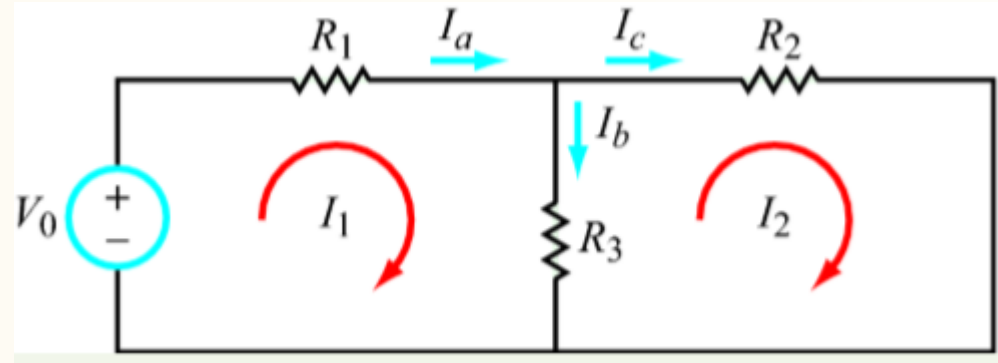Original Method VS Nodal Method VS Mesh Method



Original method (KL)

1. Labels
2. Distinguish loops
3. Create current equations using KVL+Ohm's law
4. KCL
5. Simultaneous solution of equations

Nodal Method

0. Supernodes and quasi-super node

1. Identify extraordinary nodes, label $(n_{ex} - 1)$ extraordinary nodes and one ground node.
2. At $(n_{ex} - 1)$ extraordinary nodes, label current as leaving the nodes.
3. At each $(n_{ex} - 1)$ extraordinary node, apply KCL
4. Try to substitute the currents with the terms of voltages
5. Simultaneous solution of equations


Mesh method

0. ?

1. Identify all the meshes and assign each of them an unknown mesh current (Usually clockwise).
2. KVL+Ohm's law
3. Solve the simultaneous equations to get the mesh current.
4. Transfer mesh current to actual current

Mesh analysis

Supermesh

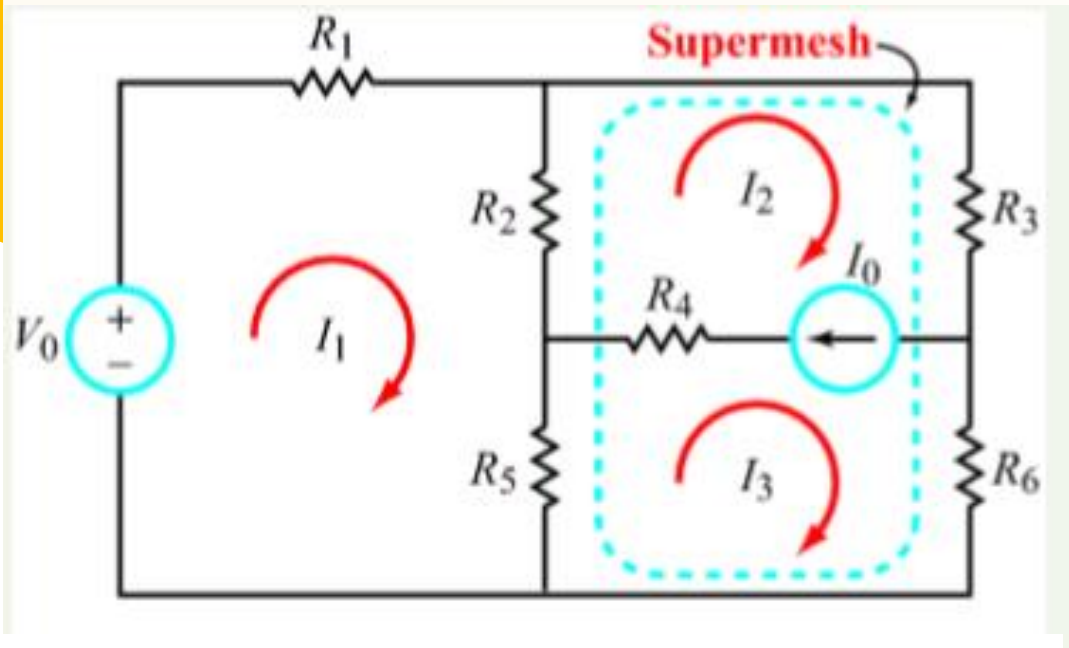

Two adjoining meshes that share a current source constitute a supermesh. The current source may be of the independent or dependent type, and it may include a resistor in series with it.

Mesh method

0. supermesh, mesh current directly from current

1. Identify all the meshes and assign each of them an unknown mesh current (Usually clockwise).
2. KVL+Ohm's law
3. Solve the simultaneous equations to get the mesh current.
4. Transfer mesh current to actual current


$$-V_0 + R_1 I_1 + (I_1 - I_2) R_2 + (I_1 - I_3) R_5 = 0 \quad (\text{Mesh 1})$$

$$(I_3 - I_1) R_5 + (I_2 - I_1) R_2 + I_2 R_3 + I_3 R_6 = 0 \quad (\text{Super Mesh})$$


$$I_0 = I_2 - I_3 \quad (\text{auxiliary eq.})$$

Mesh analysis

Determine V_x

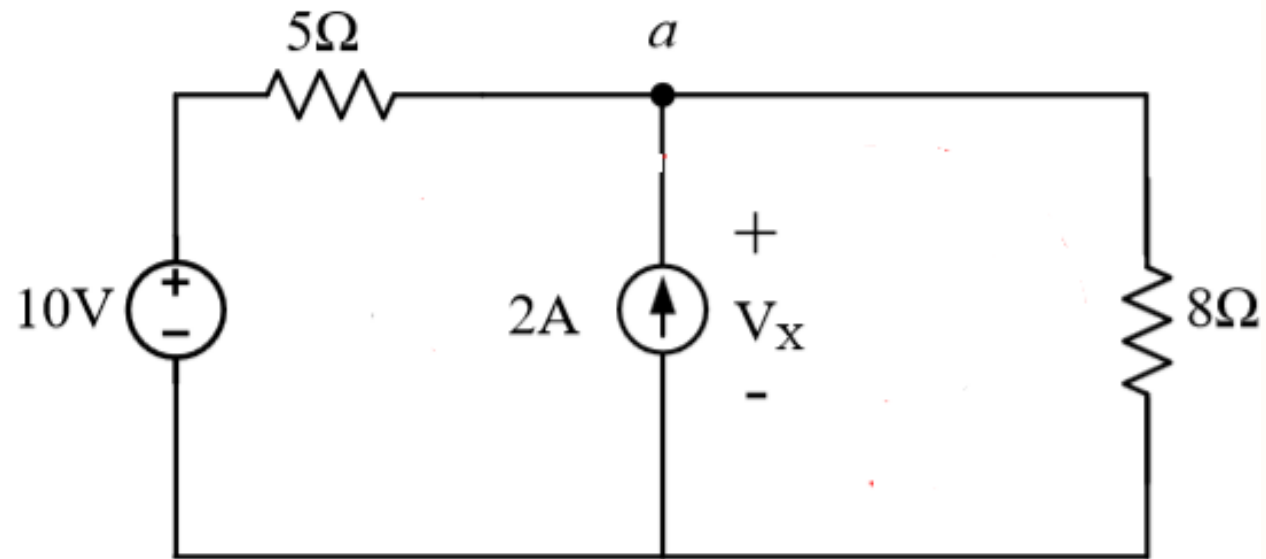

Thevenin's and Norton's Theorems


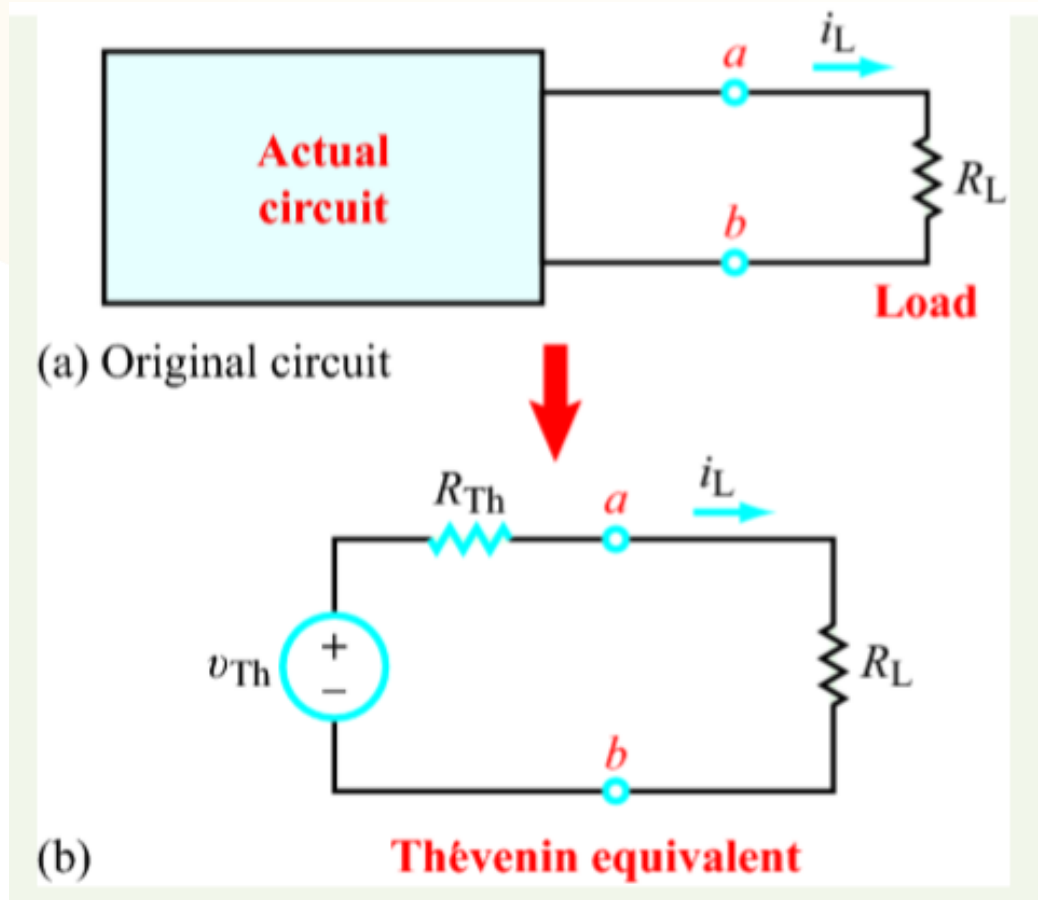


Thevenin's Theorem

A **linear** circuit can be represented at its output terminals by an equivalent circuit consisting of a series combination of a voltage source V_{Th} and a resistor R_{Th} .

Thevenin's and Norton's Theorems

Open-circuit/short-circuit method

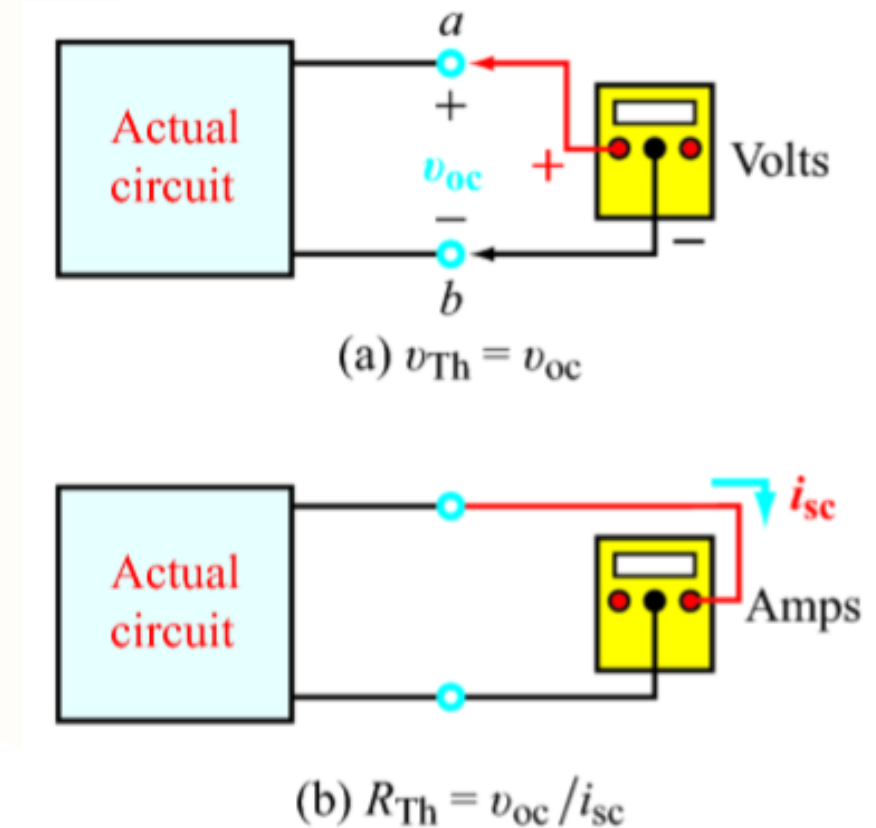
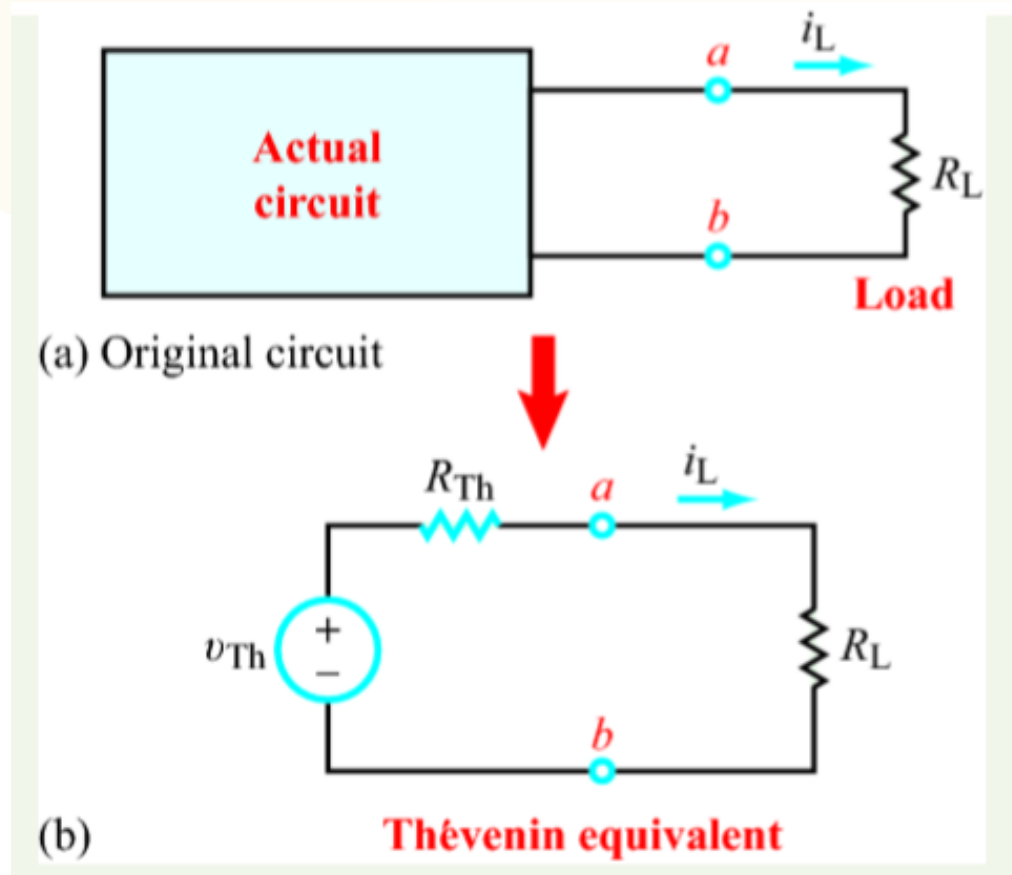


The Thevenin voltage V_{Th} is obtained by removing the load R_L (replacing it with an open circuit), and then measuring or computing the open-circuit voltage at the same terminals. The short-circuit current i_{sc} is obtained by replacing the load with a short circuit and then measuring or computing the short-circuit current flowing through it.


Thevenin's and Norton's Theorems

Open-circuit/short-circuit method


Find R_L could make I_L as 0.5 A

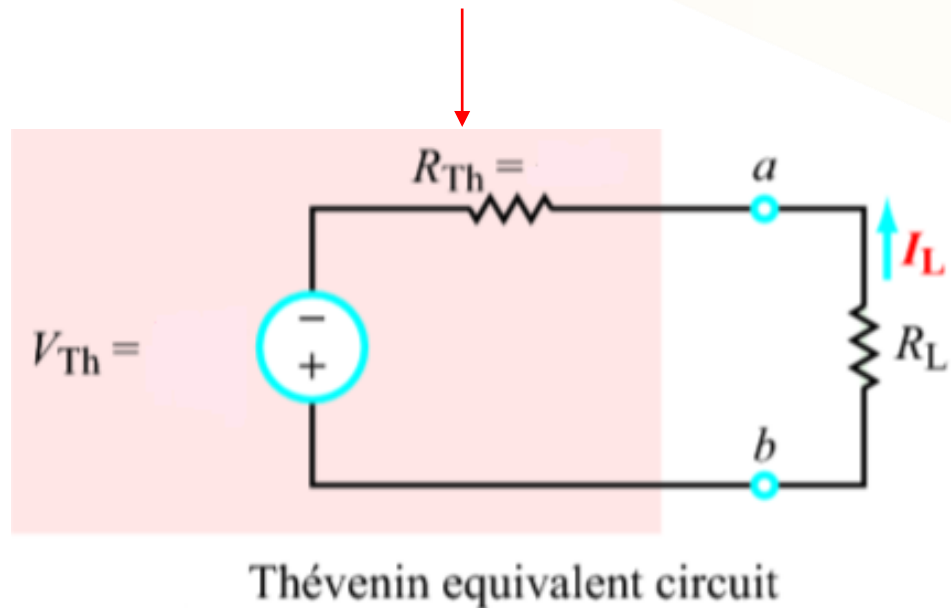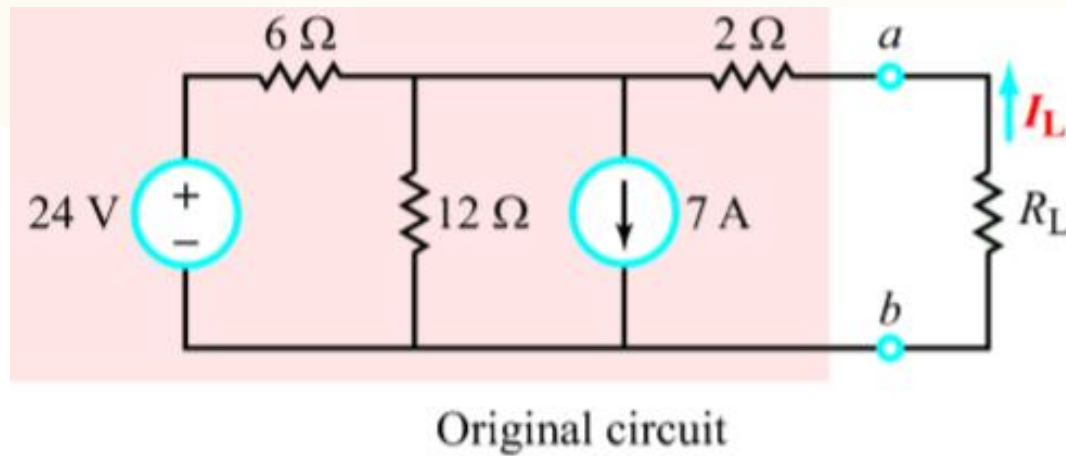

Step 1:

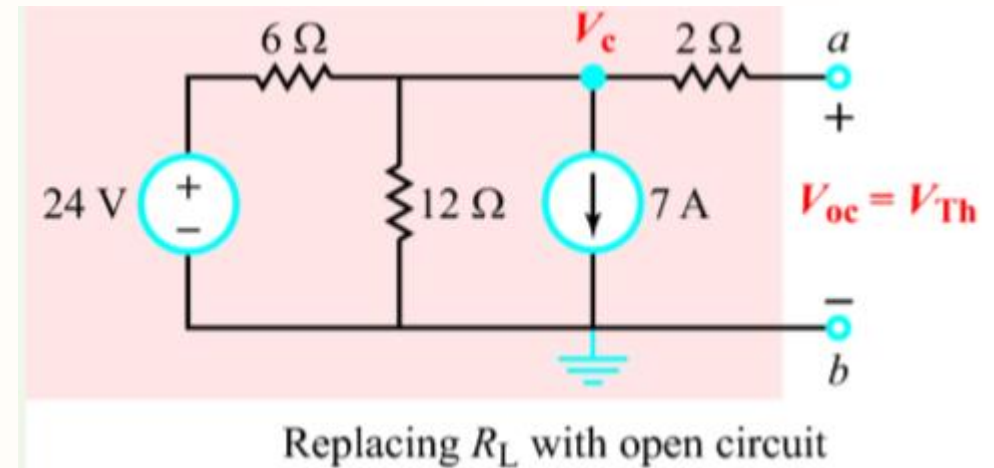

Step 2:

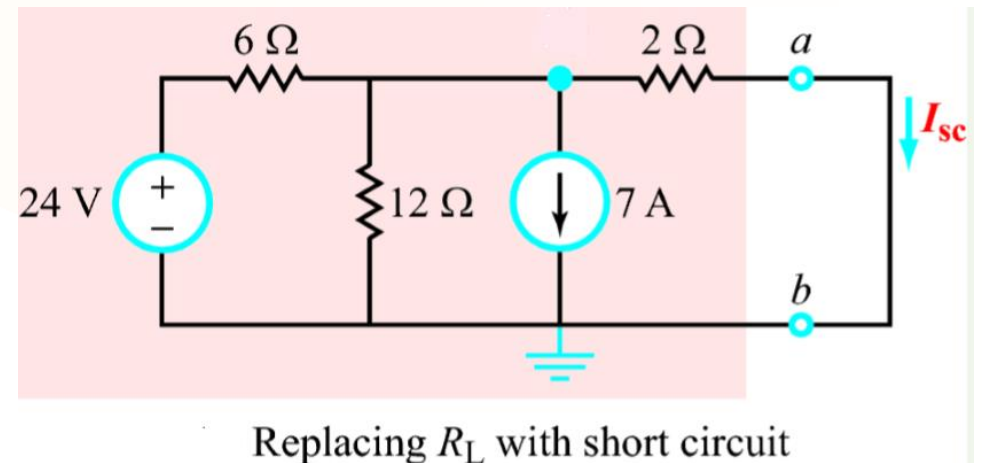

$$R_{Th} = V_{Th} / I_{sc}$$

Step 3:

$$I_L = V_{Th} / (R_L + R_{Th})$$


Note: This method is applicable to any circuit with at least one independent source, regardless of whether or not it contains dependent sources.

Thevenin's and Norton's Theorems

Equivalent-resistance method for R_{Th}



E.g.

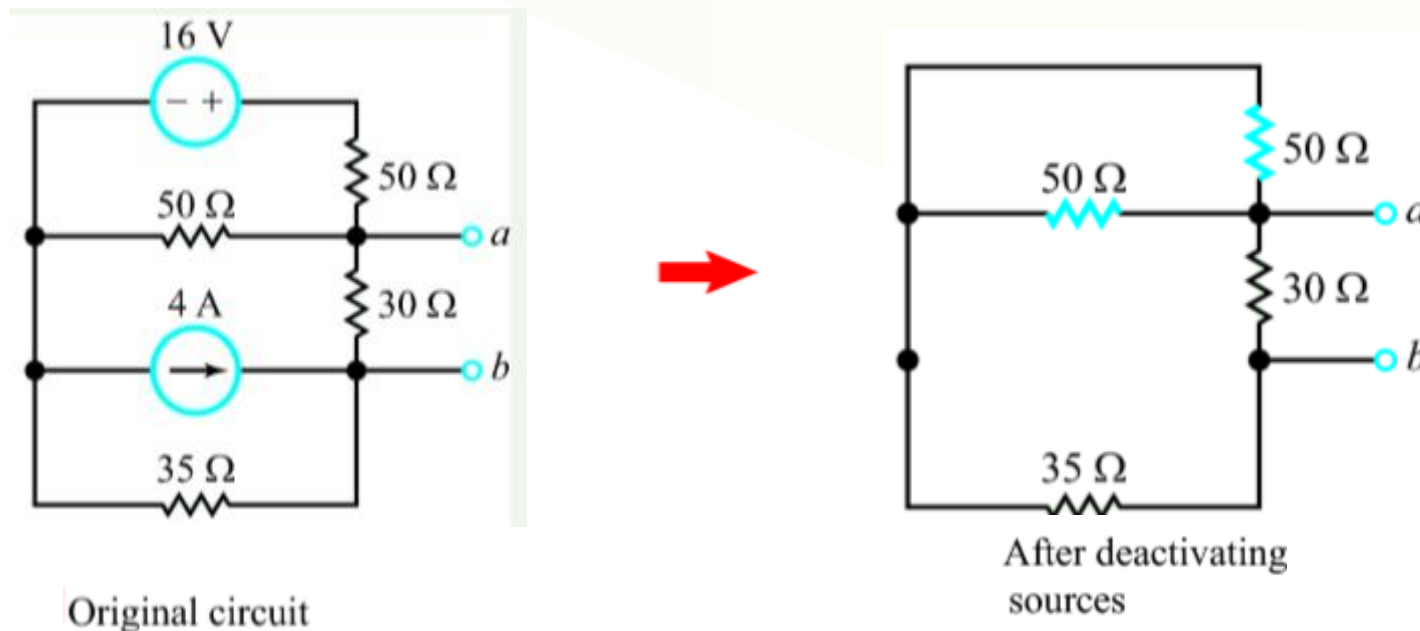


1. Replace voltage sources with short circuits
2. Replace current sources with open circuits

Note: This method is not applicable to circuit with that contain dependent sources.

Thevenin's and Norton's Theorems


External-source method for R_{Th}

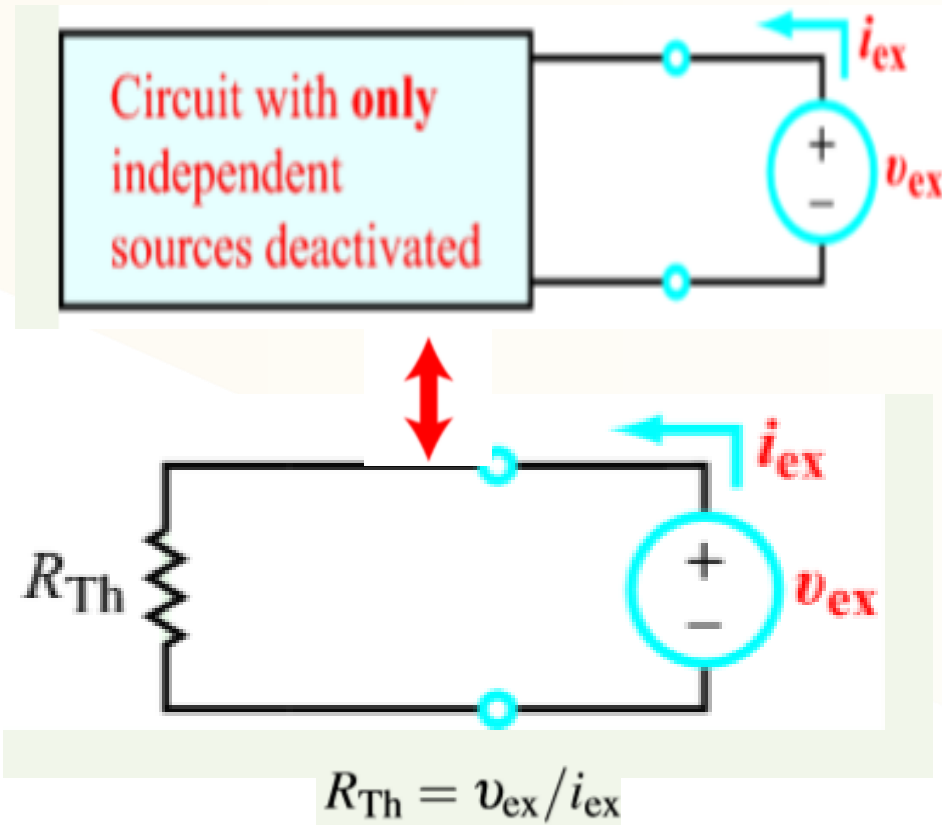

1. Replace independent voltage sources with short circuits
2. Replace independent current sources with open circuits
3. Left the dependent sources alone
4. Add an external voltage source v_{ex} , and calculate v_{ex} and i_{ex}

Note: This method is applicable to circuit with that contain dependent sources.

E. g.

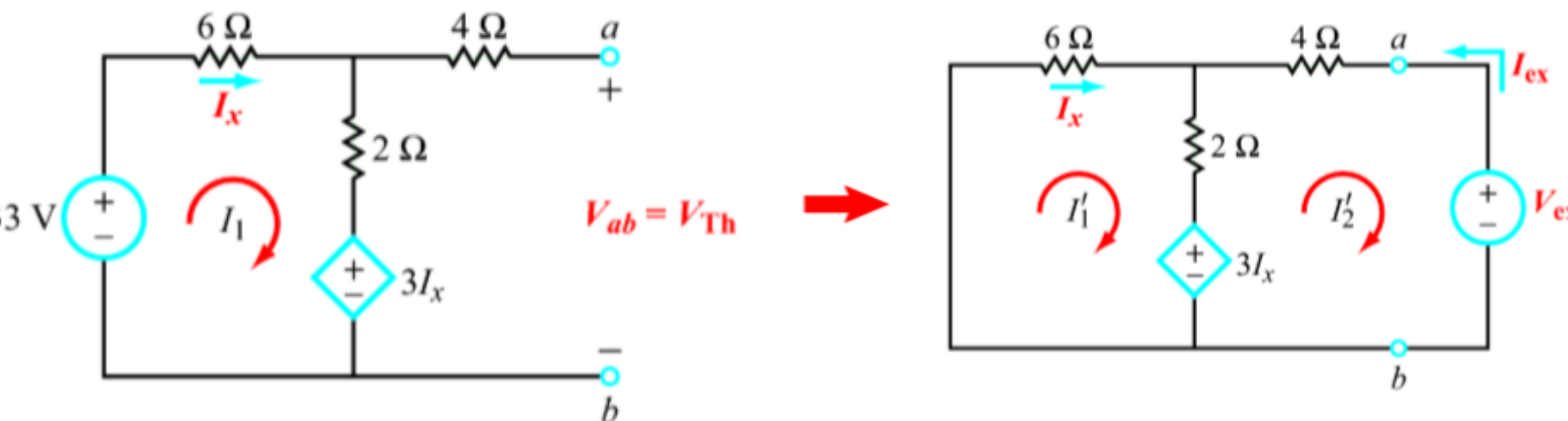


calculate v_{ex} and i_{ex}

$$R_{Th} = v_{ex} / i_{ex}$$

Thevenin and Norton Equivalency

Thévenin and Norton Equivalency

Thévenin
equivalent
circuit

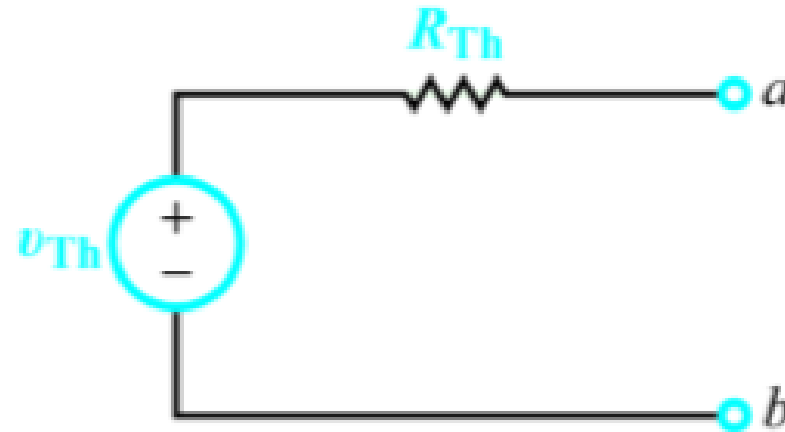

Norton equivalent
circuit

$$i_N = v_{Th} / R_{Th}$$
$$R_N = R_{Th}$$

