

# Signals and Circuits

**ENGR 35500**

Operational Amplifier



# Problems can be solved by Op-amp

- **Signals are too small**
- **Signals are too noisy**
- **Need to improve the compatibility of system (impedance)**
- **Need some special operations**

Summers

Inverters

Comparator

Differentiators

Integrators

# What is an Operational Amplifier?

An operational amplifier is a DC-coupled high gain electronic voltage amplifier with a differential input and usually, a single-end output. (Wikipedia)

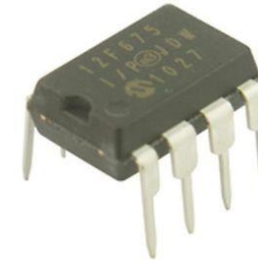
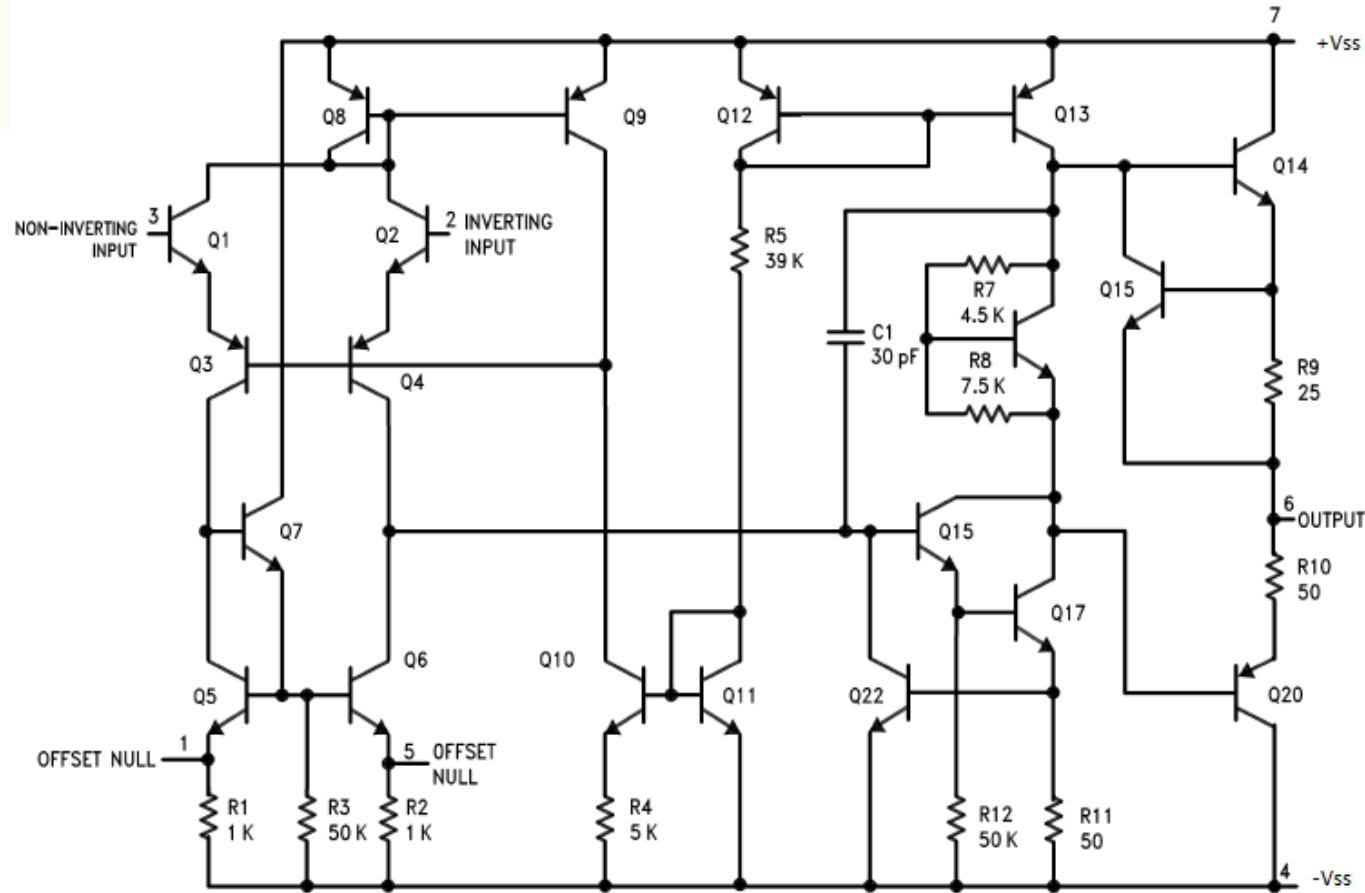


Fig. 1. Op-amp chip inside schematic representation

# What is an Operational Amplifier?

An operational amplifier is a DC-coupled high gain electronic voltage amplifier with a differential input and usually, a single-end output. (Wikipedia)

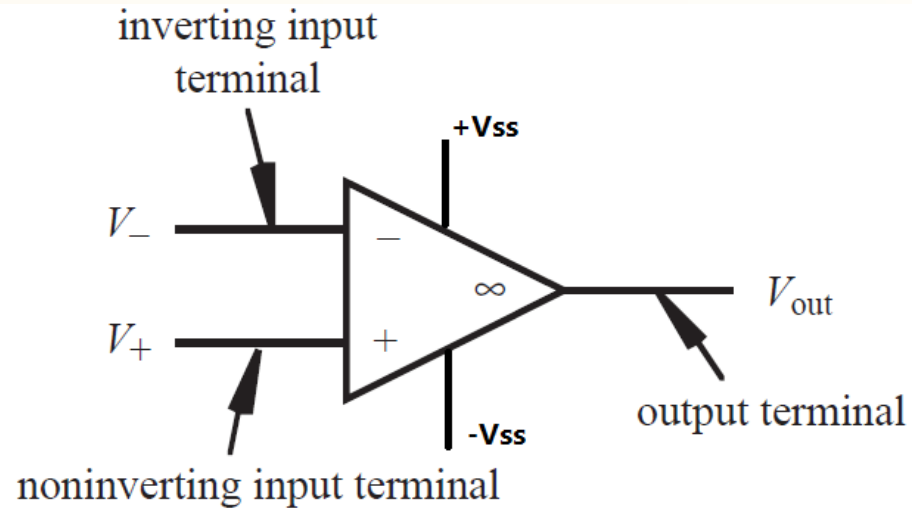
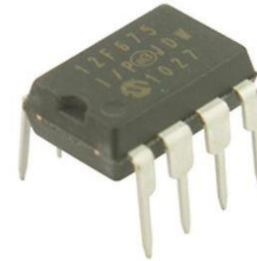


Fig.2. Op-amp schematic representation

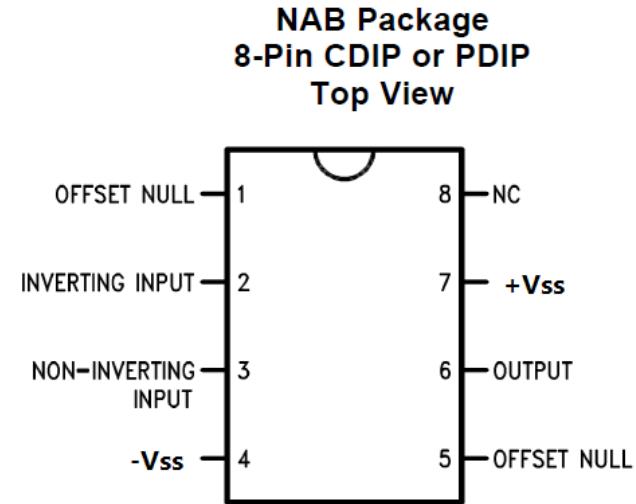


Fig.3. Op-amp schematic representation

# What is an Operational Amplifier?

An operational amplifier is a DC-coupled high gain electronic voltage amplifier with a differential input and usually, a single-end output. (Wikipedia)

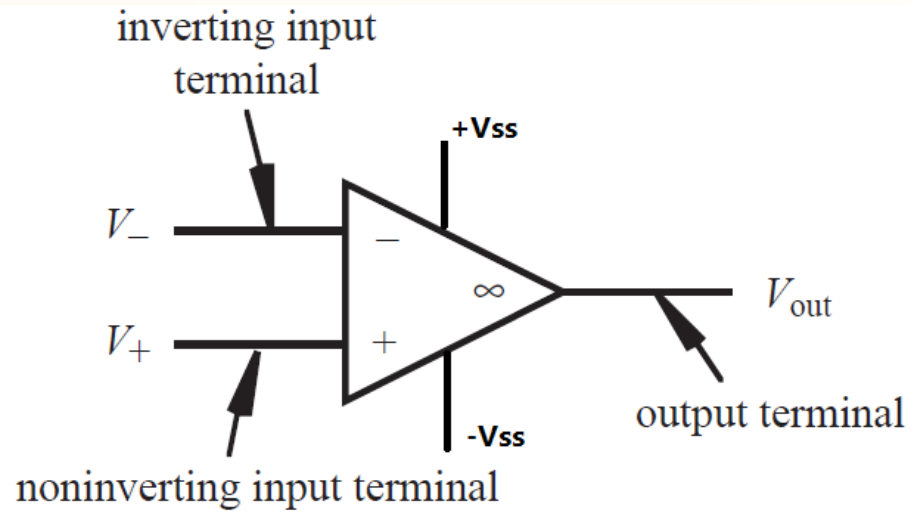


Fig.2. Op-amp schematic representation

$$V_{out} = (V_+ - V_-)A_v$$

$$A_v \rightarrow \text{infinity (large number)}$$

$$V_{out} \in (-V_{ss}, +V_{ss})$$

$$V_{out} = \begin{cases} +V_{ss} & V_+ > V_- \\ -V_{ss} & V_- > V_+ \end{cases}$$

# What is an Operational Amplifier?

An operational amplifier is a DC-coupled high gain electronic voltage amplifier with a differential input and usually, a single-end output. (Wikipedia)

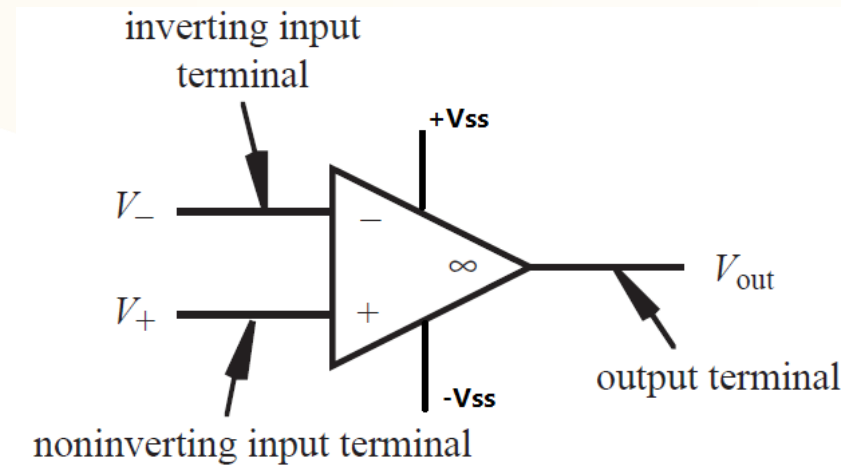


Fig.2. Op-amp schematic representation (open-loop)

$$V_{out} = (V_+ - V_-)A_v$$

$A_v \rightarrow \text{infinity (large number)}$

$$V_{out} = \begin{cases} +V_{ss} & V_+ > V_- \\ -V_{ss} & V_- > V_+ \end{cases}$$

$V_S$

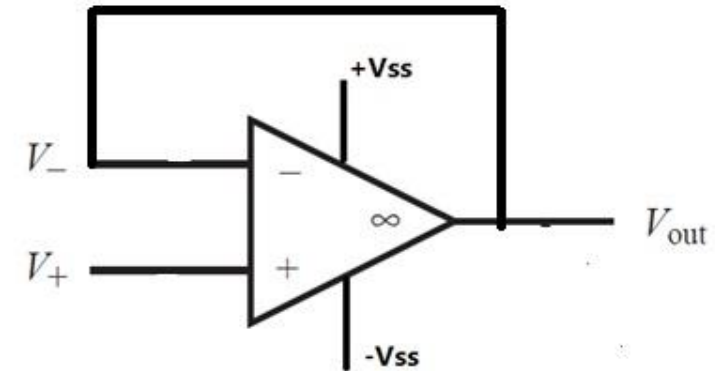


Fig.3. Op-amp schematic representation (closed-loop)

$$V_{out} = V_- = (V_+ - V_-)A_v$$

$A_v \rightarrow \text{infinity (large number)}$

$$V_{out} \in (-V_{ss}, +V_{ss})$$

$(V_+ - V_-) \rightarrow 0 \text{ (very small number)}$


**Golden Rule 1:**

$$V_+ = V_-$$
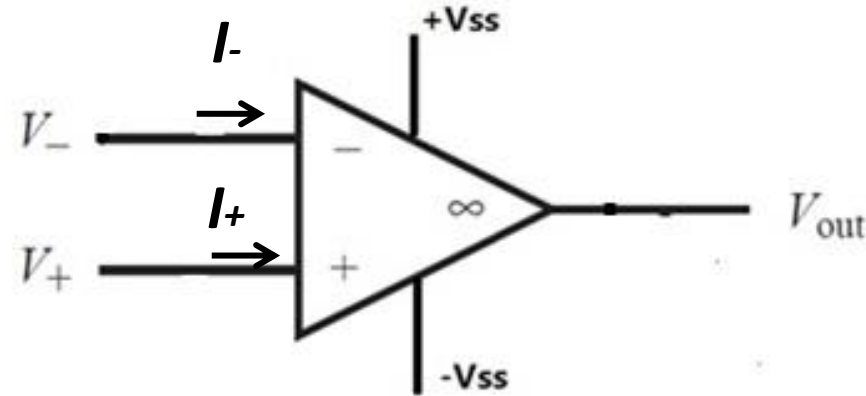
# What is an Operational Amplifier?

One more characteristic about Op-amp:

It has infinite impedance/resistance at both inputs



Golden Rule 2:

$$I_+ = I_- = 0$$



# What is an Operational Amplifier? (sum up)

An operational amplifier is a DC-coupled high gain electronic voltage amplifier with a differential input and usually, a single-end output. (Wikipedia)

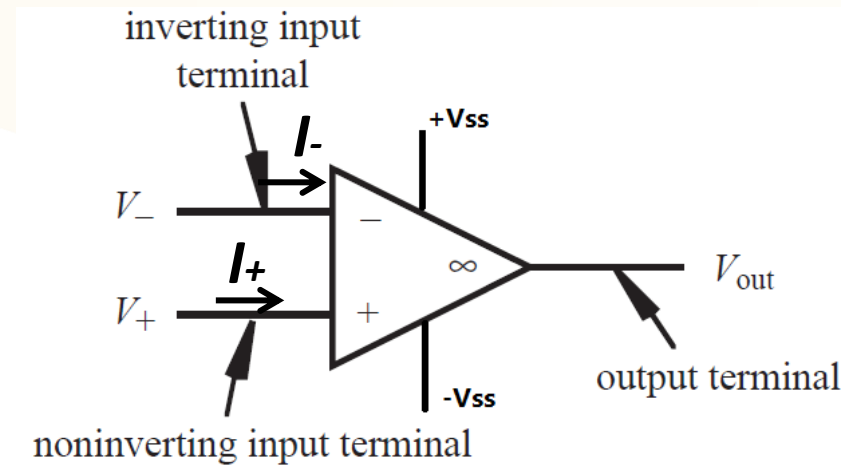


Fig.2. Op-amp schematic representation (open-loop)

$$V_{out} = \begin{cases} +V_{ss} & V_+ > V_- \\ -V_{ss} & V_- > V_+ \end{cases}$$

Golden Rule 2:

$$I_+ = I_- = 0$$

$V_S$

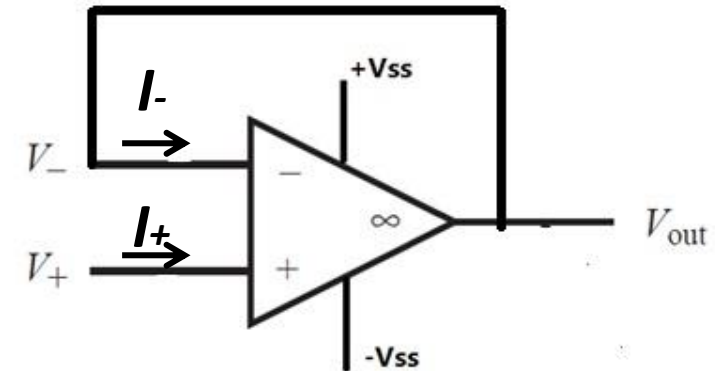


Fig.3. Op-amp schematic representation (closed-loop)

Golden Rule 1:

$$V_+ = V_-$$

Golden Rule 2:

$$I_+ = I_- = 0$$



# Op-amp application example

E. g.





After connecting, we hope  $V_3 = 0.25V_1$




**Really?**

# Op-amp application example


E. g.

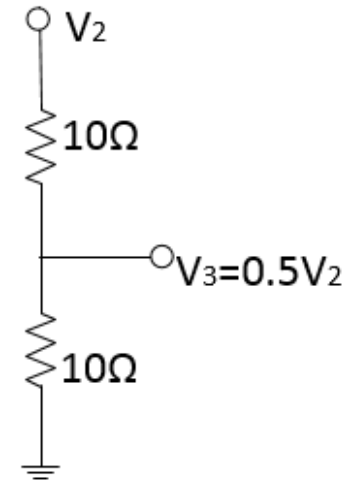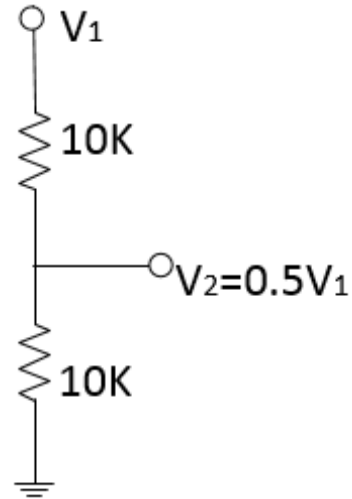


If connected

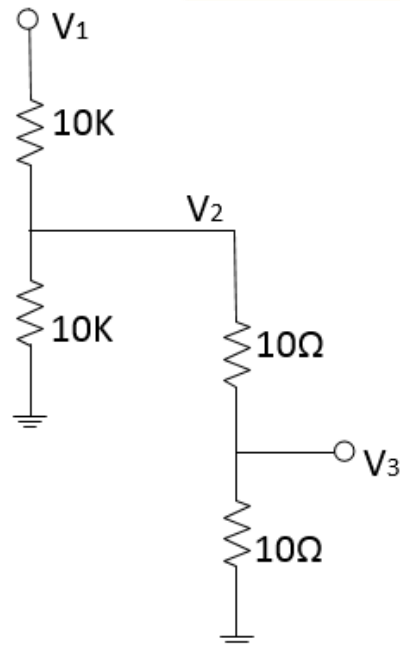

=

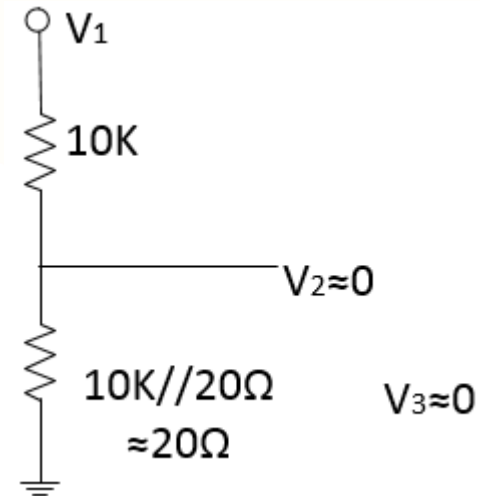

# Solution

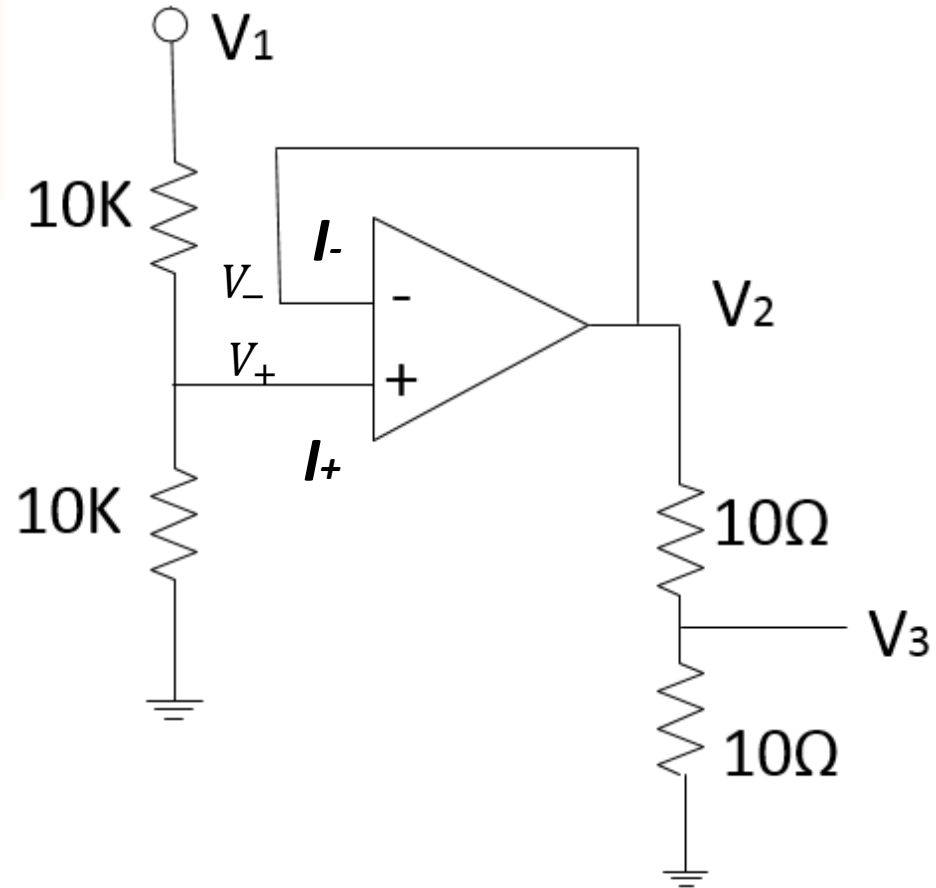


Golden rules:

$$V_+ = V_-$$

$$I_+ = I_- = 0$$

# Op-Amp Application


## 1. Buffer or follower

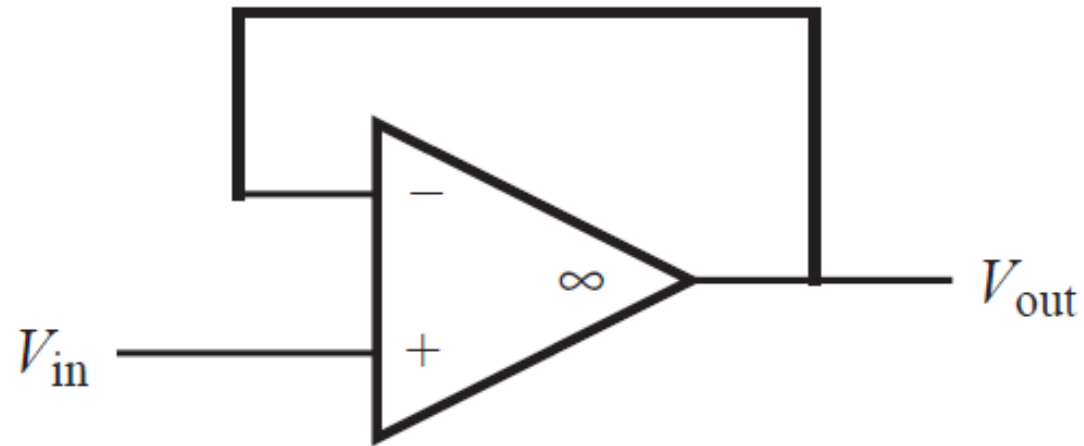

$$V_{in} = V_{out}$$

# Op-Amp Application

## 2. Non-inverting op-amp

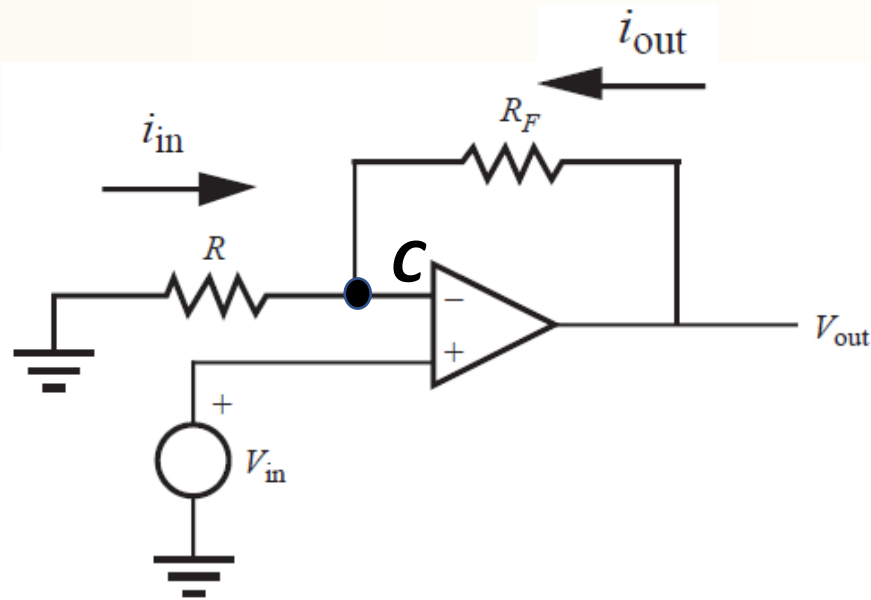

Golden rules:

$$V_+ = V_-$$

$$I_+ = I_- = 0$$

Ohm's law

Kirchhoff's current law (KCL)

Step 1: Ohm's law to  $R$  and Golden Rule 1

$$i_{in} = \frac{-V_{in}}{R} \quad (4.1)$$

Step 2: Ohm's law to  $R_F$  Golden Rule 1

$$i_{out} = \frac{V_{out} - V_{in}}{R_F} \quad (4.2)$$

Step 3: Rewrite Eq. (4.2)

$$V_{out} = i_{out} R_F + V_{in} \quad (4.3)$$

Step 4: Apply Kirchhoff's current law to node C and Gold Rule 2

$$i_{in} = -i_{out} \quad (4.4)$$

Step 5: Combine Eq. (4.1) with Eq. (4.4)


$$V_{in} = i_{out} R \quad (4.5)$$

Step 6: Use Eq. (4.3) and Eq. (4.5)

$$\frac{V_{out}}{V_{in}} = \frac{i_{out} R_F + V_{in}}{V_{in}} = \frac{i_{out} R_F + i_{out} R}{i_{out} R} = 1 + \frac{R_F}{R} \quad (4.6)$$


# Op-Amp Application

## 2. Non-inverting op-amp

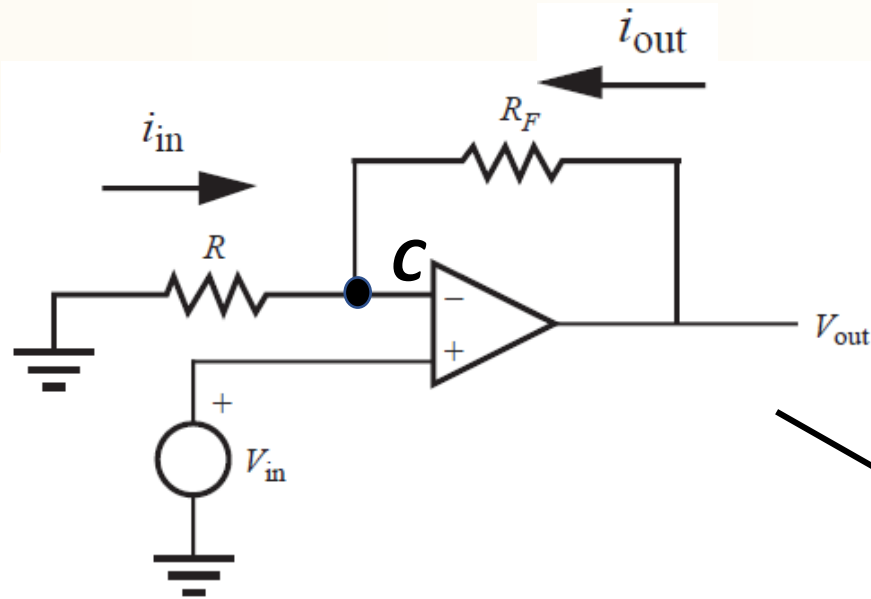


$$\frac{V_{out}}{V_{in}} = \frac{i_{out} R_F + V_{in}}{V_{in}} = \frac{i_{out} R_F + i_{out} R}{i_{out} R} = 1 + \frac{R_F}{R}$$

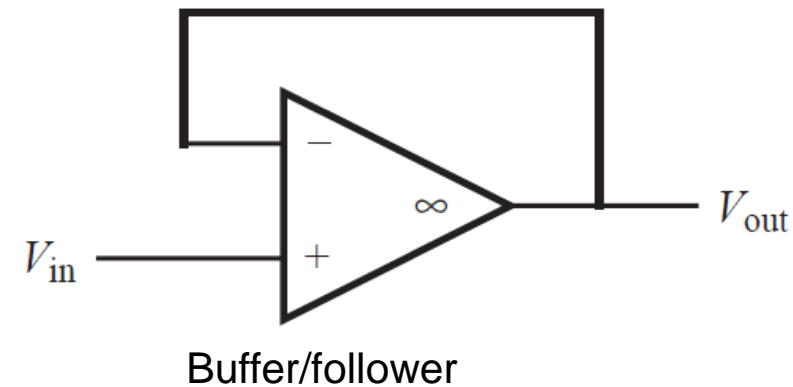What will happen if  $R_F=0$ , and  $R$  is very large?



# Op-Amp Application

**Note:**

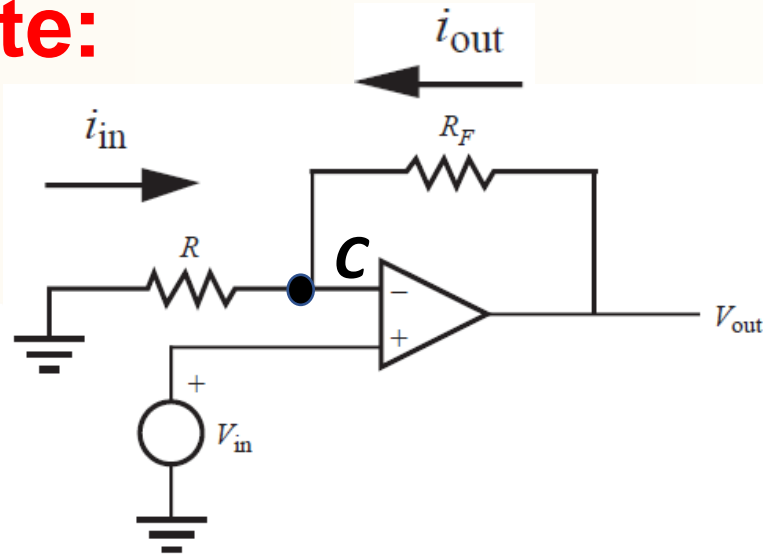

Step 1: Ohm's law to  $R$  and Golden Rule 1

$$i_{in} = \frac{-V_{in}}{R} \quad (4.1)$$

Step 2: Ohm's law to  $R_F$  Golden Rule 1

$$i_{out} = \frac{V_{out} - V_{in}}{R_F} \quad (4.2)$$

Step 3: Rewrite Eq. (4.2)

$$V_{out} = i_{out} R_F + V_{in} \quad (4.3)$$

Step 4: Apply Kirchhoff's current law to node C and Golden Rule 2

$$i_{in} = -i_{out} \quad (4.4)$$


Step 5: Combine Eq. (4.1) with Eq. (4.4)

$$V_{in} = i_{out} R \quad (4.5)$$

Step 6: Use Eq. (4.3) and Eq. (4.5)

$$\frac{V_{out}}{V_{in}} = \frac{i_{out} R_F + V_{in}}{V_{in}} = \frac{i_{out} R_F + i_{out} R}{i_{out} R} = 1 + \frac{R_F}{R} \quad (4.6)$$


## Practice

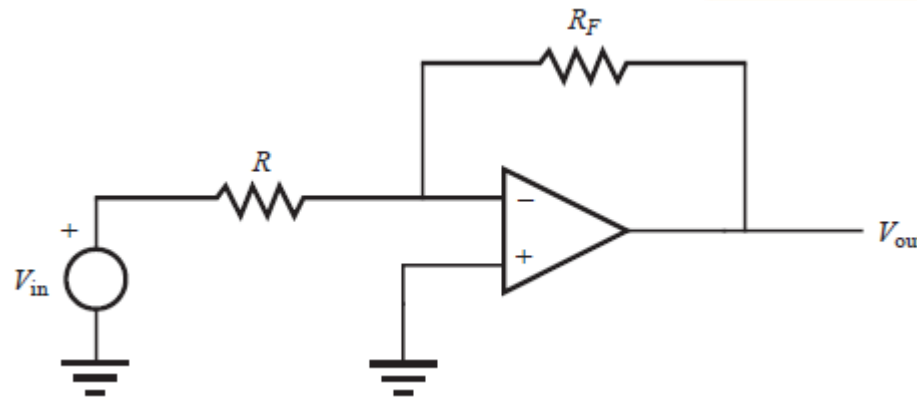



# Op-Amp Application

## 3. Inverting op-amp

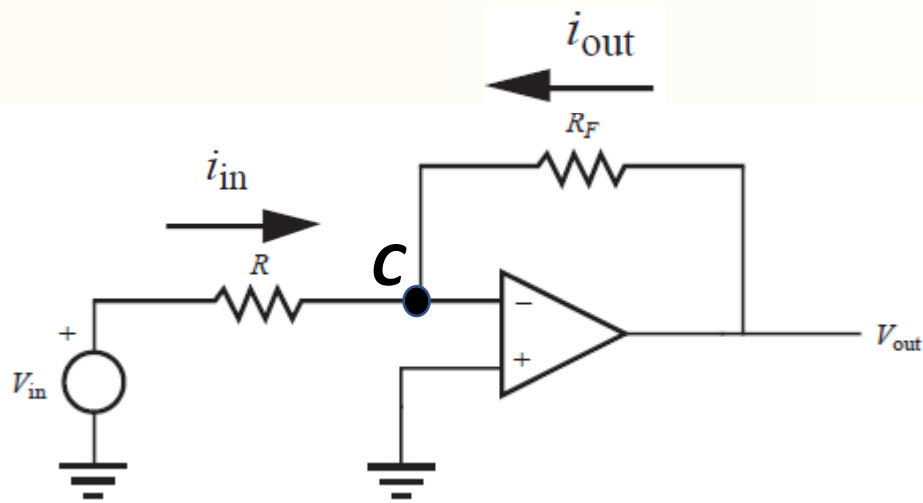

Golden rules:

$$V_+ = V_-$$
$$I_+ = I_- = 0$$

Ohm's law

Kirchhoff's current law (KCL)

Step 1: Apply Kirchhoff's current law to node C and with Golden Rule 2

$$i_{in} = -i_{out} \quad (4.7)$$

Step 2: Golden Rule 1

$$V_C = 0 \quad (4.8)$$

Step 3: Ohm's law to R

$$V_{in} - V_C = i_{in}R \quad (4.9)$$

Step 4: Ohm's law to  $R_F$  and combine Eq.(4.7)

$$V_{out} = -i_{in}R_F \quad (4.10)$$


Step 5: Combine the last two equations

$$\frac{V_{out}}{V_{in}} = -\frac{R_F}{R} \quad (4.11)$$

# Op-Amp Application

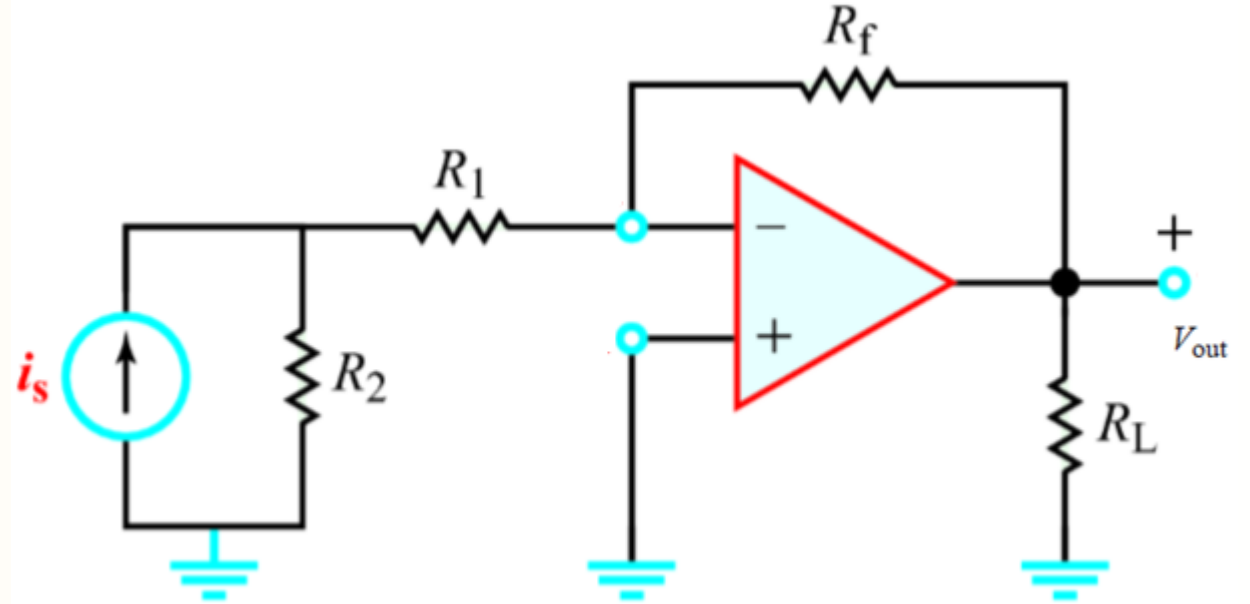
## Practice

Given  $i_s = 1\text{mA}$ ,  $R_1 = 1\text{k}\Omega$ ,  $R_2 = 2\text{k}\Omega$ ,  $R_f = 30\text{k}\Omega$ ,  $R_L = 10\text{k}\Omega$ , determine  $V_{out}$



# Op-Amp Application(open-loop)

## 4. Comparator

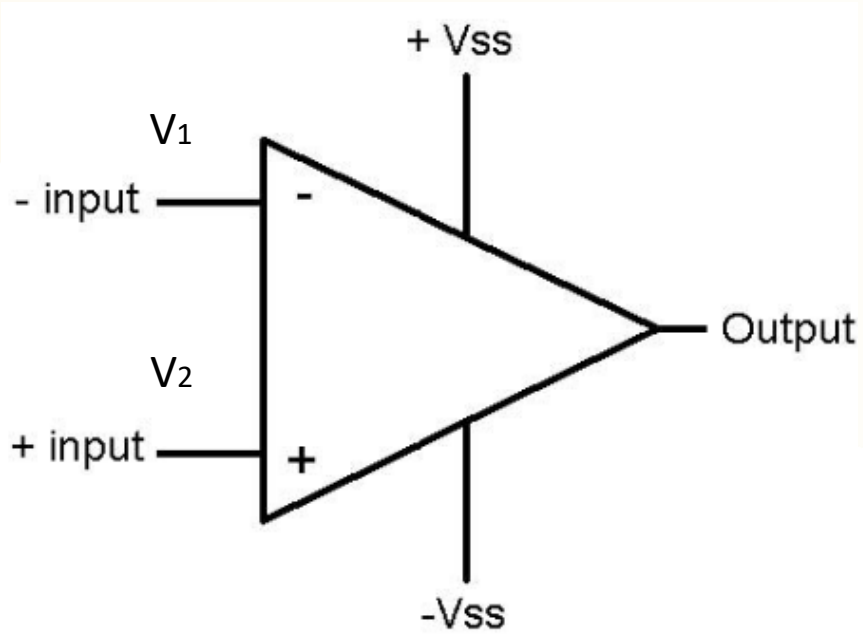

$$V_{\text{out}} = \begin{cases} +V_{SS} \\ -V_{SS} \end{cases}$$



$$V_2 > V_1$$

$$V_1 > V_2$$

# Op-Amp Application


## 4. Comparator

E.g. Low Battery indicator

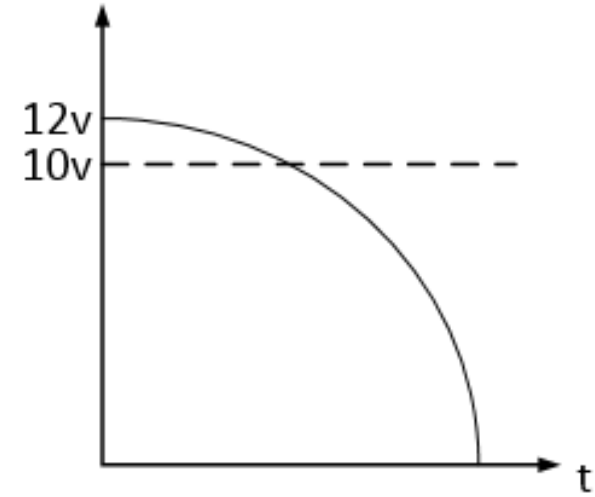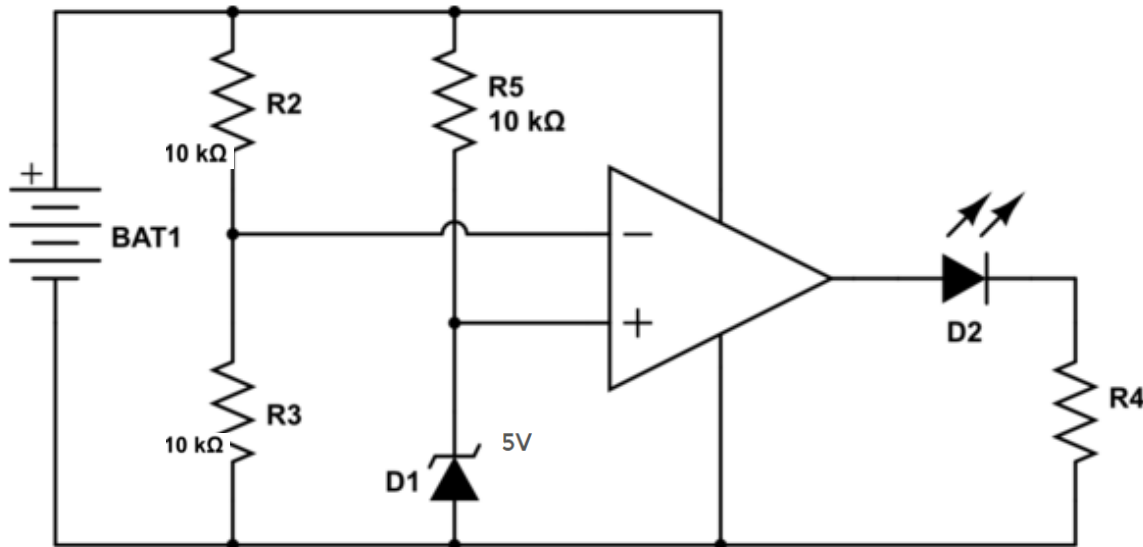

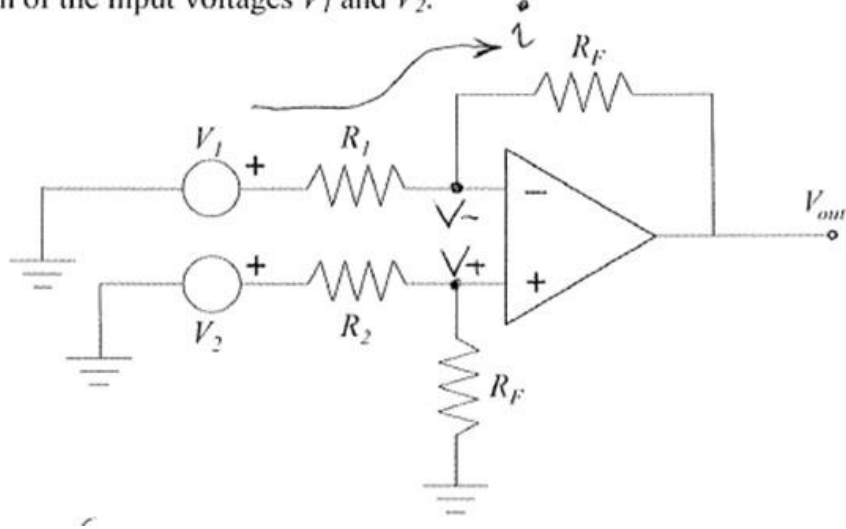
# Op-Amp Application (Practice)

The following is the schematic of a difference amplifier circuit. Find the output voltage  $V_{out}$  as a function of the input voltages  $V_1$  and  $V_2$ .



# Op-Amp Application

## 5. Summing Op-Amp

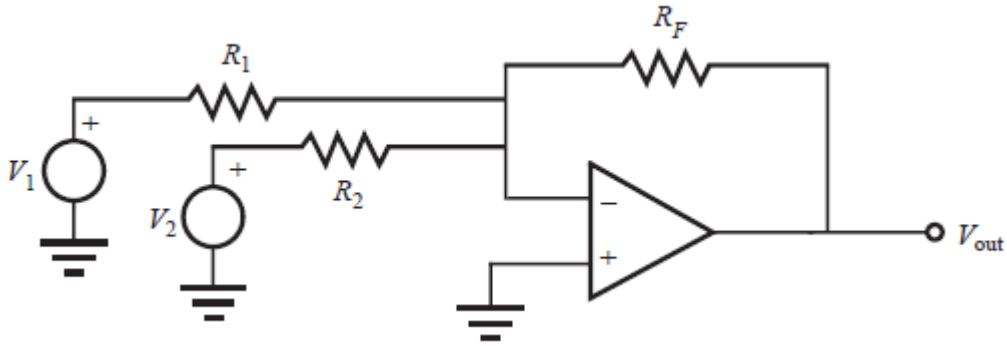

$$V_{out} = -\frac{R_F}{R_1}V_1 - \frac{R_F}{R_2}V_2 \quad (4.11)$$


Golden rules:

$$I_+ = I_- = 0$$

$$V_+ = V_-$$

# Op-Amp Application

## 6. Integrator

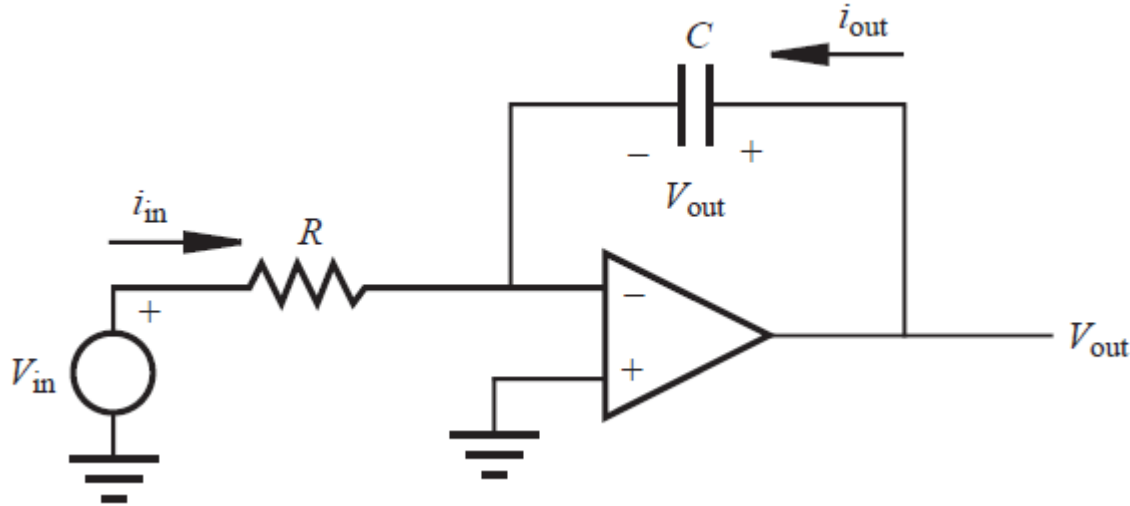

Golden rules:

$$I_+ = I_- = 0$$

$$V_+ = V_-$$

$$\frac{dV_{\text{out}}}{dt} = \frac{i_{\text{out}}}{C} \quad (4.12)$$

$$V_{\text{out}}(t) = \frac{1}{C} \int_0^t i_{\text{out}}(\tau) d\tau \quad (4.13)$$


Since  $i_{\text{out}} = -i_{\text{in}}$  and  $i_{\text{in}} = V_{\text{in}}/R$ ,

$$V_{\text{out}}(t) = -\frac{1}{RC} \int_0^t V_{\text{in}}(\tau) d\tau \quad (4.14)$$



# Op-Amp Application

## 7. Differentiator

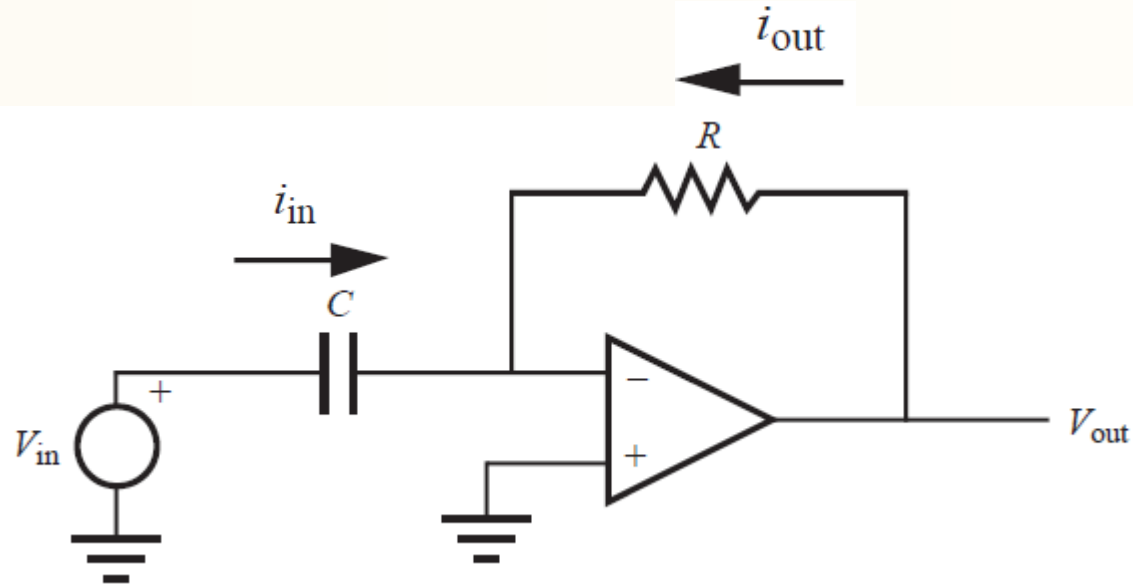

$$\frac{dV_{in}}{dt} = \frac{i_{in}}{C} \quad (4.13)$$

Since  $i_{in} = -i_{out}$  and  $i_{out} = V_{out}/R$ ,


$$V_{out} = -RC \frac{dV_{in}}{dt} \quad (4.14)$$

Golden rules:

$$I_+ = I_- = 0$$

$$V_+ = V_-$$

# Summary

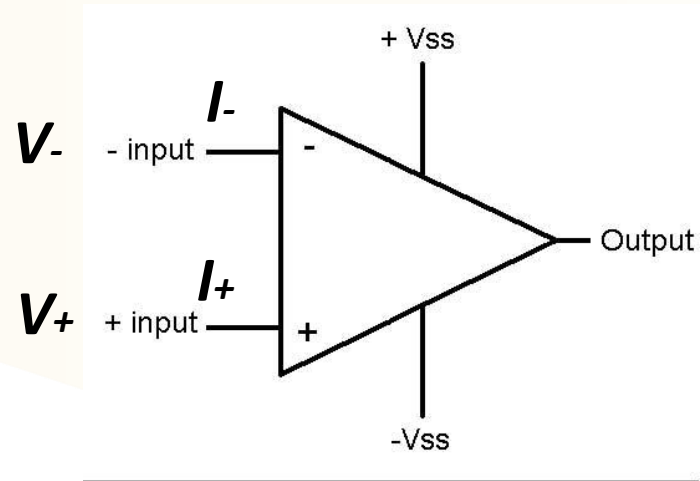

Golden rules:

$$I_+ = I_- = 0$$

$$V_+ = V_-$$

Kirchhoff's Current Law

Electronic component characteristics