

Signals and Circuits

ENGR 35500

Kirchhoff's law


2-2 (Kirchhoff's Law)

Ulaby, Fawwaz T., and Maharbiz, Michael M., *Circuits*, 2nd Edition, National Technology and Science Press, 2013.



Kirchhoff's Current Law (KCL)

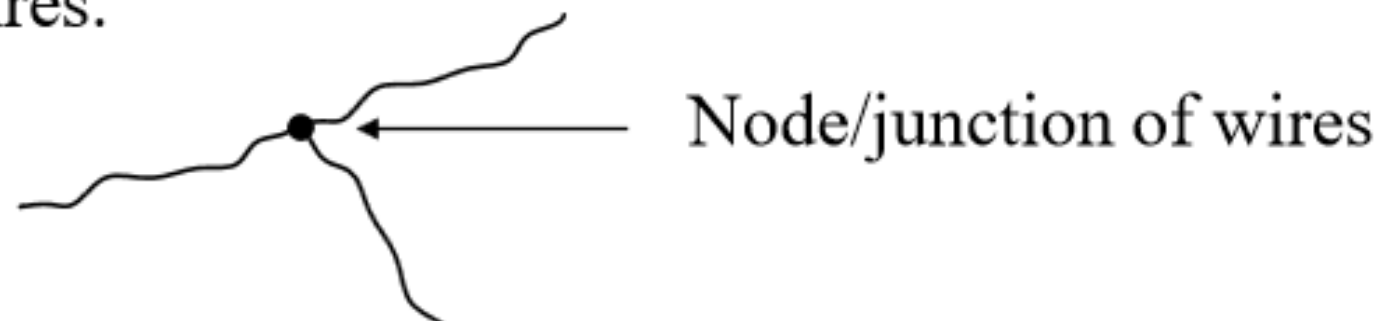- Conservation of charge implies that charge is neither created nor destroyed in electrical circuits.
- This principle leads directly to a constraint on the current at a junction (node) of wires.



- KCL: Because charge is conserved, the sum of currents (Algebraic sum of all currents) leaving (or entering) a node is zero at all times.

$$\sum_{k=1}^n I_k = 0$$


Kirchhoff's Current Law (KCL)

A Common convention is to assign a positive “+” sign to a current if it entering the node and a negative “-” sign if it is leaving it.

$$i_1 - i_2 - i_3 + i_4 = 0$$




$$i_1 + i_4 = i_2 + i_3$$

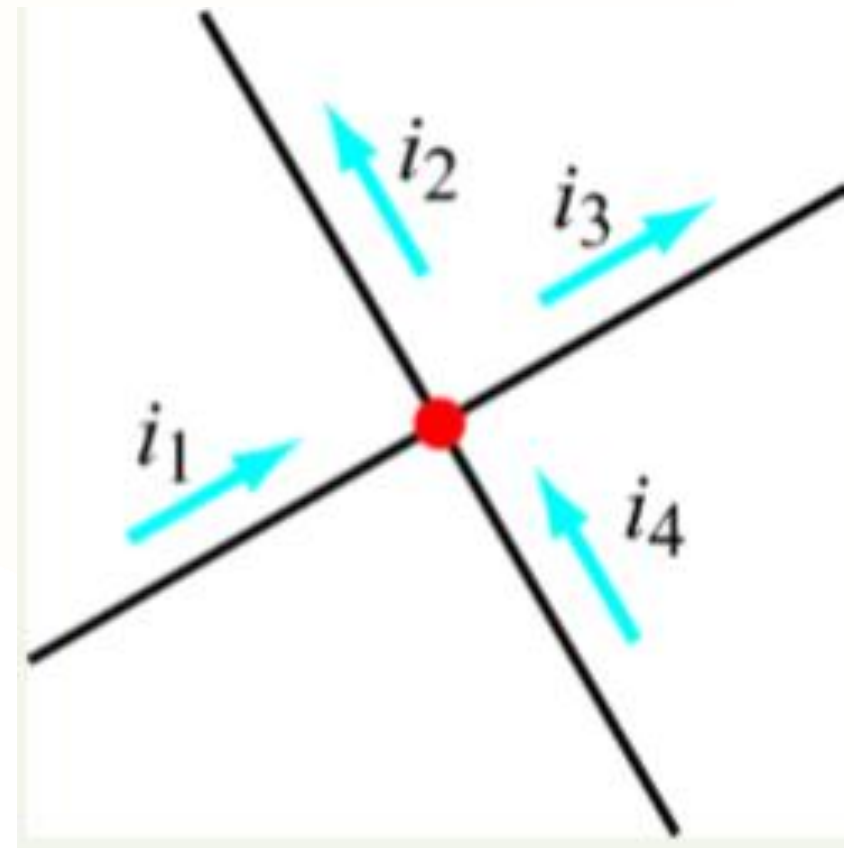


Kirchhoff's Current Law (KCL)

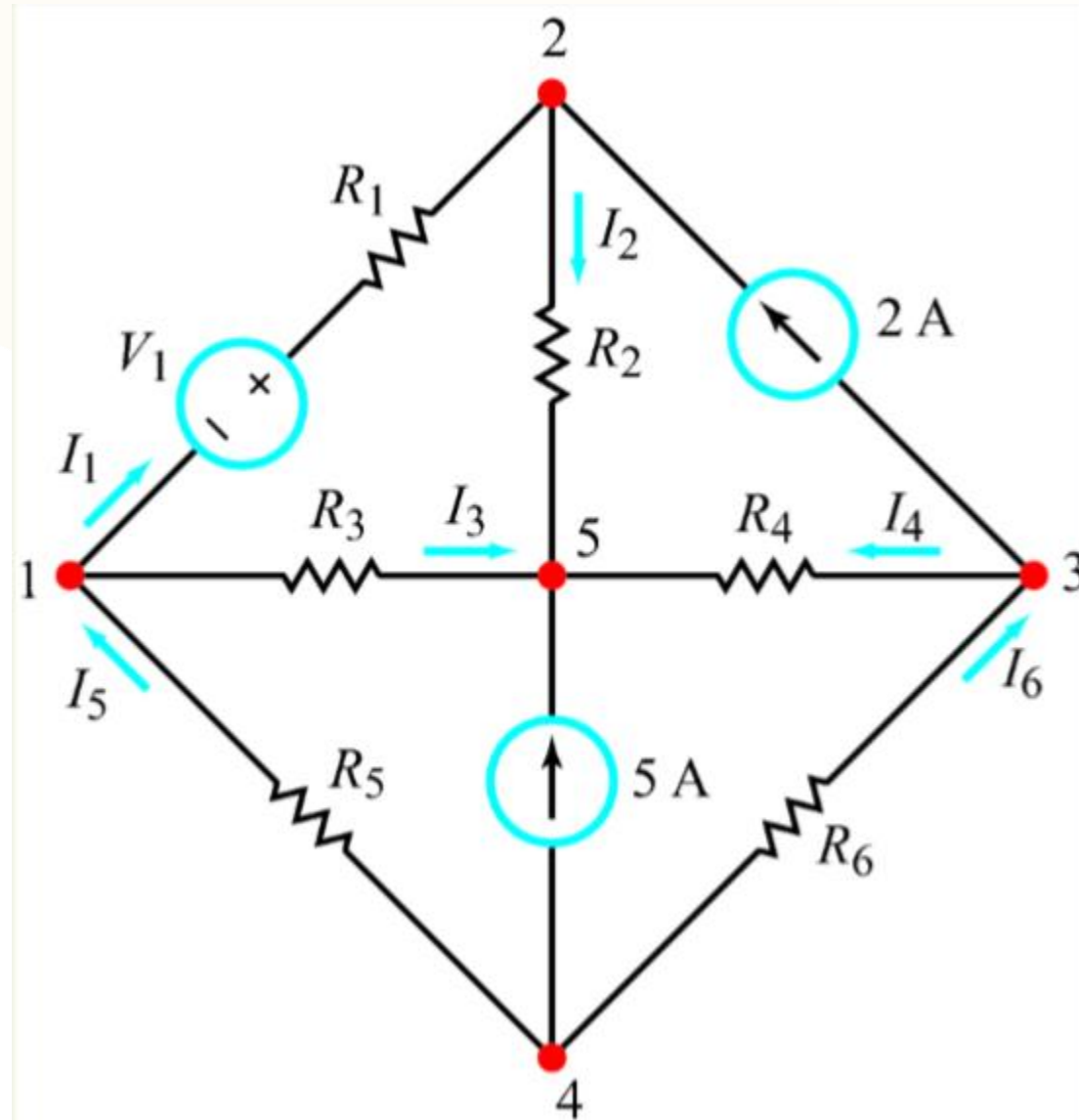Write the KCL equations at nodes 1 through 5 in the circuit.




Kirchhoff's Current Law (KCL)

Example: Find i_2

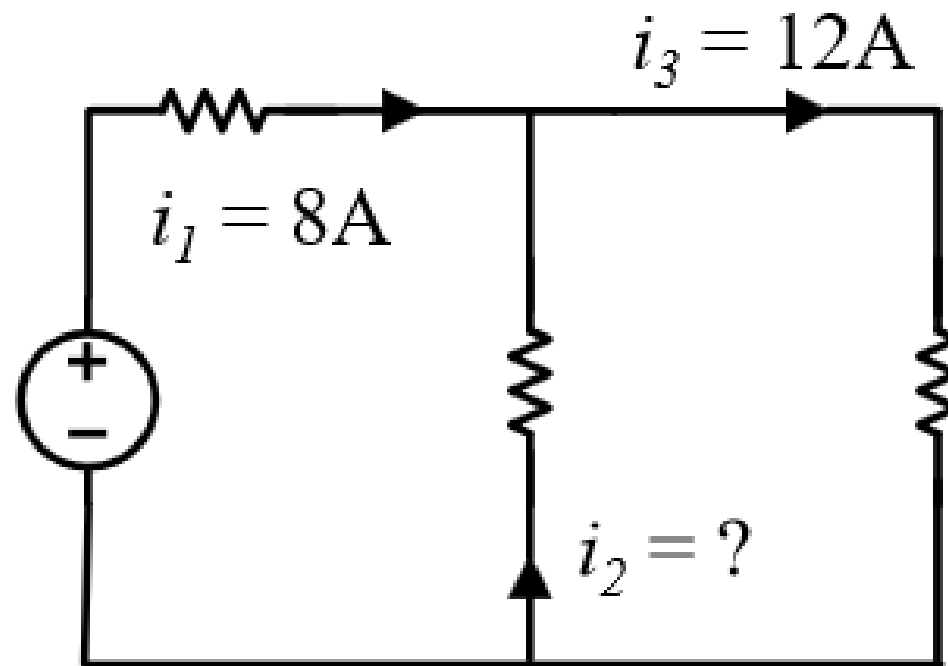

Kirchhoff's Current Law (KCL)

Conservation of Power **VS** KCL

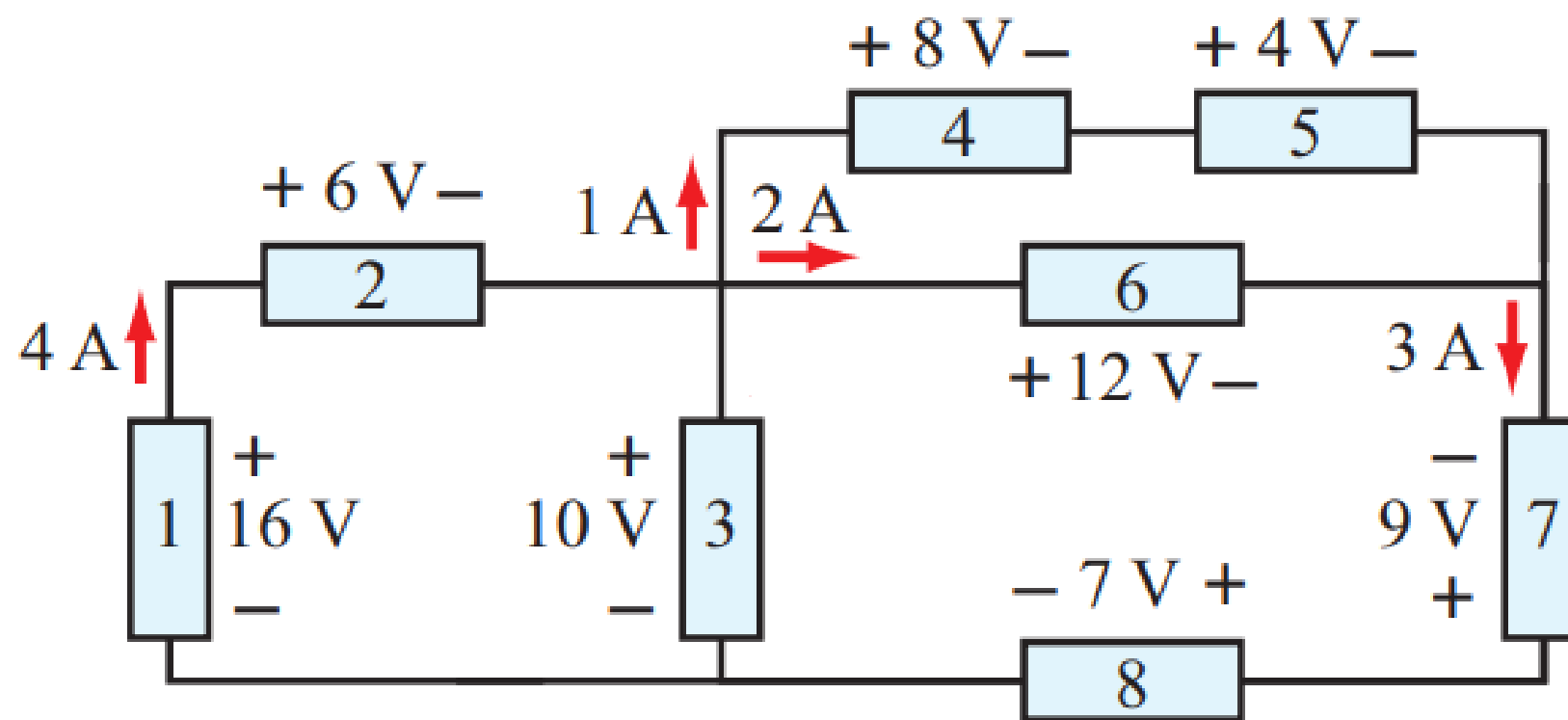

Kirchhoff's Voltage Law (KVL)

The law of conservation of energy mandates that if we move electric charge around a closed loop, starting and ending at exactly the same location, the net gain or loss of energy must be zero.

The algebraic sum of the voltages around a closed loop must always be zero.


$$\sum_{n=1}^N v_n = 0 \quad (KVL)$$

Kirchhoff's Voltage Law (KVL)

Sign Convention

Add up the voltages in a systemic clockwise movement around the loop.

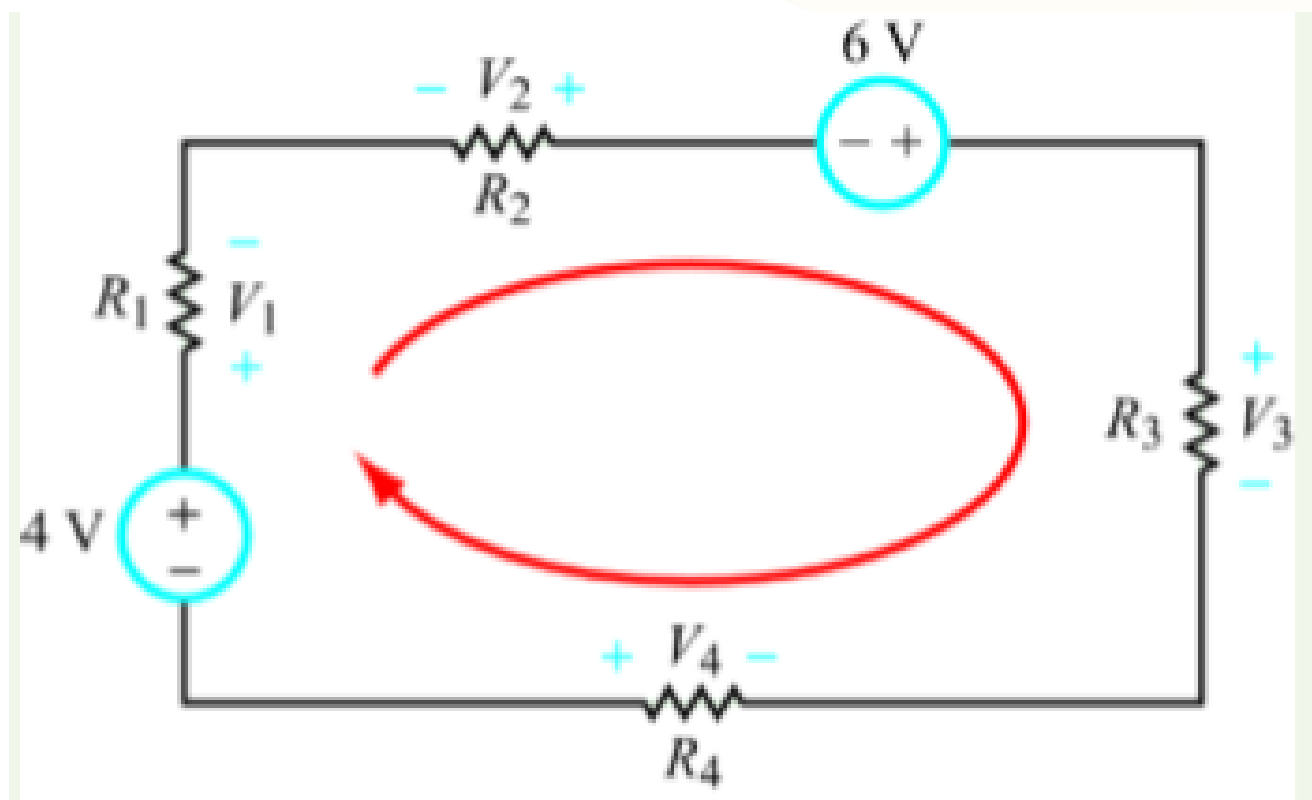Assign a positive sign to the voltage across an element if the (+) side of that voltage is encountered first, and assign a negative sign if the (-) side is encountered first.




$$-4 + V_1 - V_2 - 6 + V_3 - V_4 = 0$$

Kirchhoff's Voltage Law (KVL)

Sign Convention

Add up the voltages in a systemic clockwise movement around the loop.

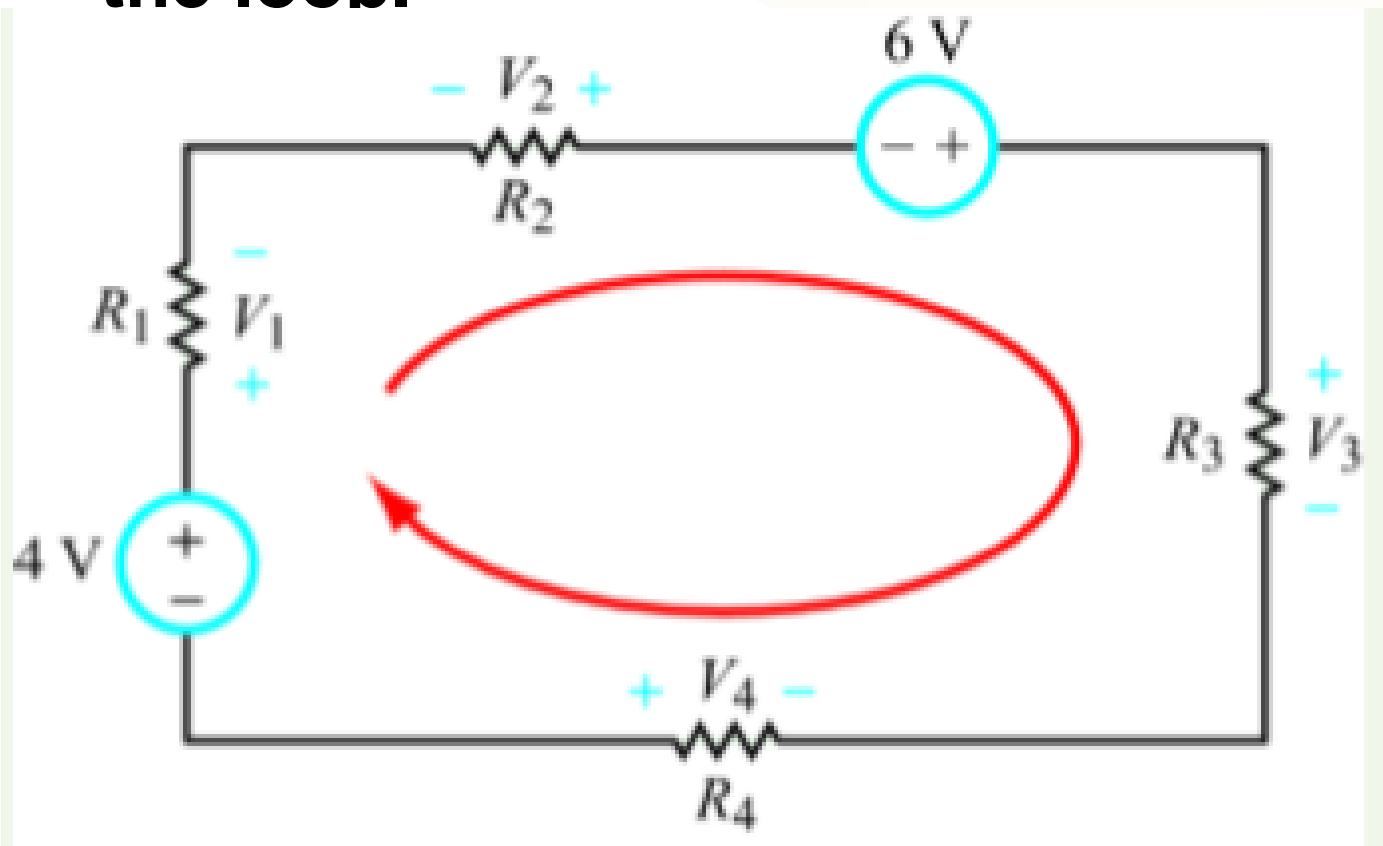
Alternative statement of KVL is that the total voltage rise around a closed loop must equal the total voltage drop around the loop.



$$4 + V_2 + 6 + V_4 = V_1 + V_3$$

Kirchhoff's Voltage Law (KVL)

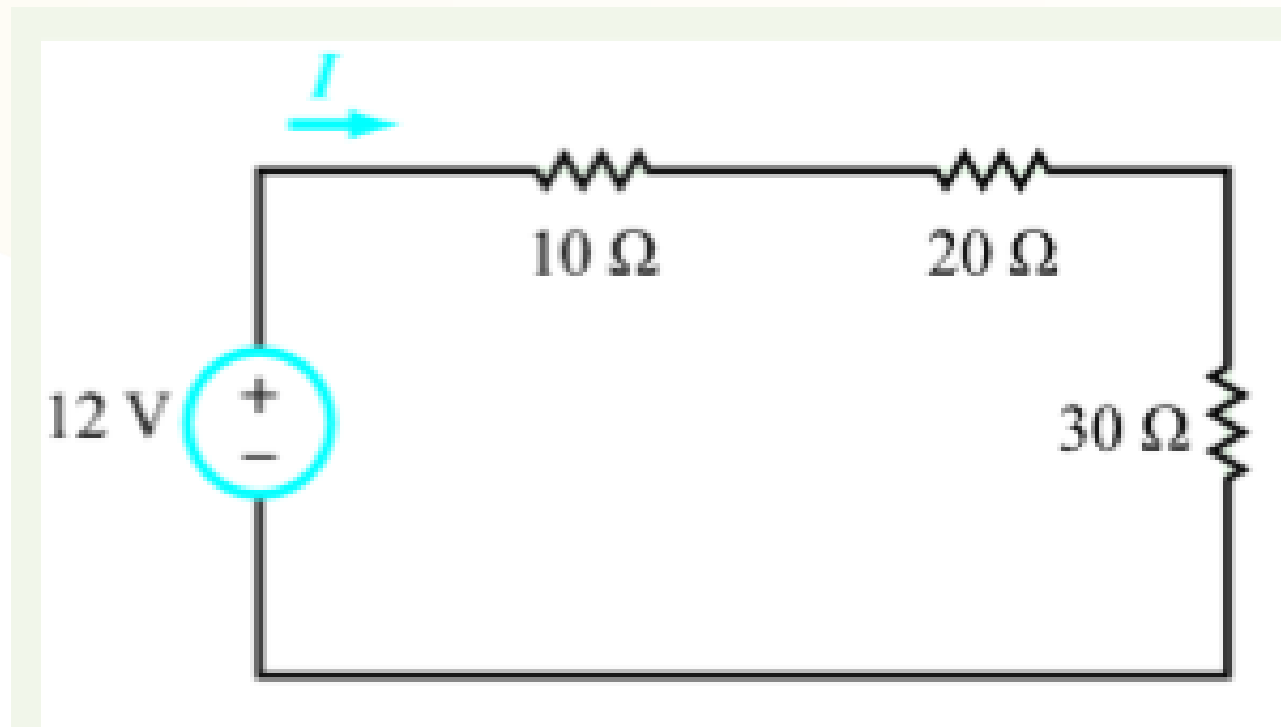
Determine the value of current I in the circuit.



Kirchhoff's Law

Determine

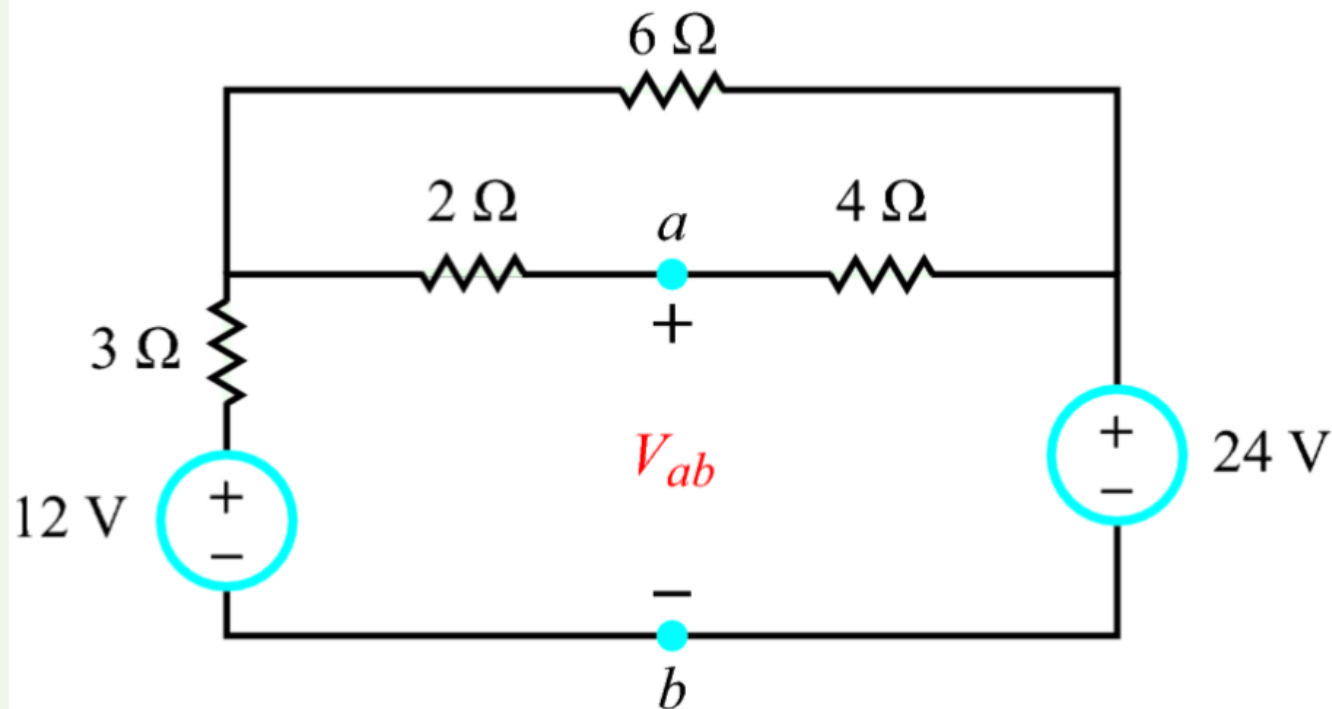- The current through each of the other resistors;
- The voltage of V_{ab} ;
- The power delivered to the circuit by the battery on the right.




Steps:

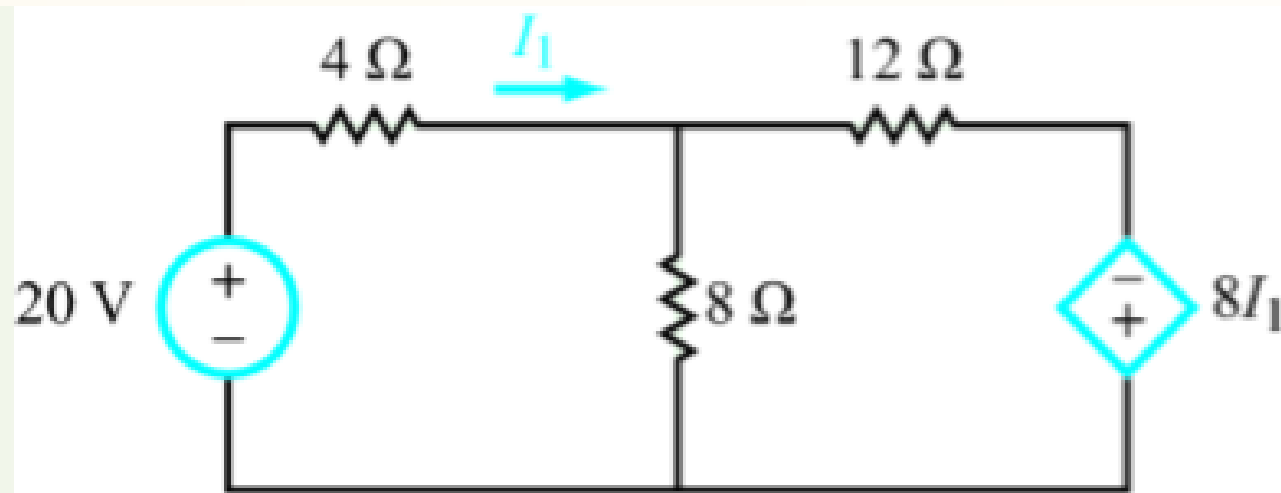1. Labels
2. Distinguish loops
3. KVL
4. Ohm's law
5. KCL
6. Simultaneous solution of equations

Kirchhoff's Law

Determine the amount of power consumed by the $12\ \Omega$ resistor.



Steps:

1. Labels
2. Distinguish loops
3. KVL
4. Ohm's law
5. KCL
6. Simultaneous solution of equations